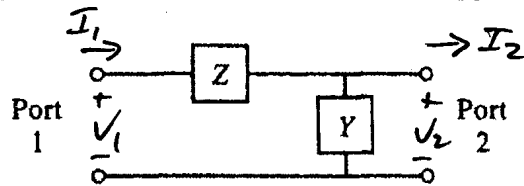



- 4.23 Find the $ABCD$ matrix for the circuit shown below by direct calculation using the definition of the $ABCD$ matrix, and compare with the $ABCD$ matrix of the appropriate cascade of canonical circuits from Table 4.1.

Direct
Calculation



Per text (pp. 190-191), $A = \frac{V_1}{V_2} \big|_{I_2=0}$ & $C = \frac{I_1}{V_2} \big|_{I_2=0}$

$$B = \frac{V_1}{I_2} \big|_{V_2=0} \text{ & } D = \frac{I_1}{I_2} \big|_{V_2=0}$$

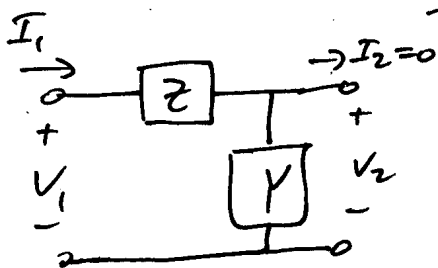


By voltage division

$$V_2 = V_1 \frac{\frac{1}{Y}}{Z + \frac{1}{Y}} = V_1 \left(\frac{1}{YZ + 1} \right)$$

$$\underline{\underline{A = \frac{V_1}{V_2} = YZ + 1 = 1 + YZ}}$$

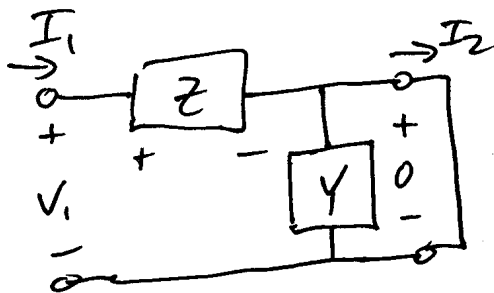By Ohm's Law $V_2 = I_1 / Y \Rightarrow \underline{\underline{C = Y}}$




$$I_2 = I_1 \Rightarrow \underline{\underline{D = \frac{I_1}{I_2} = 1}}$$

By KVL, $V_1 = I_1 Z + 0$


$$\hookrightarrow \underline{\underline{B = \frac{V_1}{I_1} = Z}}$$

$$\boxed{\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + YZ & Z \\ Y & 1 \end{bmatrix}}$$

From Table 4.1

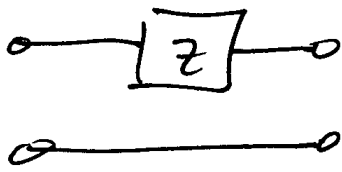
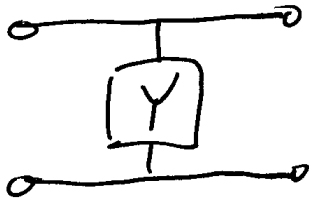
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_Z = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_Y = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

Per (4.71),

$$\begin{aligned} \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{TOT} &= \begin{bmatrix} A & B \\ C & D \end{bmatrix}_Z \begin{bmatrix} A & B \\ C & D \end{bmatrix}_Y \\ &= \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \end{aligned}$$

$$\boxed{\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + YZ & Z \\ Y & 1 \end{bmatrix}}$$

Same answer!