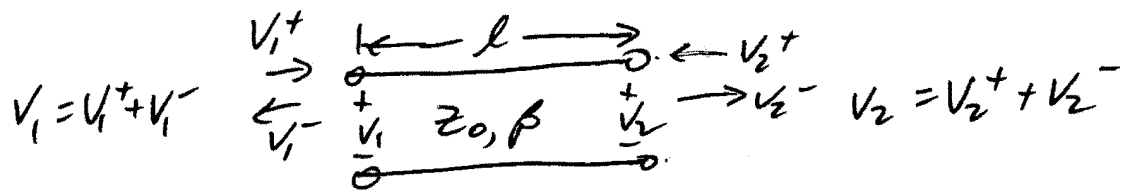
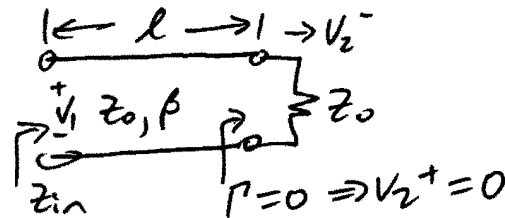


Find the S-parameters of a matched lossless transmission line (TL) with a characteristic impedance Z_0 and an electrical length βl .



Per (4.41), $S_{ij} = \frac{V_i^-}{V_j^+} \Big|_{V_k^+ = 0 \text{ for } k \neq j}$

S_{11} & S_{21} $V_2^+ = 0 \Rightarrow Z_L = Z_0$ on port 2



$S_{11} = \frac{V_1^-}{V_1^+} = \Gamma_1 = 0$ since $Z_{in} = Z_0$

By symmetry, $S_{22} = S_{11} = 0$

$S_{21} = \frac{V_2^-}{V_1^+}$

Per (2.36a), $V(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$

Here, $V_0^+ = V_2^-$ and $\Gamma = 0 \Rightarrow V(z) = V_2^- e^{-j\beta z}$

@ $z = -l$, $V(-l) = V_1 = V_2^- e^{-j\beta(-l)}$

$V_1^+ + \underbrace{V_1^-}_{=0 \text{ (since } \Gamma_1 = 0)} = V_2^- e^{j\beta l} \Rightarrow \underline{\underline{S_{21} = e^{-j\beta l} = S_{12}}}$

$[S] = \begin{bmatrix} 0 & e^{-j\beta l} \\ e^{-j\beta l} & 0 \end{bmatrix}$