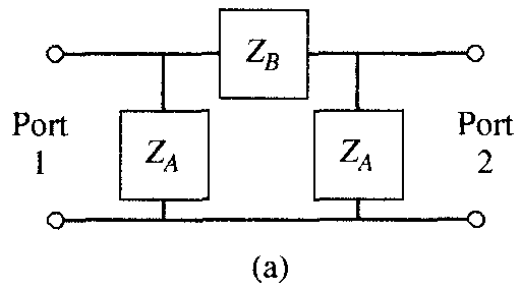


Evaluate $[S]$ for the pi-network of problem 4.7a when $Z_A = -j50 \Omega$, $Z_B = 100 + j40 \Omega$, and $Z_0 = 50 \Omega$.



Method 1

Use equations from prior problem with $Z_A = -j50 \Omega$ and $Z_B = 100 + j40 \Omega$.

$$Z_A := -j \cdot 50 \quad \Omega \qquad Z_B := 100 + j \cdot 40 \quad \Omega \qquad Z_0 := 50 \quad \Omega$$

$$S_{11} := \frac{Z_A^2 \cdot Z_B - Z_B \cdot Z_0^2 - 2 \cdot Z_A \cdot Z_0^2}{Z_A^2 \cdot Z_B + 2 \cdot Z_A \cdot Z_B \cdot Z_0 + 2 \cdot Z_A^2 \cdot Z_0 + Z_B \cdot Z_0^2 + 2 \cdot Z_A \cdot Z_0^2}$$

$$S_{21} := \left[\frac{2 \cdot (Z_A^2 \cdot Z_B + Z_A \cdot Z_B \cdot Z_0 + Z_A^2 \cdot Z_0)}{Z_A^2 \cdot Z_B + 2 \cdot Z_A \cdot Z_B \cdot Z_0 + 2 \cdot Z_A^2 \cdot Z_0 + Z_B \cdot Z_0^2 + 2 \cdot Z_A \cdot Z_0^2} \right] \cdot \left(\frac{Z_A \cdot Z_0}{Z_A \cdot Z_B + Z_A \cdot Z_0 + Z_B \cdot Z_0} \right)$$

$$S_{12} := S_{21} \qquad S_{22} := S_{11}$$

$$|S_{11}| = 0.66851$$

$$\arg(S_{11}) \cdot \frac{180}{\pi} = -91.89652 \quad \text{deg}$$

$$|S_{12}| = 0.3326$$

$$\arg(S_{12}) \cdot \frac{180}{\pi} = -86.18593 \quad \text{deg}$$

$$|S_{21}| = 0.3326$$

$$\arg(S_{21}) \cdot \frac{180}{\pi} = -86.18593 \quad \text{deg}$$


$$|S_{22}| = 0.66851$$

$$\arg(S_{22}) \cdot \frac{180}{\pi} = -91.89652 \quad \text{deg}$$

$$[S] = \begin{bmatrix} 0.6685 \angle -91.897^\circ & 0.3326 \angle -86.186^\circ \\ 0.3326 \angle -86.186^\circ & 0.6685 \angle -91.897^\circ \end{bmatrix}$$

Method 2 Direct calculation

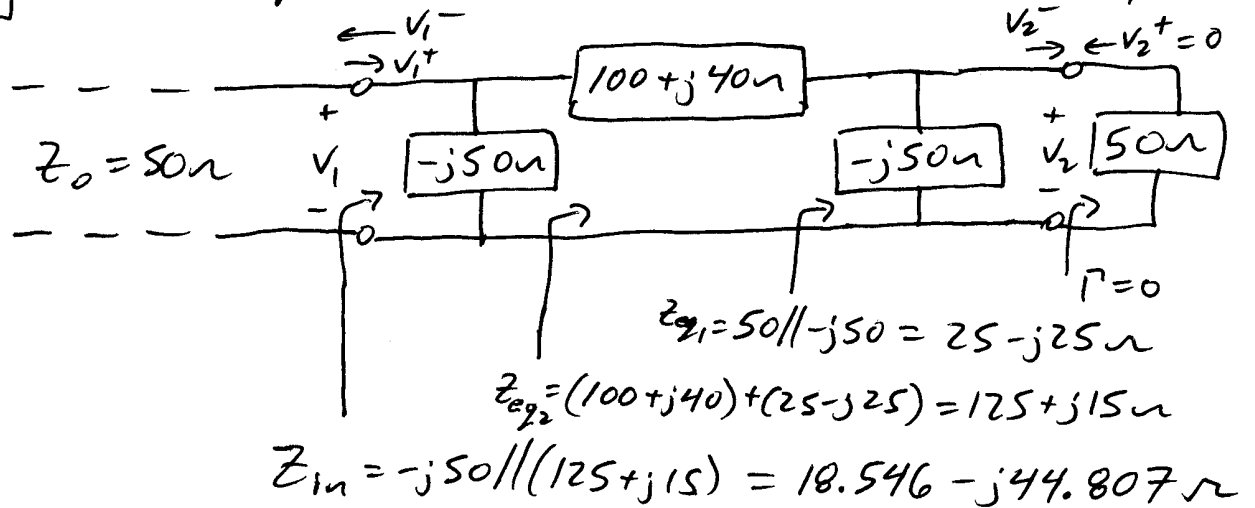S_{11} Match port 2 with load $Z_L = Z_0 = 50\Omega$,



$$S_{11} = \Gamma_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{(18.546 - j44.807) - 50}{(18.546 - j44.807) + 50}$$

$$\underline{\underline{S_{11} = 0.668508 \angle -91.89652^\circ = S_{22} \text{ (symmetry)}}}$$

S_{21} Same Circuit. Find $V_2^- = V_2$ (voltage across $Z_L = Z_0$) in terms of V_1^+ .

By voltage division $V_2 = V_2^- = V_1 \frac{Z_{eq1}}{Z_{eq2}} = V_1^+ (1 + \Gamma_{11}) \frac{Z_{eq1}}{Z_{eq2}}$

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0} = (1 + \Gamma_{11}) \frac{Z_{eq1}}{Z_{eq2}}$$

$$= (1 + 0.668508 \angle -91.89652^\circ) \left(\frac{25 - j25}{125 + j15} \right)$$

$$\underline{\underline{S_{21} = 0.332595 \angle -86.185925^\circ = S_{12} \text{ (symmetry)}}}$$