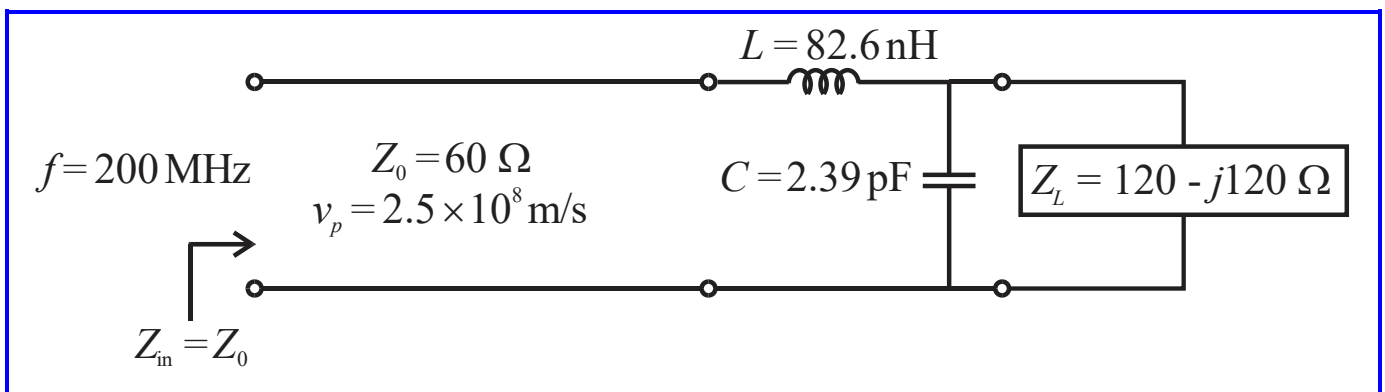


For a circuit operating at 200 MHz, design and sketch a lossless L -network using a parallel capacitor to match a load $Z_L = 120 - j120 \Omega$ to a lossless transmission line (60Ω , 2.5×10^8 m/s). Use Smith chart solution method and give component values to 3 significant figures. Confirm component values using analytic equations.

- Note that $R_L = 120 \Omega > Z_0 = 60 \Omega \Rightarrow L$ -network has parallel capacitor first, then series element.
- Calculate the normalized load impedance $z_L = Z_L / Z_0 = (120 - j120) / 60 \Rightarrow \mathbf{z_L = 2 - j2 \Omega/\Omega}$. Plot z_L on Smith chart.
- Use compass to draw a circle through z_L , centered on Smith chart. Use a straight edge to draw line through center of Smith chart & z_L to outer rings of Smith chart.
- Move 180° around circle of constant $|\Gamma|$ from z_L point to $\mathbf{y_L = 0.25 + j0.25 \text{ S/S}}$.
- Draw rotated $r = 1$ circle.
- Follow the $g_L = 0.25 \text{ S/S}$ circle from y_L to where it intersects the rotated $r = 1$ circle at $\mathbf{y_{m,L} = 0.25 - j0.43 \text{ S/S}}$ and $\mathbf{y_{m,C} = 0.25 + j0.43 \text{ S/S}}$. Choose $y_{m,C}$ as it requires a parallel capacitor.
- Calculate $b_{\text{cap}} = b_{m,C} - b_L = 0.43 - 0.25 = 0.18 \text{ S/S}$. Then, calculate $C = b_{\text{cap}} / \omega Z_0 = 0.18 / [(2\pi)200 \times 10^6 (60)] \Rightarrow \mathbf{C = 2.3873 \times 10^{-12} \text{ F} = 2.39 \text{ pF}}$.
- Draw a circle through $y_{m,C}$, centered on Smith chart. Use a straight edge to draw line through center of Smith chart & $y_{m,C}$ to outer rings of Smith chart.
- Move 180° around this circle of constant $|\Gamma|$ from $y_{m,C}$ point to $\mathbf{z_{m,c} = 1 - j1.73 \Omega/\Omega}$.
- To match, add a series normalized inductive reactance of $1.74 \Omega/\Omega$. The inductor required is $L = x_{\text{ind}} Z_0 / \omega = 1.73(60) / [(2\pi)200 \times 10^6] \Rightarrow \mathbf{L = 8.260 \times 10^{-8} \text{ H} = 82.6 \text{ nH}}$.




Simple Smith Chart

$$Z_0 = 60 \, \Omega$$

$$f = 200 \, \text{MHz}$$

$$v_p = 2.5 \cdot 10^8 \, \text{m/s}$$

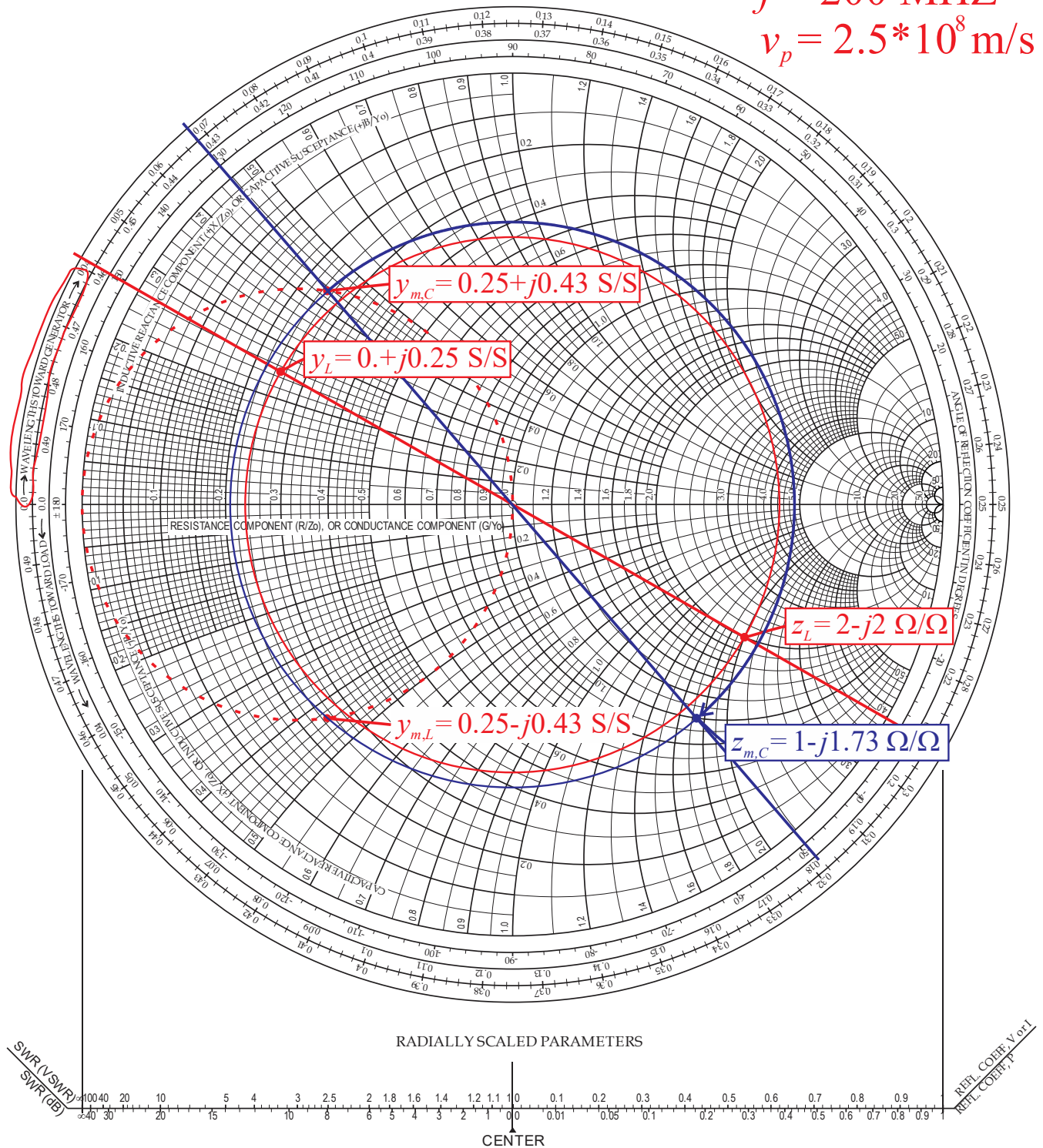

Verify using analytic equations-

First, use (5.3a)

$$\begin{aligned}
 B &= \frac{X_L \pm \sqrt{R_L / Z_0} \sqrt{R_L^2 + X_L^2 - Z_0 R_L}}{R_L^2 + X_L^2} \\
 &= \frac{-120 \pm \sqrt{120 / 60} \sqrt{(120)^2 + (-120)^2 - 60(120)}}{(120)^2 + (-120)^2} \\
 &= \frac{-120 \pm 207.8460969}{28800} \\
 &\Rightarrow B = 0.0030502 \text{ S (capacitive)} \text{ or } B = -0.01138545 \text{ S.}
 \end{aligned}$$

Next, use (5.3b)

$$\begin{aligned}
 X &= \frac{1}{B} + \frac{X_L Z_0}{R_L} - \frac{Z_0}{B R_L} = \frac{1}{0.0030502} + \frac{-120(60)}{120} - \frac{60}{0.0030502(120)} \\
 &\Rightarrow X = 103.923677 \Omega \text{ (inductive)}
 \end{aligned}$$

Parallel capacitor value

$$C = B/\omega = 0.0030502 / [(2\pi)200 \times 10^6] \Rightarrow C = 2.4273 \times 10^{-12} \text{ F} = 2.43 \text{ pF}.$$

This is a touch higher than the 2.39 pF value found using Smith chart.

Series inductor value

$$L = X/\omega = 103.923677 / [(2\pi)200 \times 10^6] \Rightarrow L = 8.1904 \times 10^{-8} \text{ H} = 81.9 \text{ nH}.$$

This is a bit lower than the 82.6 nH value found using Smith chart.