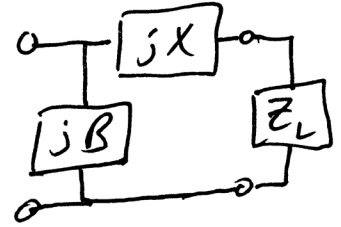


For a circuit operating at 125 MHz, design and sketch a lossless  $L$ -network using a series inductor match a load  $Z_L = 150 + j120 \Omega$  to a lossless transmission line ( $300 \Omega$ ,  $2.8 \times 10^8$  m/s). Use Smith chart solution method. Confirm results using analytic equations.

Note that  $R_L = 150 \Omega < Z_0 = 300 \Omega$

$L$ -network



Follow notes:

→ Calculate  $y_L = \frac{Z_L}{Z_0} = \frac{150 + j120}{300} = 0.5 + j0.4 \Omega$  and plot on Smith Chart.

→ On circle of constant  $r_L = 0.5 \Omega$  go CW (add more inductive reactance) to get to  $y_{m,top} = 0.5 + j0.5 \Omega = r_L + jx_m$

→  $x_m = X_L + x = 0.5 = 0.4 + x \Rightarrow x = 0.1$ .

The required series inductance is


$$\text{then } L = \frac{x Z_0}{\omega} = \frac{0.1(300)}{2\pi(125 \times 10^6)} \Rightarrow \underline{\underline{L = 38.197 \text{ nH}}}$$

→ Go  $\lambda/4$  around Smith Chart on circle of constant  $|r|$  to arrive at  $y_{m,top} = 1 - j1 \text{ S/S} = 1 - jb_{m,top}$


→ Since  $b_{m,top} = -1 \text{ S/S}$ , we need a parallel capacitor to match.  $C = \frac{b_{cap}}{\omega Z_0} = \frac{1}{2\pi(125 \times 10^6) 300}$   
C = 4.244 pF

NAME	TITLE	DWG. NO.
SMITH CHART FORM ZY-01-N	ANALOG INSTRUMENTS COMPANY, NEW PROVIDENCE, N.J. 07974	DATE
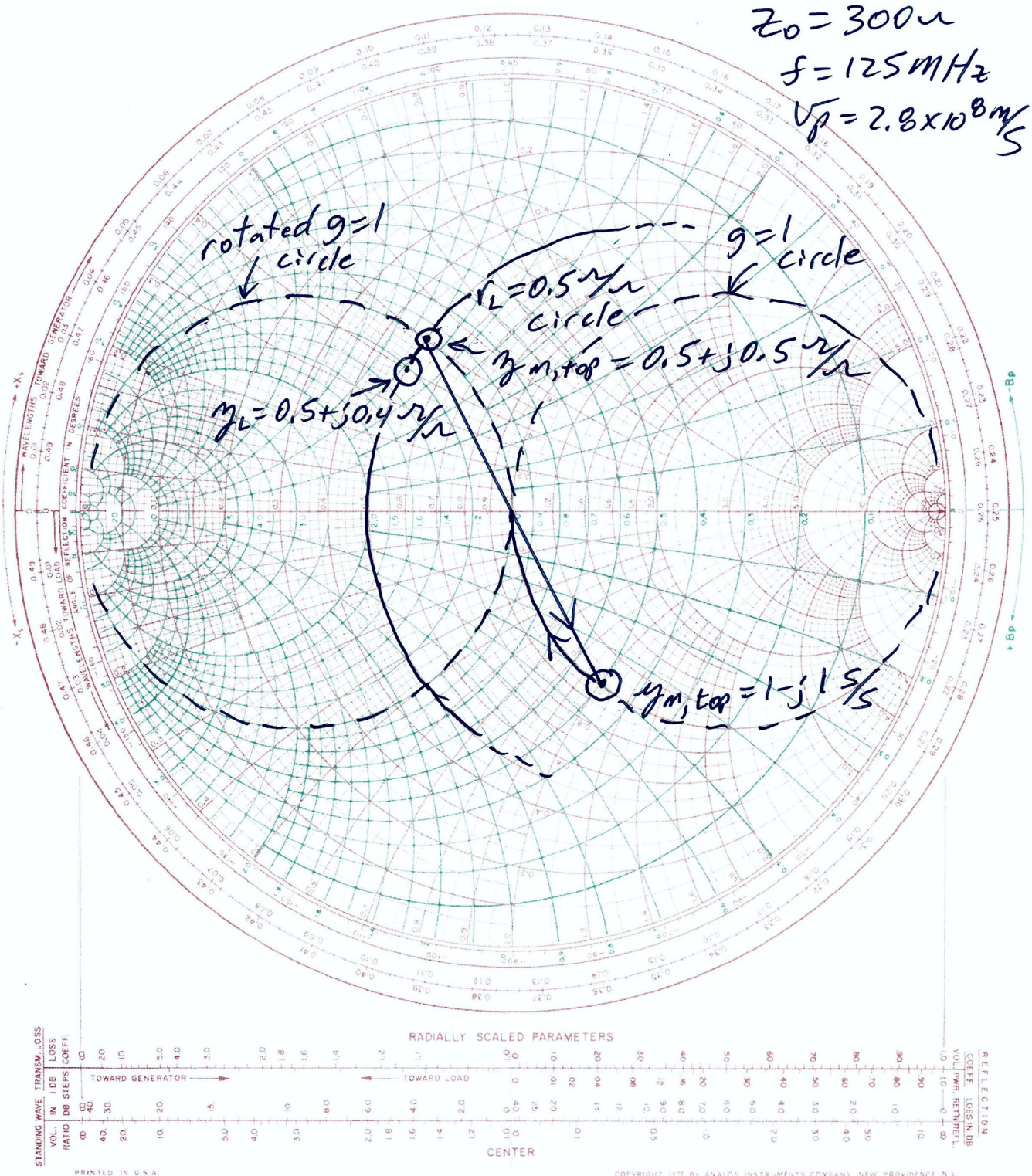
## NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



# Smith Chart L-network design

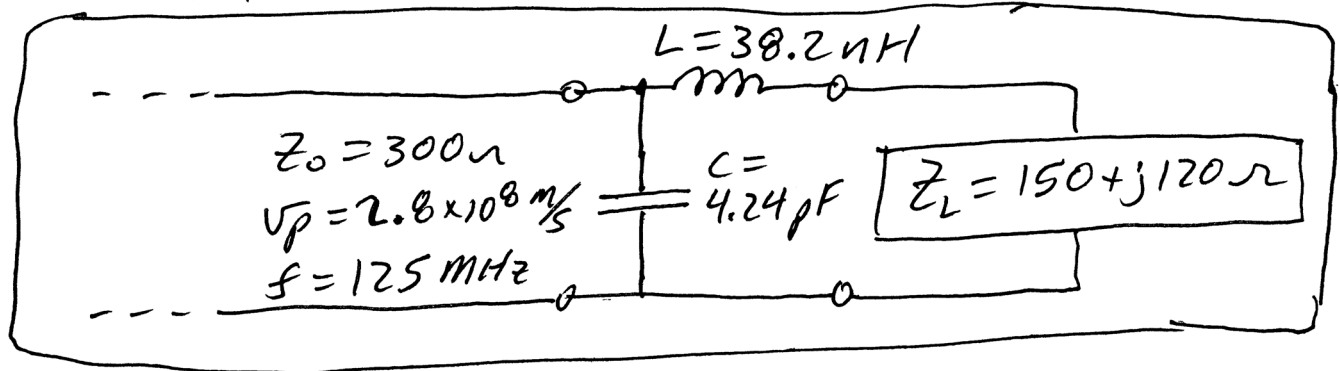

Verify design using analytic equations

$$(5.6a) \quad X = -X_L \pm \sqrt{R_L(Z_0 - R_L)} = -120 \pm \sqrt{150(300 - 150)}$$

$$= -120 \pm 150 = \underline{30 \Omega} \text{ or } -270 \Omega$$

↑ inductive reactance

$$L = \frac{X_{ind}}{\omega} = \frac{30}{2\pi(125 \times 10^6)} \Rightarrow \underline{\underline{L = 38.197 \text{ nH}}}$$

$$(5.6b) \quad B = \overset{\text{choose '+' sol'n}}{\frac{+ \sqrt{(Z_0 - R_L)/R_L}}{Z_0}} = \frac{\sqrt{(300 - 150)/150}}{300}$$

$$= \frac{1}{300} \text{ S} = \omega C \leftarrow \text{parallel}$$

$$C = \frac{1}{300(2\pi)125 \times 10^6}$$

$$\underline{\underline{C = 4.244 \text{ pF}}}$$

Both agree exactly w/ Smith chart solution!