

A lossless transmission line (75Ω , 1.98×10^8 m/s) has a load of $16.5 - j34.5 \Omega$ at 2.2 GHz. Design and sketch a quarter-wave transformer (QWT), using a Smith chart, to match the load with the QWT placed as close as possible to the load. Assume that the QWT section has a phase velocity of 2.08×10^8 m/s.

→ Calculate $y_L = \frac{Z_L}{Z_0} = \frac{16.5 - j34.5 \Omega}{75 \Omega} = 0.22 - j0.46 \text{ } \Omega$

→ Draw circle of $|Y| = 0.695$ through y_L

→ Note $y_{\min} = 0.18 \text{ } \Omega$ & $y_{\max} \approx 5.5 \text{ } \Omega$
closest

→ Find distance from y_L to $y_{\min}$ using WTL Scale $l_{\min} = 0.5 - 0.429 \lambda = \underline{\underline{0.071 \lambda}}$

where $\lambda = \frac{v_p}{f} = \frac{1.98 \times 10^8}{2.2 \times 10^9} = 9 \text{ cm} = \underline{\underline{0.639 \text{ cm}}}$


→ Use $Z_1 = \sqrt{Z_0 Z_{\min}} = \sqrt{75 (0.18) 75} = \sqrt{75 (13.5)}$

$Z_1 = 31.82 \Omega$ for $\lambda/4$ section

where $\lambda_1 = \frac{2.08 \times 10^8}{2.2 \times 10^9} = 0.0945 \text{ m} = 9.45 \text{ cm}$

↳ $\lambda_{1/4} = 2.36 \text{ cm}$

QWT Design

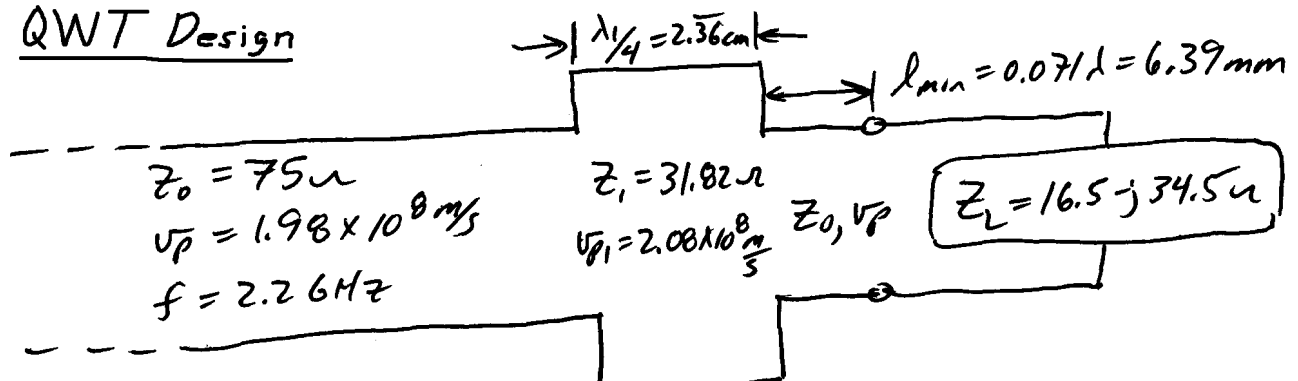

Simple Smith Chart

$$Z_0 = 75 \Omega$$

$$V_p = 1.98 \times 10^8 \text{ m/s}$$

$$f = 2.2 \text{ GHz}$$

