

A lossless transmission line ( $300 \Omega$ ,  $2 \times 10^8$  m/s) of length 125 cm connects a load of  $180 + j240 \Omega$  to a matched 16 V generator operating at 500 MHz. Using a Smith chart, find the unmatched input impedance and load power. Then, design and sketch a shunt double-stub tuning network with short circuit terminations. Place the stubs at  $\lambda/8$  intervals and make the stubs as short as possible. Find the matched input impedance and load power.

$$\text{Calculate } \lambda = v_p/f = 2 \times 10^8 / 500 \times 10^6 \Rightarrow \lambda = 0.4 \text{ m} = 40 \text{ cm.}$$

$$\text{Calculate } d_L = d = \lambda/8 = (0.4)/8 \Rightarrow \underline{d_L = d = 0.05 \text{ m} = 5 \text{ cm.}}$$

- 1) Calculate the normalized load impedance  $z_L' = Z_L' / Z_0 = (180 + j240) / 300$  and admittance  $y_L' = Z_0 / Z_L' = 300 / (180 + j240)$ . Plot  $z_L' = 0.6 + j0.8 \Omega/\Omega$  and  $y_L' = 0.6 - j0.8 \text{ S/S}$  on the Smith chart.
- 2) Calculate TL length  $\ell / \lambda = 125/40 = 3.125 \Rightarrow 0.125$ . Move  $0.125\lambda$  on an arc/circle of constant radius  $|\Gamma|$  in the “WAVELENGTHS TOWARD GENERATOR” direction (CW) from  $z_L'$  to  $z_{in,NM} = r_{\max} = 3 \Omega/\Omega$ . Calculate the unmatched input impedance as  $Z_{in,NM} = z_{in,NM} Z_0 = 3(300) \Rightarrow \underline{Z_{in,NM} = 900 \Omega}$ .
- 3) Calculate the unmatched phasor input current and voltage as

$$\bar{I}_{in,NM} = \frac{\bar{V}_g}{Z_g + Z_{in,NM}} = \frac{16 \angle 0^\circ}{300 + 900} \Rightarrow \underline{\bar{I}_{in,NM} = 0.01333 \angle 0^\circ \text{ A}} \text{ and}$$

$$\bar{V}_{in,NM} = \bar{V}_g \frac{Z_{in,NM}}{Z_g + Z_{in,NM}} = (16 \angle 0^\circ) \frac{900}{300 + 900} \Rightarrow \underline{\bar{V}_{in,NM} = 12 \angle 0^\circ \text{ V.}}$$

For a lossless TL, the input power and load power are the same.

$$P_{L,NM} = P_{in,NM} = 0.5 \text{Re}\{V_{in,NM} I_{in,NM}^*\} = 0.5 \text{Re}\{12(0.0133)\} \Rightarrow \underline{P_{L,NM} = 0.08 \text{ W} = 80 \text{ mW.}}$$

- 4) Draw the rotated ‘match’ circle  $g = 1$  at  $d/\lambda = \lambda/8$  in the “WAVELENGTHS TOWARD LOAD” direction, i.e., rotate  $90^\circ$  CCW. Note that  $g_0 = 2 \text{ S/S}$ .
- 5) Move the selected distance  $d_L/\lambda$  on an arc/circle of constant radius  $|\Gamma|$  in the “WAVELENGTHS TOWARD GENERATOR” direction (CW) from  $y_L'$  to  $y_L$ . Plot  $y_L = 0.33 \text{ S/S}$  on the Smith chart. Note that  $g_L < g_0$  (good).
- 6) From  $y_L$ , move along circle of constant  $g_L = 0.33 \text{ S/S}$  to where it intersects the rotated  $g = 1$  circle. There are two match points,  $y_{1a} = 0.33 + j0.255 \text{ S/S}$  or  $y_{1b} = 0.33 + j1.75 \text{ S/S}$ . To minimize the length of the first stub select  $y_{1a}$ . The normalized stub 1 susceptance  $b_{1a} = 0.255 - 0 \Rightarrow \underline{b_{1a} = 0.255 \text{ S/S}}$ .


- For the desired  $j0.255$  S/S, the length of a short-circuit terminated ( $y_{SC} \rightarrow \infty$ ) stub 1 is  $\ell_1 = 0.25\lambda + 0.039\lambda = 0.289(40 \text{ cm}) \Rightarrow \underline{\ell_1 \approx 11.56 \text{ cm}}$ .

7) Next, we will move the selected distance  $d/\lambda = \lambda/8 = 0.125\lambda$  on an arc/circle of constant radius  $|\Gamma|$  in the “WAVELENGTHS TOWARD GENERATOR” direction (CW) from  $y_{1a}$  to  $y_{1at}$ . This places us at  $y_{1at} = 1 - jb_2 = 1 + j1.24$  S/S on the  $g = 1$  ‘match’ circle.

8) Complete the match by adding shunt stub 2 with a normalized susceptance of  $jb_2 = -j1.24$  S/S. This yields  $y_2 = y_{1at} + y_{\text{stub}2} = (1 + j1.24) - j1.24 \Rightarrow y_2 = 1$  S/S.

- For the desired  $-j1.24$  S/S, the length of a short-circuit terminated ( $y_{SC} \rightarrow \infty$ ) stub 2 is  $\ell_2 = 0.358\lambda - 0.25\lambda = 0.108(40 \text{ cm}) \Rightarrow \underline{\ell_2 \approx 4.32 \text{ cm}}$ .

### Final Design

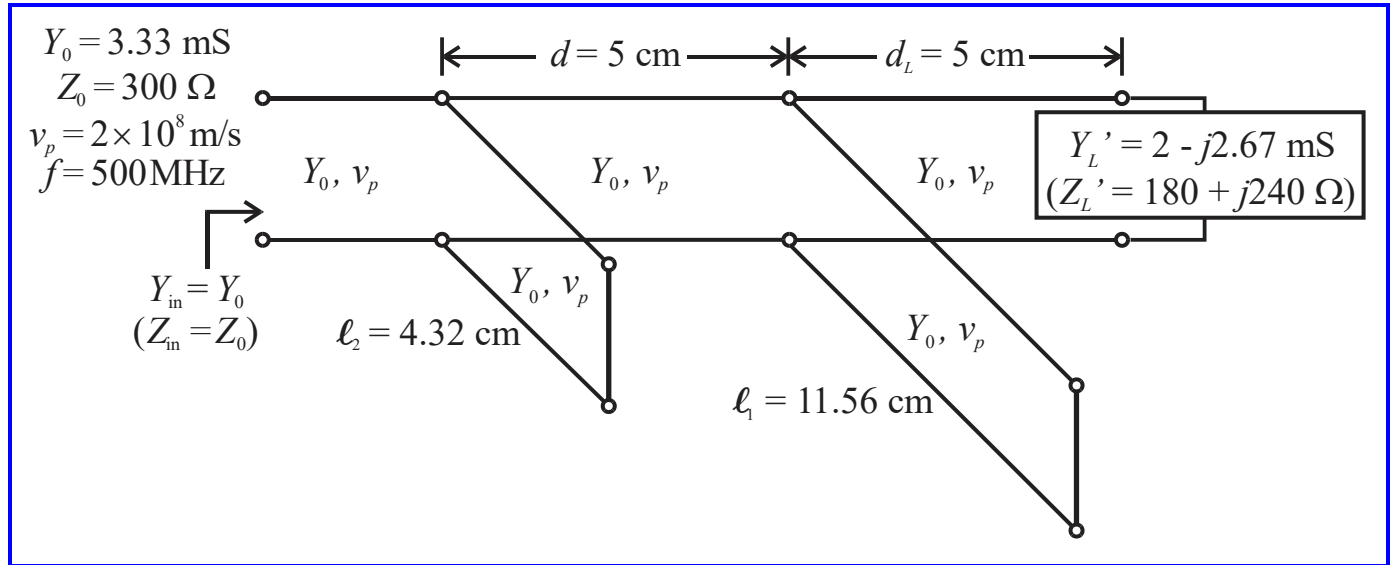

9) By definition the matched input impedance is  $\Rightarrow \underline{Z_{in,M} = Z_0 = 300 \Omega}$ .

10) Calculate the matched phasor input current and voltage as

$$\bar{I}_{in,M} = \frac{\bar{V}_g}{Z_g + Z_{in,M}} = \frac{16\angle 0^\circ}{300 + 300} \Rightarrow \underline{\bar{I}_{in,M} = 0.026\bar{6}\angle 0^\circ \text{ A}} \text{ and}$$

$$\bar{V}_{in,M} = \bar{V}_g \frac{Z_{in,M}}{Z_g + Z_{in,M}} = (16\angle 0^\circ) \frac{300}{300 + 300} \Rightarrow \underline{\bar{V}_{in,M} = 8\angle 0^\circ \text{ V}}.$$

For a lossless TL, the input power and load power are the same.

$$P_{L,M} = P_{in,M} = 0.5 \text{ Re}\{V_{in,M} I_{in,M}^*\} = 0.5 \text{ Re}\{8(0.0267)\} \Rightarrow \underline{P_{L,M} = 0.1067 \text{ W} = 106.7 \text{ mW}}.$$

This is 33.3% higher than the unmatched case!

