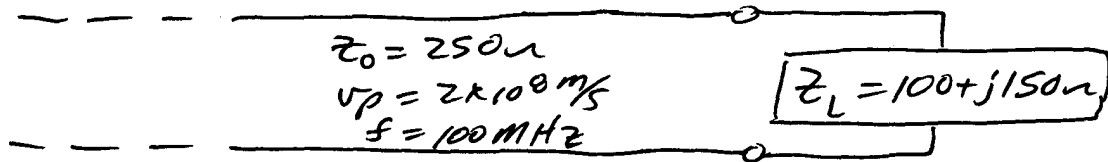


For a circuit operating at 100 MHz, design and sketch a series single-stub with open circuit termination tuning network for a load $Z_L = 100 + j150 \Omega$ connected to a lossless transmission line (250Ω , 2×10^8 m/s) using a Smith chart. Place the stub as close as possible to the load and make the stub as short as possible.



→ Calculate $y_L = \frac{Z_L}{Z_0} = \frac{100 + j150}{250} = 0.4 + j0.6$ y

→ Plot y_L on Smith Chart and draw $|r| = 0.56$ circle through y_L .

→ Move WTB on $|r| = 0.56$ circle to $y_{in} = 1 + j1.35$ y

$$d_1 = 0.172\lambda - 0.0945\lambda = \underline{\underline{0.0775\lambda}}$$


→ Need an open circuit stub w/ $y_{stub} = -j1.35$ y
Plot y_{stub} .

→ Move WTB from $y_{oc} \rightarrow \infty$ to y_{stub}

$$l_1 = 0.3518\lambda - 0.25\lambda = \underline{\underline{0.1018\lambda}}$$

→ Calculate $\lambda = \frac{v_p}{f} = \frac{2 \times 10^8}{100 \times 10^6} = 2$ m

Final Series OC stub Design

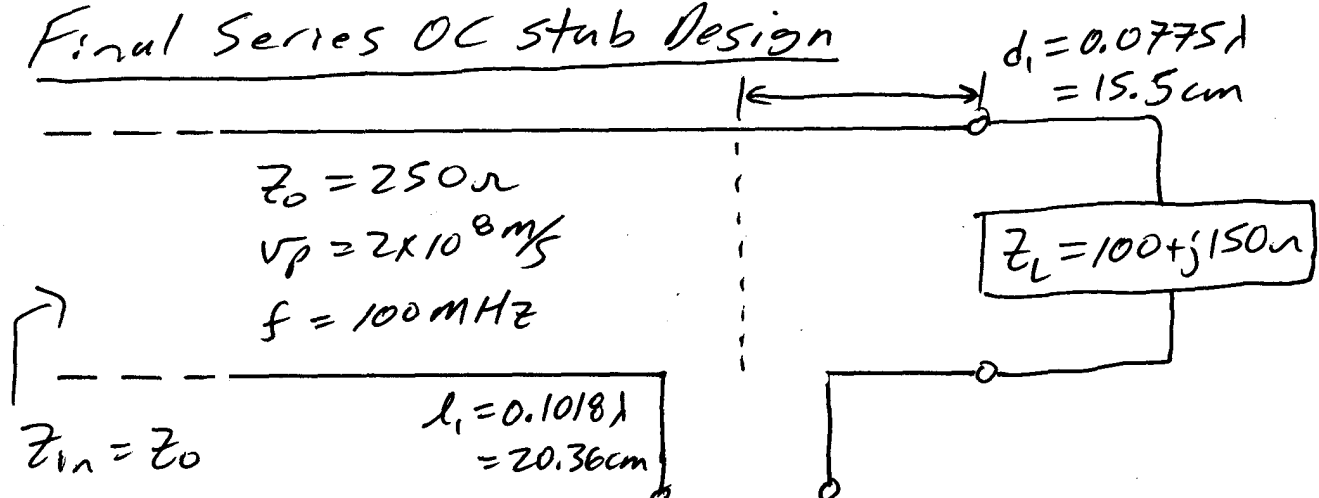

$$\begin{aligned} z_0 &= 250 \Omega \\ v_p &= 2 \times 10^8 \text{ m/s} \\ f &= 100 \text{ MHz} \end{aligned}$$
