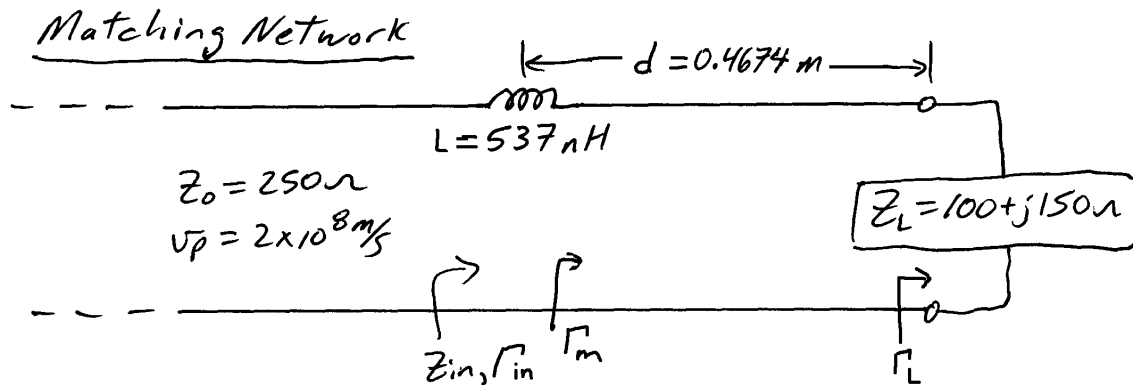


For problem 1), using the designed match, calculate the match-point impedance, inductor impedance, input impedance (at terminals of matching network), input reflection coefficient, and SWR at 95, 100, & 105 MHz. Tabulate results. Format: col. 1 frequency, col. 2 Z_m , col. 3 Z_{ind} , col. 4 Z_{in} , col. 4 Γ_{in} , & col. 5 SWR.

For a circuit operating at 100 MHz, design and sketch a single series inductor matching network for a load $Z_L = 100 + j150 \Omega$ connected to a lossless transmission line (250Ω , 2×10^8 m/s). Use Smith chart solution method.



Used MathCad (next page) for calculations of the equations below-

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \text{ (fixed value)}$$

$$\beta = \frac{\omega}{v_p} = \frac{2\pi f}{v_p} \text{ (changes w/ frequency)}$$

$$\Gamma_m = \Gamma_L e^{-j2\beta d} \Rightarrow Z_m = Z_0 \left(\frac{1 + \Gamma_m}{1 - \Gamma_m} \right)$$

$$Z_{ind} = j\omega L = j2\pi f L \Rightarrow Z_{in} = Z_{ind} + Z_m$$

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \Rightarrow SWR = \frac{1 + |\Gamma_{in}|}{1 - |\Gamma_{in}|}$$

f (MHz)	Z_m (Ω)	Z_{ind} (Ω)	Z_{in} (Ω)	Γ_{in} (Ω)	SWR
95	304.87-j366.31	j320.54	304.87-j45.77	0.1283 $\angle$ -35.1°	1.294
100	248.15-j334.16	j337.41	248.15+j3.24	0.0075 $\angle$ 119.3°	1.015
105	205.92-j301.2	j354.28	205.92+j53.08	0.1503 $\angle$ 123.1°	1.354

Given:

$$v_p := 2 \cdot 10^8 \text{ m/s} \quad Z_0 := 250 \quad \Omega \quad Z_L := 100 + j \cdot 150 \quad \Omega$$

$$d := 0.4674 \text{ m} \quad \underline{L} := 537 \cdot 10^{-9} \text{ H}$$

$$\Gamma_L := \frac{Z_L - Z_0}{Z_L + Z_0} \quad |\Gamma_L| = 0.5571 \quad \arg(\Gamma_L) \cdot \frac{180}{\pi} = 111.801 \quad \text{deg}$$

$$\text{SWR} := \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad \text{SWR} = 3.5155 \quad \text{no match}$$

$$f_{95} := 95 \cdot 10^6 \text{ MHz} \quad f_{100} := 100 \cdot 10^6 \text{ MHz} \quad f_{105} := 105 \cdot 10^6 \text{ MHz}$$

$$\beta_{95} := \frac{2 \cdot \pi \cdot f_{95}}{v_p} \quad \beta_{100} := \frac{2 \cdot \pi \cdot f_{100}}{v_p} \quad \beta_{105} := \frac{2 \cdot \pi \cdot f_{105}}{v_p}$$

$$\beta_{95} = 2.985 \text{ rad/m} \quad \beta_{100} = 3.142 \text{ rad/m} \quad \beta_{105} = 3.299 \text{ rad/m}$$

$$\Gamma_{m95} := \Gamma_L \cdot e^{-j \cdot 2 \cdot \beta_{95} \cdot d} \quad \Gamma_{m100} := \Gamma_L \cdot e^{-j \cdot 2 \cdot \beta_{100} \cdot d} \quad \Gamma_{m105} := \Gamma_L \cdot e^{-j \cdot 2 \cdot \beta_{105} \cdot d}$$

$$Z_{m95} := Z_0 \cdot \frac{(1 + \Gamma_{m95})}{(1 - \Gamma_{m95})} \quad Z_{m100} := Z_0 \cdot \frac{(1 + \Gamma_{m100})}{(1 - \Gamma_{m100})} \quad Z_{m105} := Z_0 \cdot \frac{(1 + \Gamma_{m105})}{(1 - \Gamma_{m105})}$$

$$\boxed{Z_{m95} = 304.87 - 366.31i} \quad \Omega \quad \boxed{Z_{m100} = 248.15 - 334.16i} \quad \Omega \quad \boxed{Z_{m105} = 205.92 - 301.2i} \quad \Omega$$

$$Z_{ind95} := j \cdot 2 \cdot \pi \cdot f_{95} \cdot L \quad Z_{ind100} := j \cdot 2 \cdot \pi \cdot f_{100} \cdot L \quad Z_{ind105} := j \cdot 2 \cdot \pi \cdot f_{105} \cdot L$$

$$\boxed{Z_{ind95} = 320.537i} \quad \Omega \quad \boxed{Z_{ind100} = 337.407i} \quad \Omega \quad \boxed{Z_{ind105} = 354.277i} \quad \Omega$$

$$Z_{in95} := Z_{m95} + Z_{ind95} \quad Z_{in100} := Z_{m100} + Z_{ind100} \quad Z_{in105} := Z_{m105} + Z_{ind105}$$

$$\boxed{Z_{in95} = 304.87 - 45.77i} \quad \Omega \quad \boxed{Z_{in100} = 248.15 + 3.24i} \quad \Omega \quad \boxed{Z_{in105} = 205.92 + 53.08i} \quad \Omega$$

$$\Gamma_{in95} := \frac{Z_{in95} - Z_0}{Z_{in95} + Z_0} \quad \Gamma_{in100} := \frac{Z_{in100} - Z_0}{Z_{in100} + Z_0} \quad \Gamma_{in105} := \frac{Z_{in105} - Z_0}{Z_{in105} + Z_0}$$

$$\boxed{|\Gamma_{in95}| = 0.1283} \quad \boxed{|\Gamma_{in100}| = 0.00749} \quad \boxed{|\Gamma_{in105}| = 0.15032}$$

$$\boxed{\arg(\Gamma_{in95}) \cdot \frac{180}{\pi} = -35.12} \quad \text{deg} \quad \boxed{\arg(\Gamma_{in100}) \cdot \frac{180}{\pi} = 119.28} \quad \text{deg} \quad \boxed{\arg(\Gamma_{in105}) \cdot \frac{180}{\pi} = 123.07} \quad \text{deg}$$

$$\text{SWR}_{95} := \frac{1 + |\Gamma_{in95}|}{1 - |\Gamma_{in95}|} \quad \text{SWR}_{100} := \frac{1 + |\Gamma_{in100}|}{1 - |\Gamma_{in100}|} \quad \text{SWR}_{105} := \frac{1 + |\Gamma_{in105}|}{1 - |\Gamma_{in105}|}$$

$$\boxed{\text{SWR}_{95} = 1.294} \quad \boxed{\text{SWR}_{100} = 1.015} \quad \boxed{\text{SWR}_{105} = 1.354}$$