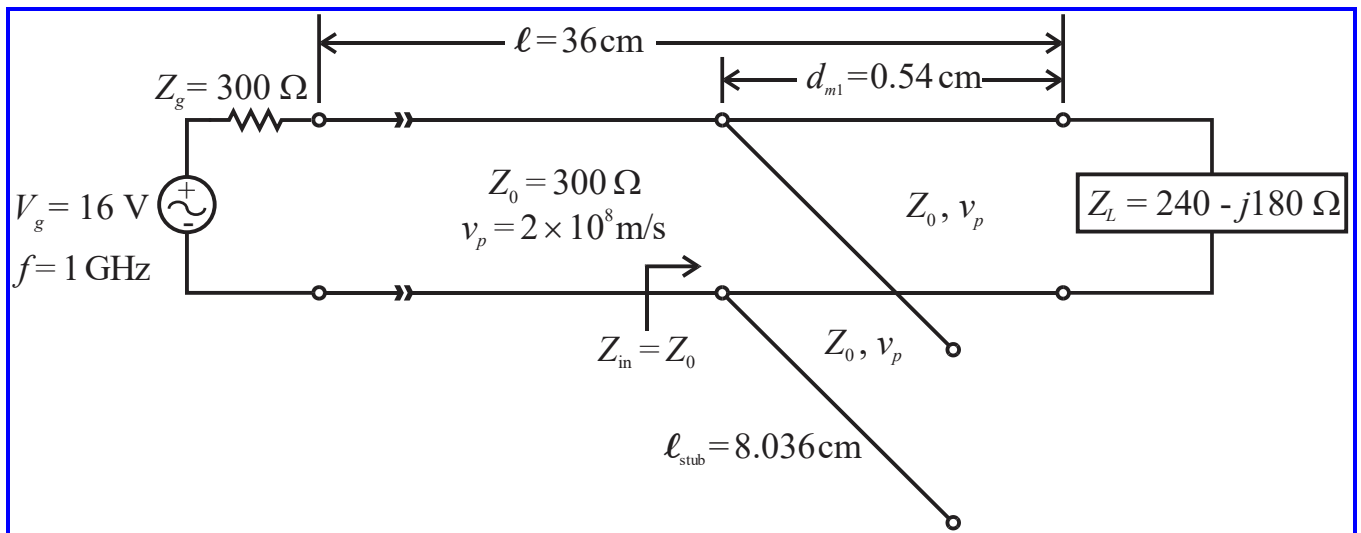


A lossless transmission line ( $300 \Omega$ ,  $2 \times 10^8$  m/s) of length 36 cm connects a load of  $240 - j180 \Omega$  to a matched 16 V generator operating at 1 GHz. Using a Smith chart, find the unmatched input impedance and load power. Then, design and sketch a shunt single-stub tuning network with an open circuit termination. Place the stub as close as possible to the load and make the stub as short as possible. Find the matched input impedance and load power.

- Calculate wavelength  $\lambda = v_p / f = 2 \times 10^8 / 1 \times 10^9 \Rightarrow \lambda = 0.2 \text{ m} = 20 \text{ cm}$ .
- Calculate the normalized load impedance  $z_L = Z_L / Z_0 = (240 - j180) / 300 \Rightarrow z_L = 0.8 - j0.6 \Omega/\Omega$ . Plot  $z_L$  on Smith chart.
- Use compass to draw a circle through  $z_L$ , centered on Smith chart. Use a straight edge to draw line through center of Smith chart &  $z_L$  to outer rings of Smith chart. Note  $|\Gamma| = 0.5$  and  $\text{SWR} = 3$ .
- Calculate  $\ell/\lambda = 36/20 = 1.8$ . Remove extraneous  $1.5\lambda$  to get  $\ell/\lambda = 0.3$ . Move  $0.3\lambda$  in the “WAVELENGTHS TOWARD GENERATOR” direction along the circle of constant  $|\Gamma|$  to  $z_{\text{in,NM}} = 1.24 + j0.75 \Omega/\Omega$ . The unmatched input impedance is then  $Z_{\text{in,NM}} = z_{\text{in,NM}} Z_0 = 1.24 + j0.75(300) \Rightarrow Z_{\text{in,NM}} = 372 + j225 \Omega$ .
- The unmatched input current is  $I_{0,\text{NM}} = V_g / (Z_g + Z_{\text{in,NM}}) = 16 \angle 0^\circ / (300 + 372 + j225) \Rightarrow I_{0,\text{NM}} = 0.02258 \angle -18.512^\circ \text{ A}$ . The unmatched input voltage is  $V_{0,\text{NM}} = I_{0,\text{NM}} (Z_{\text{in,NM}}) = (0.02258 \angle -18.512^\circ)(372 + j225) \Rightarrow V_{0,\text{NM}} = 9.816 \angle 12.656^\circ \text{ V}$ .
- The unmatched input power is  $P_{0,\text{NM}} = 0.5 \text{ Re}(V_{0,\text{NM}} I_{0,\text{NM}}^*) = 0.5 \text{ Re}\{(9.816 \angle 12.656^\circ)(0.02258 \angle 18.512^\circ)\} \Rightarrow P_{0,\text{NM}} = 0.094813 \text{ W} = 94.813 \text{ mW}$ .
- To match, begin by moving  $180^\circ$  around the circle of constant  $|\Gamma|$  from  $z_L$  point to  $y_L = 0.8 + j0.6 \text{ S/S}$ .
- Note the match points where the circle of constant  $|\Gamma| = 0.33$  intersects the circle of  $g = 1 \text{ S/S}$  at  $y_{m1} = 1 + j0.71 \text{ S/S}$  and  $y_{m2} = 1 - j0.71 \text{ S/S}$ . Choose  $y_{m1}$  as it is closest.
- Find distance in the “WAVELENGTHS TOWARD GENERATOR” direction from  $y_L$  to  $y_{m1}$  as  $d_{m1} = 0.152\lambda - 0.125\lambda \Rightarrow d_{m1} = 0.027\lambda = 0.54 \text{ cm}$ .

- To match, connect an open circuit stub with input admittance  $y_{\text{stub}} = -j0.71 \text{ S/S}$  at  $y_{M1}$  location.
- To find the stub length, plot  $y_{oc} \rightarrow \infty$  at 0 and go in the “WAVELENGTHS TOWARD GENERATOR” direction to the location of  $y_{\text{stub}} = -j0.71 \text{ S/S}$  at  $0.4018\lambda$   
 $\Rightarrow \ell_{\text{stub}} = 0.4018\lambda = 8.036 \text{ cm}.$



- The matched input impedance is  $Z_{\text{in},M} = Z_0 = 300 \Omega.$
- The matched input current is  $I_{0,M} = V_g / (Z_g + Z_{\text{in},M}) = 16 \angle 0^\circ / (300 + 300) \Rightarrow I_{0,M} = 0.02667 \angle 0^\circ \text{ A}.$  The matched input voltage is  $V_{0,M} = I_{0,M} (Z_{\text{in},M}) = (0.02667 \angle 0^\circ)(300) \Rightarrow V_{0,M} = 8 \angle 0^\circ \text{ V}.$
- The matched input power is  $P_{0,M} = 0.5 \text{ Re}(V_{0,M} I_{0,M}^*) = 0.5 \text{ Re}\{(8 \angle 0^\circ)(0.02667 \angle 0^\circ)\} \Rightarrow P_{0,M} = 0.10667 \text{ W} = 106.667 \text{ mW},$  an increase of 11.85 mW over the unmatched case.

