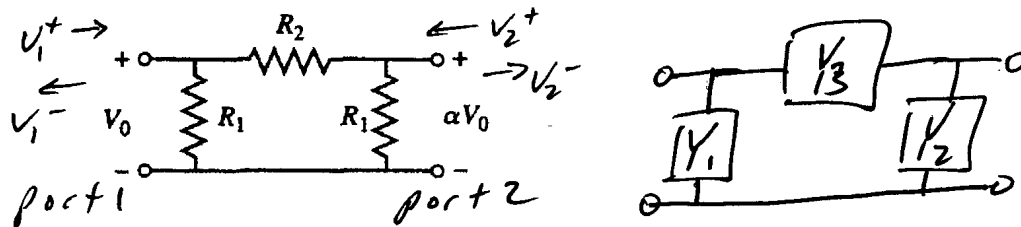


7.7 Consider the π resistive attenuator circuit shown below. If the input and output are matched to Z_0 , and the ratio of output voltage to input voltage is α , derive the design equations for R_1 and R_2 for each circuit. If $Z_0 = 50 \Omega$, compute R_1 and R_2 for 3, 10, and 20 dB attenuators of each type.



- Do π resistive attenuator only.

Per Table 4.1, the ABCD parameters for an admittance π -network are:

$$A = 1 + Y_2/Y_3 = 1 + Y_1/Y_2 = 1 + R_2/R_1$$

$$B = 1/Y_3 = 1/Y_2 = R_2$$

$$C = Y_1 + Y_2 + \frac{Y_1 Y_2}{Y_3} = \frac{1}{R_1} + \frac{1}{R_1} + \frac{Y_1(Y_2)}{Y_2} = \frac{2}{R_1} + \frac{R_2}{R_1^2}$$

$$D = 1 + Y_1/Y_3 = 1 + Y_1/Y_2 = 1 + R_2/R_1$$

For the input to be matched to $z_0 \Rightarrow S_{11} = 0$.

Per Table 4.2, $S_{11} = \frac{A + B/z_0 - C z_0 - D}{A + B/z_0 + C z_0 + D}$. The only

way $S_{11} = 0$ is if the numerator is zero:

$$(1 + \cancel{R_2/R_1}) + R_2/z_0 - \left(\frac{2}{R_1} + \frac{R_2}{R_1^2}\right) z_0 - (1 + \cancel{R_2/R_1}) = 0$$

$$\frac{R_2}{z_0} = \left(\frac{2}{R_1} + \frac{R_2}{R_1^2}\right) z_0 \quad (1)$$

$$\times z_0 R_1^2 \quad R_2 R_1^2 = 2 R_1 z_0^2 + R_2 z_0^2 \Rightarrow R_2 (R_1^2 - z_0^2) = 2 R_1 z_0^2$$

$$R_2 = \frac{2 R_1 z_0^2}{R_1^2 - z_0^2} = \frac{2 R_1 z_0^2}{(R_1 + z_0)(R_1 - z_0)} \quad (2)$$

$$\text{Per (4.41), } S_{12} = \frac{V_1^-}{V_2^+} \Big|_{V_1^+ = 0} \quad \& \quad S_{21} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0}$$

By symmetry, $S_{12} = S_{21} = \frac{\alpha V_0}{V_0} = \alpha$ since
 $V_2 = V_2^- = \alpha V_0$ when $V_2^+ = 0$

Per Table 4.2, $S_{21} = \frac{2}{A + B/Z_0 + C Z_0 + D} = \alpha$

$$\frac{2}{\alpha} = (1 + R_2/R_1) + \frac{R_2}{Z_0} + Z_0 \left(\frac{2}{R_1} + \frac{R_2}{R_1^2} \right) + (1 + R_2/R_1)$$

$$= 2 + \frac{2R_2}{R_1} + \frac{R_2}{Z_0} + \frac{R_2}{Z_0} \quad \textcircled{1}$$

$$\frac{1}{\alpha} = 1 + R_2/R_1 + R_2/Z_0 \xrightarrow{\times R_1 Z_0} \frac{R_1 Z_0}{\alpha} = R_1 Z_0 + R_2 Z_0 + R_2 R_1$$

$$R_1 Z_0 \left(\frac{1}{\alpha} - 1 \right) = R_2 (R_1 + Z_0) = \frac{2R_1 Z_0^2}{(R_1 + Z_0)(R_1 - Z_0)} \quad (R_1 \cancel{\times} Z_0)$$

②

$$\frac{1}{\alpha} - 1 = \frac{2Z_0}{R_1 - Z_0} \xrightarrow{\times \alpha (R_1 - Z_0)} (R_1 - Z_0)(1 - \alpha) = 2Z_0 \alpha$$

$$R_1 (1 - \alpha) = 2Z_0 \alpha + Z_0 (1 - \alpha) = Z_0 (1 + \alpha)$$

$$\underline{\underline{R_1 = Z_0 \frac{1 + \alpha}{1 - \alpha}}}$$

Substitute for R_1 in eq'n ②

$$R_2 = \frac{2 \left[Z_0 \frac{1 + \alpha}{1 - \alpha} \right] Z_0^2}{Z_0^2 \frac{(1 + \alpha)^2}{(1 - \alpha)^2} - Z_0^2} = \frac{2 Z_0 (1 + \alpha)}{\frac{(1 + \alpha)^2}{1 - \alpha} - (1 - \alpha)}$$

$$= \frac{2 Z_0 (1 + \alpha)(1 - \alpha)}{(1 + \alpha)^2 - (1 - \alpha)^2} = \frac{2 Z_0 (1 - \alpha^2)}{1 + 2\alpha + \alpha^2 - (1 - 2\alpha + \alpha^2)}$$

$$\underline{\underline{R_2 = Z_0 \frac{1 - \alpha^2}{2\alpha}}}$$

$$P_{e-}(2.52), I_L = -20 \log |T| = -20 \log \alpha$$

$$\hookrightarrow \alpha = 10^{-I_L/20}$$

$$\boxed{I_L = 3 \text{ dB}} \Rightarrow \alpha = 10^{-3/20} = 0.707946$$

$$R_1 = 50 \frac{1 + 0.70795}{1 - 0.70795} \Rightarrow \underline{\underline{R_1 = 292.4 \Omega}}$$

$$R_2 = 50 \frac{1 - 0.70795^2}{2(0.70795)} \Rightarrow \underline{\underline{R_2 = 17.6 \Omega}}$$

$$\boxed{I_L = 10 \text{ dB}} \Rightarrow \alpha = 10^{-10/20} = 0.3162278$$

$$R_1 = 50 \frac{1 + 0.31623}{1 - 0.31623} \Rightarrow \underline{\underline{R_1 = 96.25 \Omega}}$$

$$R_2 = 50 \frac{1 - 0.31623^2}{2(0.31623)} \Rightarrow \underline{\underline{R_2 = 71.15 \Omega}}$$

$$\boxed{I_L = 20 \text{ dB}} \Rightarrow \alpha = 10^{-20/20} = 0.1$$

$$R_1 = 50 \frac{1 + 0.1}{1 - 0.1} \Rightarrow \underline{\underline{R_1 = 61.11 \Omega}}$$

$$R_2 = 50 \frac{1 - 0.1^2}{2(0.1)} \Rightarrow \underline{\underline{R_2 = 247.5 \Omega}}$$