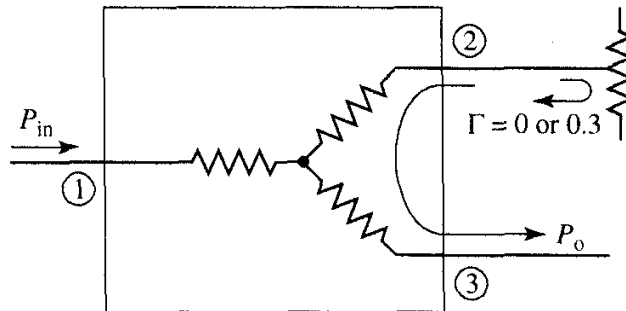



- 7.8 Design a three-port resistive divider for an equal power split and a $100\ \Omega$ system impedance. If port 3 is matched, calculate the change in output power at port 3 (in dB) when port 2 is connected first to a matched load, and then to a load having a mismatch of $\Gamma = 0.3$. See the figure below.



- Also, draw labeled sketch of design.


Per Fig. 7.7, the required resistance for an equal split resistive divider is
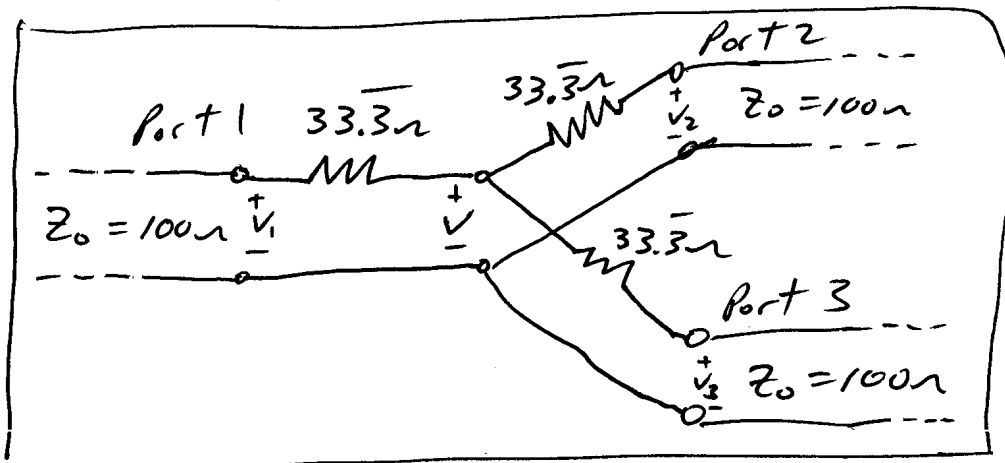
$$R = Z_0/3 = \frac{100}{3} \Rightarrow \underline{\underline{R = 33.\bar{3}\ \Omega}}$$



To calculate the change in power, we can use S-param. or circuit theory.

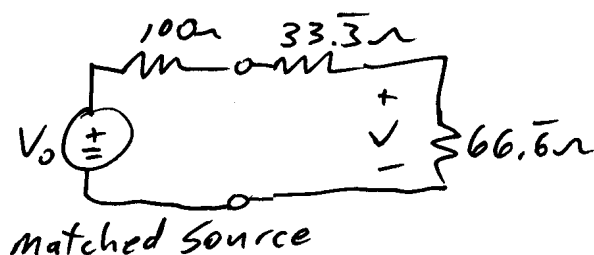
Ports 2 & 3 matched Input V_0 will 'see' a load of $33.\bar{3}\ \Omega$ in series with the parallel combination of $(33.\bar{3} + 100) \parallel (33.\bar{3} + 100) = 66.\bar{6}\ \Omega$



At the center junction,

$$V = \frac{V_0 \cdot 66.\bar{6}}{100 + 33.\bar{3} + 66.\bar{6}} = 0.\bar{33} V_0$$

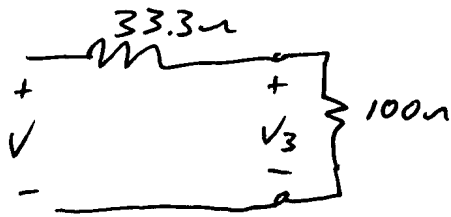Looking down to port 3, the voltage V 'sees' 33.3Ω in series w/ 100Ω . The voltage into port 3



$$V_3 = V \frac{100}{100 + 33.3} = 0.3 V_1 + \frac{100}{133.3}$$


$$= 0.25 V_0$$

$$P_{3, \text{mat}} = \frac{1}{2} \frac{|V_3|^2}{Z_0} = \frac{0.25^2 |V_0|^2}{200} = \frac{|V_0|^2}{3200}$$

Port 2 w/ $\Gamma = 0.3$ & Port 3 matched

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.3 = \frac{Z_L - 100}{Z_L + 100} \Rightarrow Z_L = \frac{130}{0.7} = 185.7143\Omega$$

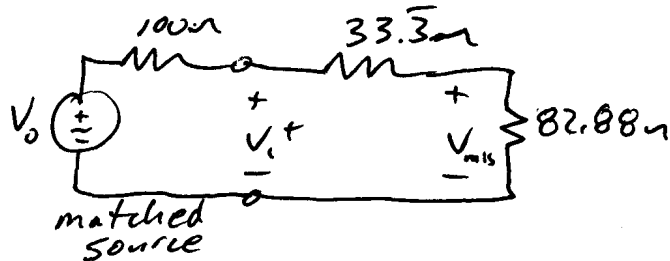Now, input V_0 will see a load of 33.3Ω in series with the parallel combination $(33.3 + 185.71) \parallel (33.3 + 100) = 82.883\Omega$



$$V_{\text{mis}} = \frac{V_0 \cdot 82.883}{100 + 33.3 + 82.883}$$

$$= 0.383 V_0$$

Looking down to port 3, the voltage V_{mis} 'sees' 33.3Ω in series w/ 100Ω . The voltage into port 3 is

$$V_3 = V_{\text{mis}} \frac{100}{100 + 33.3} = 0.383 V_0 \frac{100}{133.3} = 0.2875 V_0$$

$$\text{Now, } P_{3, \text{mis}} = \frac{1}{2} \frac{|V_3|^2}{Z_0} = \frac{0.2875^2 |V_0|^2}{200} = \frac{|V_0|^2}{2419.66}$$

$$\frac{P_{3, \text{mis}}}{P_{3, \text{mat}}} (\text{dB}) = 10 \log_{10} \left[\frac{\frac{|V_0|^2}{2419.66}}{\frac{|V_0|^2}{3200}} \right] = 10 \log_{10} \frac{3200}{2419.66} = \underline{\underline{1.214 \text{ dB}}}$$