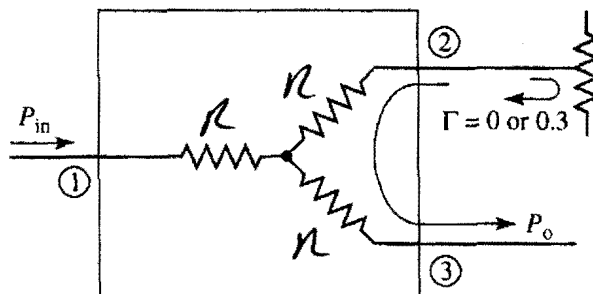



- 7.8 Design a three-port resistive divider for an equal power split and a $75\ \Omega$ system impedance. If port 3 is matched, calculate the change in output power at port 3 (in dB) when port 2 is connected first to a matched load, and then to a load having a mismatch of $\Gamma = 0.3$. See the figure below.




- Change to $75\ \Omega$ system impedance. Also, draw labeled sketch of design.

Per Figure 7.7, for an equal-split 3-port resistive power divider
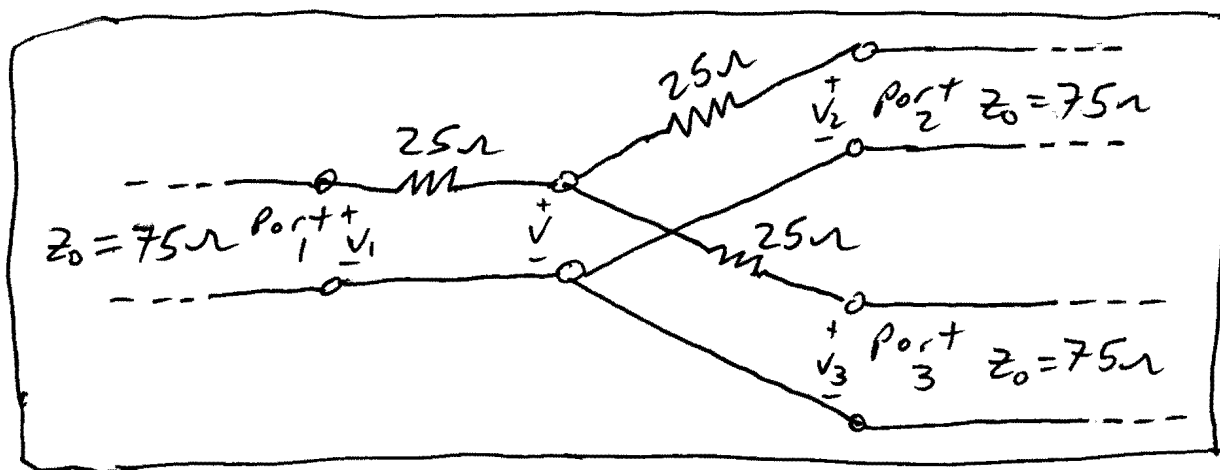
$$R = Z_0/3 = \frac{75}{3} \Rightarrow \underline{\underline{R = 25\ \Omega}}$$



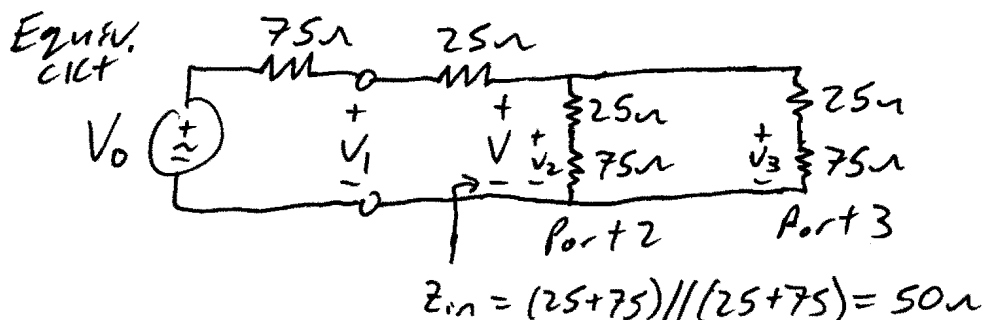First, find the power to Port 3 when both Ports 2 + 3 are terminated in matched loads ($75\ \Omega$) and Port 1 is driven by matched source.



By voltage division, $V = V_0 \frac{50}{75+25+50} = 0.3 V_0$

By voltage division, $V_3 = V \frac{75}{25+75} = 0.3 V_0 (3/4) = 0.25 V_0$

The power to Port 3 w/ Port 2 also matched is


$$P_{3,match} = \frac{1}{2} \frac{|V_3|^2}{Z_0} = \frac{0.25^2 |V_0|^2}{2(75)} \Rightarrow \underline{P_{3,mat} = 4.16 \times 10^{-4} |V_0|^2}$$

Next, find the power to Port 3 when it is matched, Port 2 has $\Gamma = 0.3$, and Port 1 is driven by a matched source.

Per (2.35), $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \Rightarrow 0.3 = \frac{Z_{L,2} - 75}{Z_{L,2} + 75}$

$$\hookrightarrow Z_{L,2} = \frac{75(1+0.3)}{1-0.3} = 139.2857 \Omega$$

Equiv. ckt

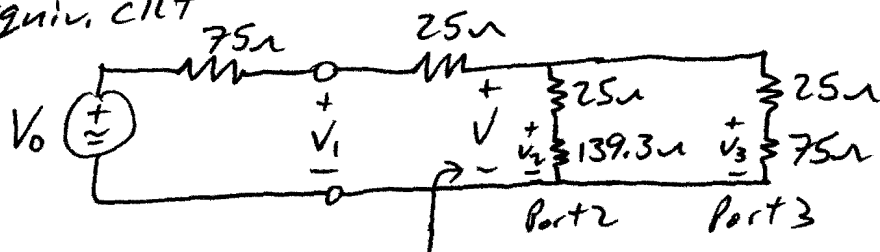

$$Z_{in} = (25 + 139.3) \parallel (25 + 75) = 62.162 \Omega$$

$$V = V_0 \frac{62.162}{75+25+62.162} = 0.383 V_0$$

$$V_3 = V \frac{75}{25+75} = 0.383 V_0 (0.75) = 0.2875 V_0$$

$$P_{3,mis} = \frac{1}{2} \frac{0.2875^2 |V_0|^2}{75} = \underline{5.510416 \times 10^{-4} |V_0|^2}$$

$$\frac{P_{3,mis}}{P_{3,mat}} = \frac{5.510416}{4.16} \Rightarrow \boxed{\frac{P_{3,mis}}{P_{3,mat}} = 1.3225 = 1.214 \text{ dB (increase)}}$$