

7.22 Design a single-section coupled line coupler with a coupling of 19.1 dB, a system impedance of 60Ω , and a center frequency of 8 GHz. If the coupler is to be made in stripline (edge-coupled), with $\epsilon_r = 2.2$ and $b = 0.32$ cm, find the necessary strip widths and separation.

- Also, draw labeled sketch of design.

$$C(\text{dB}) = -20 \log_{10} C \rightarrow C = 10^{\frac{-19.1}{20}} = 0.11092$$

Per (7.87a) and (7.87b), the even and odd mode characteristic impedances are

$$Z_{oe} = Z_0 \sqrt{\frac{1+C}{1-C}} = 60 \sqrt{\frac{1+0.1109}{1-0.1109}} = 67.06889 \Omega$$

$$Z_{oo} = Z_0 \sqrt{\frac{1-C}{1+C}} = 60 \sqrt{\frac{1-0.1109}{1+0.1109}} = 53.67615 \Omega$$

For stripline (Fig 7.29), we need

$$\left. \begin{aligned} \sqrt{\epsilon_r} Z_{oe} &= \sqrt{2.2} \cdot 67.069 = 99.4792 \Omega \\ \sqrt{\epsilon_r} Z_{oo} &= \sqrt{2.2} \cdot 53.676 = 79.6146 \Omega \end{aligned} \right\} \text{Plot on Fig 7.29}$$

From Fig 7.29, $S/b = 0.37$ & $\frac{W}{b} = 0.592$
(next page)

Using $b = 0.32 \text{ cm} = 3.2 \text{ mm}$,

$$\underline{S = 0.37(3.2) = 1.18 \text{ mm}} \quad \& \quad \underline{W = 0.592(3.2) = 1.89 \text{ mm}}$$

$$V_p = \frac{c}{\sqrt{\epsilon_r}} = \frac{2.9979 \times 10^8}{\sqrt{2.2}} = 2.021184 \times 10^8 \text{ m/s}$$

$$\lambda = \frac{V_p}{f} = \frac{2.02118 \times 10^8}{8 \times 10^9} = 25.2648 \text{ mm}$$

$$\hookrightarrow \underline{\underline{\lambda/4 = 6.316 \text{ mm}}}$$

Bonus! From MWI, $\underline{W_{60\Omega} = 3.9455 \text{ mm}}$.

Drawing on next page.


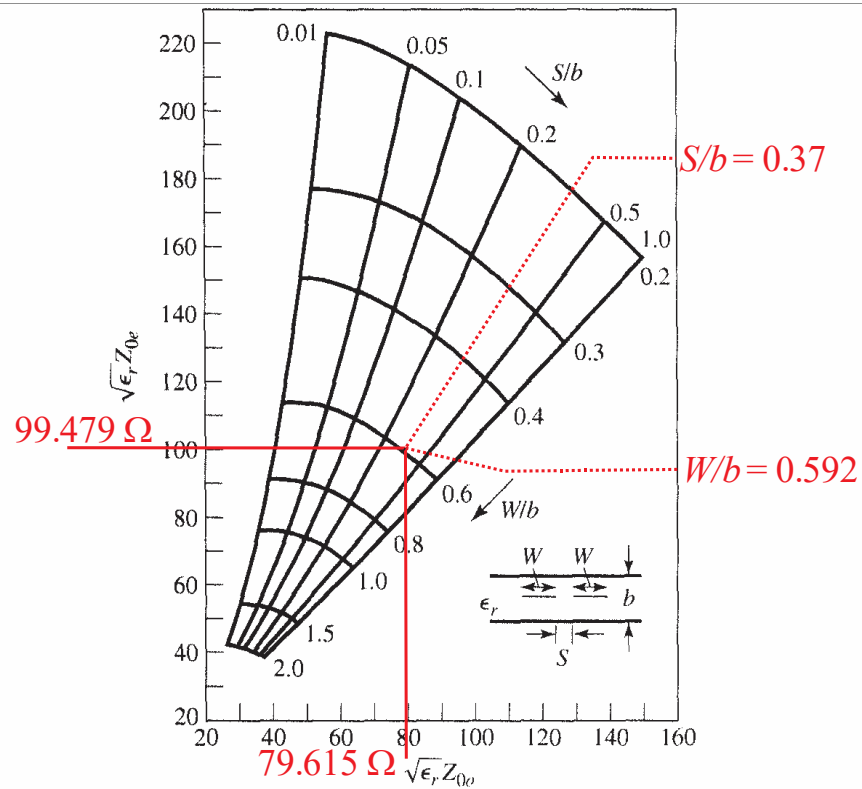


FIGURE 7.29 Normalized even- and odd-mode characteristic impedance design data for symmetric edge-coupled striplines.

Side View

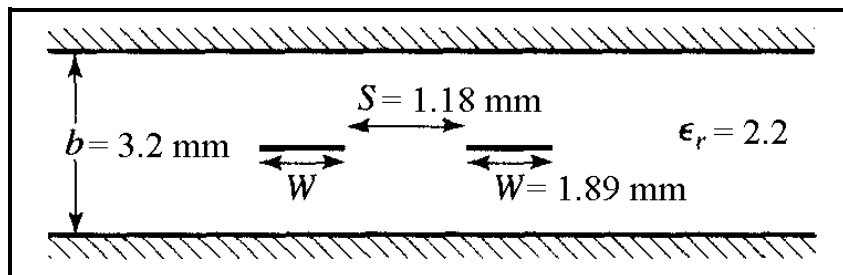

Top View

