

A 20 dB coupler using edge-coupled striplines is desired at 4 GHz in a $50\ \Omega$ system with a ground plane separation of 2.54 mm and $\epsilon_r = 2.2$. a) Find the unitless coupling coefficient C and percentage of power coupled. b) Find the required even-mode Z_{0e} and odd-mode Z_{0o} characteristic impedances. c) Using the graph of Figure 7.29, find the land/trace widths W and separation S . d) Find W_{50} , v_p and $L = \lambda/4$ for $Z_0 = 50\ \Omega$. e) Draw a fully-labeled top view sketch of the striplines for the coupler.

a) Per (7.20a), $C = 10^{-\text{CdB}/20} = 10^{-20/20}$

$\Rightarrow \underline{C = 0.1}$

Per notes, % power = $C^2(100\%) = 0.1^2(100\%)$

$\Rightarrow \underline{\% \text{ power} = 1\ \%}$

b) Per (7.87a), $Z_{0e} = Z_0 \sqrt{\frac{1+C}{1-C}} = 50 \sqrt{\frac{1+0.1}{1-0.1}}$


$\Rightarrow \underline{Z_{0e} = 55.277\ \Omega}$

Per (7.87a), $Z_{0o} = Z_0 \sqrt{\frac{1-C}{1+C}} = 50 \sqrt{\frac{1-0.1}{1+0.1}}$

$\Rightarrow \underline{Z_{0o} = 45.227\ \Omega}$

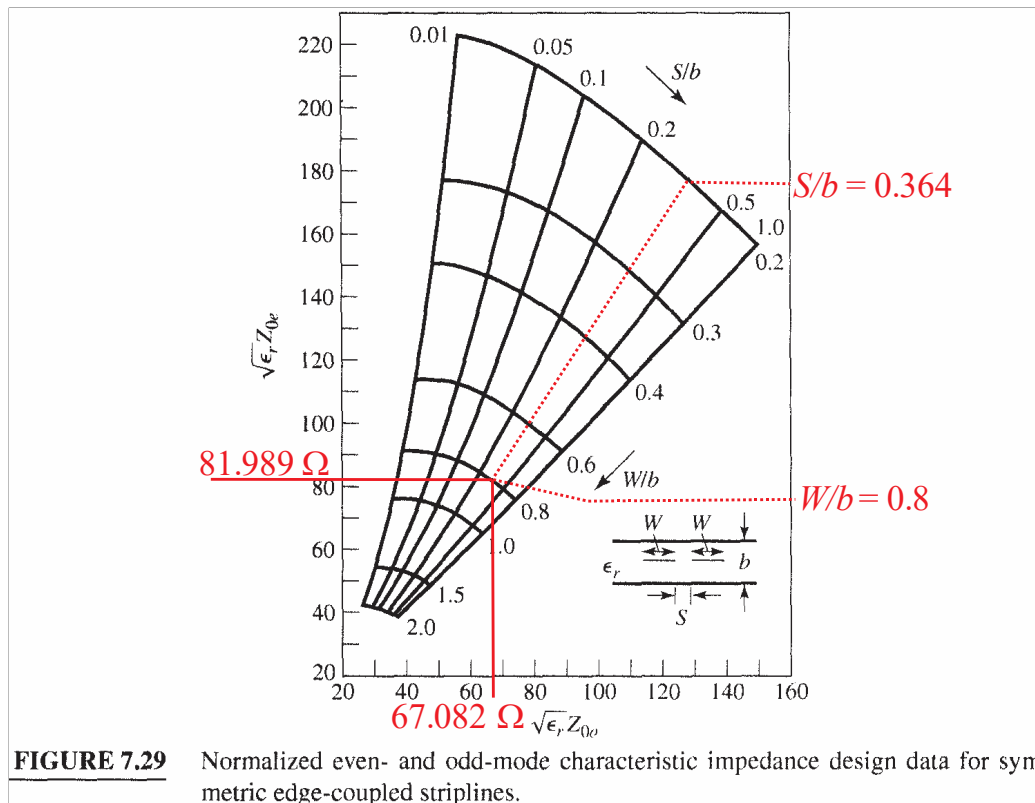c) To use graph/Fig. 7.29, we need

$\sqrt{\epsilon_r} Z_{0e} = \sqrt{2.2}(55.277) = 81.989\ \Omega$ and $\sqrt{\epsilon_r} Z_{0o} = \sqrt{2.2}(45.227) = 67.082\ \Omega$.



$S = S/b (b) = 0.364 (2.54)$

$\Rightarrow \underline{S = 0.925\ \text{mm}}$

$W = W/b (b) = 0.8 (2.54)$

$\Rightarrow \underline{W = 2.032\ \text{mm}}$

- d) To find W_{50} , we will use (3.180a) & (3.180b). Since $\sqrt{\epsilon_r} Z_0 = \sqrt{2.2} (50) = 74.162 \Omega < 120 \Omega$, we use the top equation -

$$\frac{W}{b} = x = \frac{30\pi}{\sqrt{\epsilon_r} Z_0} - 0.441 = \frac{30\pi}{\sqrt{2.2} (50)} - 0.441 = 0.8298368.$$

The land width is $W_{50} = 0.8298(2.54) \Rightarrow \underline{W_{50} = 2.108 \text{ mm.}}$

$$(3.176) v_p = c / \sqrt{\epsilon_r} = 2.9979 \times 10^8 / \sqrt{2.2} \Rightarrow \underline{v_p = 2.0212 \times 10^8 \text{ m/s.}}$$

$$L = \lambda/4 = v_p / f / 4 = 2.0212 \times 10^8 / 4 \times 10^9 / 4 \Rightarrow \underline{L = 0.01263 \text{ m} = 12.63 \text{ mm.}}$$

e)

