- 8.6 Solve the design equations in Section 8.3 for the elements of an N = 2 equal-ripple filter if the ripple specification is 1.0 dB.
- > Per (8.54), $P_{LR} = 1 + k^2 T_N^2 \left(\frac{\omega}{\omega_c}\right)$ for a Chebyshev low-pass filter.
- > Chebyshev polynomials are equal to 1 when their argument is 1, i.e., $T_N^2(1) = 1$ at $\omega = \omega_c$.

> Therefore,
$$P_{LR}(\omega_c) = 1 + k^2 T_N^2 \left(\frac{\omega_c}{\omega_c}\right) = 1 + k^2$$

- ≻ Here, we desire $P_{LR}(\omega_c) = 1 + k^2 = 1 \text{ dB} = 10^{1/10} = 1.2589254 \implies k^2 = 0.2589254.$
- > Solving we get $k = \pm 0.50884714 \implies \underline{k_{\text{pos}} = 0.50884714} \& \underline{k_{\text{neg}} = -0.50884714}$.
- > For our prototype second order low-pass filter, we let $R_s = 1$ and assume $\omega_c = 1$ rad/s.



> Now (8.54) becomes (8.61) $P_{LR} = 1 + k^2 T_N^2(\omega)$.

- > For N = 2, per (5.56b) $T_2(x) = 2x^2 1$, so $T_2^2(\omega) = (2\omega^2 1)^2$.
- > Equating the P_{LR} equation (8.60) with (8.61) yields (8.62)

$$P_{LR} = 1 + k^{2} (2\omega^{2} - 1)^{2} = 1 + k^{2} (4\omega^{4} - 4\omega^{2} + 1)$$
$$= 1 + \frac{1}{4R} \Big[(1 - R)^{2} + (R^{2}C^{2} + L^{2} - 2LCR^{2})\omega^{2} + L^{2}C^{2}R^{2}\omega^{4} \Big]$$

> Letting $\omega = 0$, we get $1 + k^2 = 1 + \frac{1}{4R} \left[(1 - R)^2 \right] \implies k^2 = \frac{(1 - R)^2}{4R}$.

After some algebra & using the quadratic formula, we get (8.63) $R = 1 + 2k^2 \pm 2k\sqrt{1+k^2}$.

➢ For this case, $R = 1 + 2(0.258925) \pm 2(\pm 0.508847) \sqrt{1.258925}$ which has two possible solutions ⇒ <u>R_{big} = 2.65972256</u> & <u>R_{small} = 0.375979</u>.

> Equating the ω^4 coefficients of (8.62) gives $4k^2 = \frac{L^2 C^2 R^2}{4R} \Rightarrow L^2 = \frac{4^2 k^2 R}{C^2 R^2} = \frac{16k^2}{C^2 R}$.

- Solving for the inductance, $L = \frac{\pm 4k}{C\sqrt{R}}$ which implies $L_{kneg} = \frac{-4k_{neg}}{C\sqrt{R}}$ or $L_{kpos} = \frac{4k_{pos}}{C\sqrt{R}}$ are the realizable solutions where L > 0.
- > Equating the ω^2 coefficients of (8.62) gives

$$-4k^{2} = \frac{1}{4R}(R^{2}C^{2} + L^{2} - 2LCR^{2})$$
$$-16k^{2}R = R^{2}C^{2} + \frac{16k^{2}}{C^{2}R} - 2LCR^{2}$$
$$16k^{2}RC^{2} + R^{2}C^{4} + \frac{16k^{2}}{R} - 2LR^{2}C^{3} = 0$$

 \triangleright If L_{kneg} is substituted in, we get a polynomial in terms of C.

$$16k^{2}RC^{2} + R^{2}C^{4} + \frac{16k^{2}}{R} - 2\left(\frac{-4k_{neg}}{C\sqrt{R}}\right)R^{2}C^{3} = 0$$
$$R^{2}C^{4} + \left(16k^{2}R + \frac{8k_{neg}R^{2}}{\sqrt{R}}\right)C^{2} + \frac{16k^{2}}{R} = 0.$$

> If L_{kpos} is substituted in, we get another polynomial in terms of C.

$$16k^{2}RC^{2} + R^{2}C^{4} + \frac{16k^{2}}{R} - 2\left(\frac{4k_{pos}}{C\sqrt{R}}\right)R^{2}C^{3} = 0$$
$$R^{2}C^{4} + \left(16k^{2}R - \frac{8k_{pos}R^{2}}{\sqrt{R}}\right)C^{2} + \frac{16k^{2}}{R} = 0.$$

- MathCAD was used to solve these polynomials for C to determine which combination(s) of R_{big} , R_{small} , k_{pos} , and k_{neg} lead to realizable values of L & C.
- ➤ As shown, only the R_{big} & k_{new} or R_{big} & k_{pos} combinations work and yield the same solutions. The 2nd-order prototype Chebyshev low-pass filter w/ a ripple of 1 dB is shown below. In terms of immittances: g₀ =1, g₁ = 1.822, g₂ = 0.685, and g₃ = 2.6597.



Case 2
$$k_{neg}$$
 and R_{small} - **NO**, **C** & **L** are complex

$$\underbrace{\operatorname{Construct}}_{\operatorname{Construct}} \operatorname{w_{neg} und} \operatorname{Rsmall}^{2} \operatorname{Rsmall}^{2} \\ 0 \\ 16 \cdot \operatorname{ksqrd} \cdot \operatorname{Rsmall} + \frac{8 \cdot \operatorname{kneg} \cdot \operatorname{Rsmall}^{2}}{\sqrt{\operatorname{Rsmall}}} \\ 0 \\ \frac{16 \cdot \operatorname{ksqrd}}{\operatorname{Rsmall}} \\ \int_{\operatorname{Construct}} \operatorname{Rsmall}^{2} \cdot \operatorname{C}^{4} + \left(16 \cdot \operatorname{ksqrd} \cdot \operatorname{Rsmall} + \frac{8 \cdot \operatorname{kneg} \cdot \operatorname{Rsmall}^{2}}{\sqrt{\operatorname{Rsmall}}} \right) \cdot \operatorname{C}^{2} + \frac{16 \cdot \operatorname{ksqrd}}{\operatorname{Rsmall}} \\ \int_{\operatorname{Construct}} \operatorname{Construct}_{2} \cdot \operatorname{C}^{4} + \left(16 \cdot \operatorname{ksqrd} \cdot \operatorname{Rsmall} + \frac{8 \cdot \operatorname{kneg} \cdot \operatorname{Rsmall}^{2}}{\sqrt{\operatorname{Rsmall}}} \right) \cdot \operatorname{C}^{2} + \frac{16 \cdot \operatorname{ksqrd}}{\operatorname{Rsmall}} \\ \int_{\operatorname{Construct}} \operatorname{Construct}_{2} \cdot \operatorname{Construct}_{2} \cdot \operatorname{Construct}_{2} \cdot \operatorname{Construct}_{2} \cdot \operatorname{Construct}_{2} \cdot \operatorname{Rsmall}_{2} \\ \operatorname{Rsmall}_{2} \cdot \operatorname{Rsmall}_{2} \cdot \operatorname{C}^{2} = \operatorname{root}(\operatorname{f}(\operatorname{C}), \operatorname{C}) \\ \operatorname{L2} := \frac{-4 \cdot \operatorname{kneg}}{\operatorname{C2} \cdot \sqrt{\operatorname{Rsmall}}} \\ \operatorname{R2} := \operatorname{Rsmall}_{2} \cdot \operatorname{R2} := \operatorname{Rsmall}_{2} \cdot \operatorname{R2} := \operatorname{Rsmall}_{2} \cdot \operatorname{R2} := \operatorname{Rsmall}_{2} \cdot \operatorname{R2} := \operatorname{Rsmall}_{2} \\ \operatorname{R3} = 1 \quad \operatorname{C2} = -1.822 - 2.347i \quad \operatorname{L2} = -0.685 + 0.882i \quad \operatorname{R2} = 0.375979 \quad \operatorname{R2}_{2} = 0.375979} \\ \end{array}$$

<u>Case 3</u> k_{pos} and R_{big} - C & L are real & positive and same values as Case 1!

$$\operatorname{vcase3} := \begin{pmatrix} \operatorname{Rbig}^{2} \\ 0 \\ 16 \cdot \operatorname{ksqrd} \cdot \operatorname{Rbig} - \frac{8 \cdot \operatorname{kpos} \cdot \operatorname{Rbig}^{2}}{\sqrt{\operatorname{Rbig}}} \\ 0 \\ \frac{16 \cdot \operatorname{ksqrd}}{\operatorname{Rbig}} \end{pmatrix} \qquad \operatorname{vcase3} = \begin{pmatrix} 7.0741 \\ 0 \\ -6.6389 \\ 0 \\ 1.5576 \end{pmatrix}$$

$$f_{\mathsf{s}}(\mathsf{C}) := \operatorname{Rbig}^{2} \cdot \mathsf{C}^{4} + \left(16 \cdot \operatorname{ksqrd} \cdot \operatorname{Rbig} - \frac{8 \cdot \operatorname{kpos} \cdot \operatorname{Rbig}^{2}}{\sqrt{\operatorname{Rbig}}} \right) \cdot \mathsf{C}^{2} + \frac{16 \cdot \operatorname{ksqrd}}{\operatorname{Rbig}}$$

$$f_{\mathsf{s}}(\mathsf{C}) := \operatorname{Rbig}^{2} \cdot \mathsf{C}^{4} + \left(16 \cdot \operatorname{ksqrd} \cdot \operatorname{Rbig} - \frac{8 \cdot \operatorname{kpos} \cdot \operatorname{Rbig}^{2}}{\sqrt{\operatorname{Rbig}}} \right) \cdot \mathsf{C}^{2} + \frac{16 \cdot \operatorname{ksqrd}}{\operatorname{Rbig}}$$

$$g_{\mathsf{s}}(\mathsf{C}) := 0.5 \qquad \operatorname{C3} := \operatorname{root}(\mathsf{f}(\mathsf{C}), \mathsf{C}) \qquad \operatorname{L3} := \frac{4 \cdot \operatorname{kpos}}{\operatorname{C3} \cdot \sqrt{\operatorname{Rbig}}} \qquad \operatorname{R3} := \operatorname{Rbig}$$

$$\overline{\operatorname{Rs}} := 1 \qquad \operatorname{C3} = 0.684997 \qquad \operatorname{L3} = 1.821967 \qquad \operatorname{R3} = 2.659723 \qquad \operatorname{R3} = 2.659$$

<u>Case 4</u> k_{pos} and R_{small} - NO, C & L are complex

$$\operatorname{vcase4} := \begin{pmatrix} \operatorname{Rsmall}^{2} \\ 0 \\ 16 \cdot \operatorname{ksqrd} \cdot \operatorname{Rsmall} - \frac{8 \cdot \operatorname{kpos} \cdot \operatorname{Rsmall}^{2}}{\sqrt{\operatorname{Rsmall}}} \\ 0 \\ \frac{16 \cdot \operatorname{ksqrd}}{\operatorname{Rsmall}} \end{pmatrix} \qquad \operatorname{vcase4} = \begin{pmatrix} 0.1414 \\ 0 \\ 0.6191 \\ 0 \\ 11.0187 \end{pmatrix}$$
$$\operatorname{f}(C) := \operatorname{Rsmall}^{2} \cdot \operatorname{C}^{4} + \left(16 \cdot \operatorname{ksqrd} \cdot \operatorname{Rsmall} - \frac{8 \cdot \operatorname{kpos} \cdot \operatorname{Rsmall}^{2}}{\sqrt{\operatorname{Rsmall}}} \right) \cdot \operatorname{C}^{2} + \frac{16 \cdot \operatorname{ksqrd}}{\operatorname{Rsmall}}$$
$$\operatorname{c}_{\operatorname{small}} := 0.5 \quad \operatorname{C4} := \operatorname{root}(\operatorname{f}(C), \operatorname{C}) \qquad \operatorname{L4} := \frac{4 \cdot \operatorname{kpos}}{\operatorname{C4} \cdot \sqrt{\operatorname{Rsmall}}} \qquad \operatorname{R4} := \operatorname{Rsmall}$$
$$\operatorname{R5} = 1 \quad \operatorname{C4} = -1.822 - 2.347i \quad \operatorname{L4} = -0.685 + 0.882i \quad \operatorname{R4} = 0.375979}$$