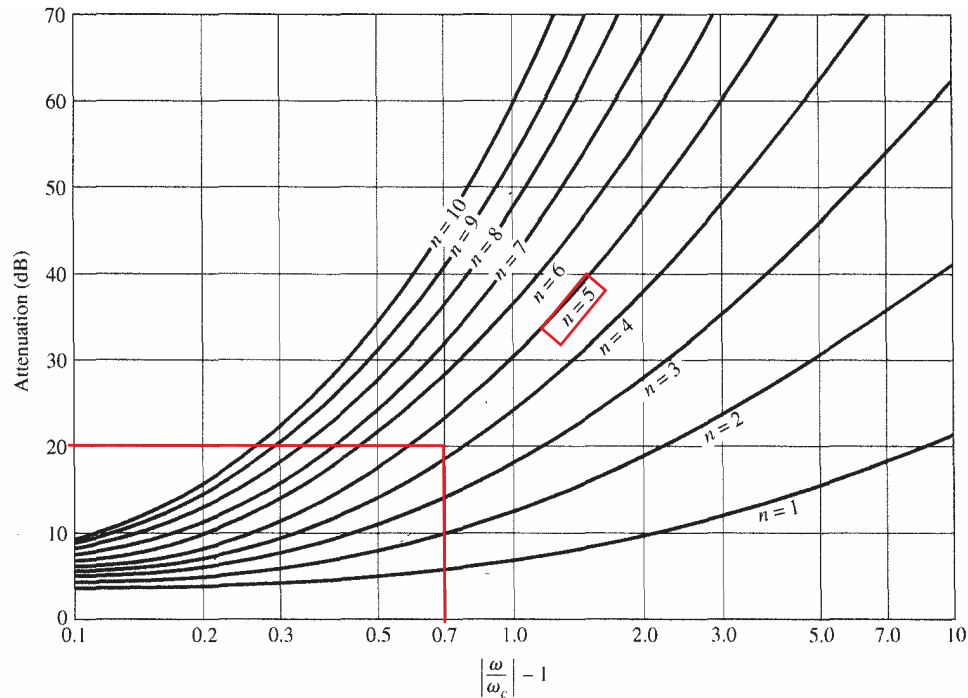


**8.7** Design a low-pass, maximally flat lumped-element filter having a passband of 0–2 GHz, and an attenuation of at least 20 dB at 3.4 GHz. The characteristic impedance is 50  $\Omega$ . Use CAD to plot the insertion loss versus frequency.

- Also, draw labeled sketch of design. CAD- Use MathCad, Matlab, ... to plot insertion loss versus frequency. **Normalize passband to 0 dB.**

➤ Calculate  $|\omega/\omega_c| - 1 = |3.4/2| - 1 = 0.7$ . From Figure 8.26, we see that a LP filter of order  $N=5$  is needed to meet the 20 dB attenuation specification.



**FIGURE 8.26** Attenuation versus normalized frequency for maximally flat filter prototypes. Adapted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

➤ From Table 8.3, we get the immittances:  $g_1 = g_5 = 0.618$ ,  $g_2 = g_4 = 1.618$ ,  $g_3 = 2$ , and  $g_6 = 1$  (matched).

**TABLE 8.3** Element Values for Maximally Flat Low-Pass Filter Prototypes ( $g_0 = 1$ ,  $\omega_c = 1$ ,  $N = 1$  to 10)

$N$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

- For the filter architecture of Fig 8.25a, we get the necessary scaled shunt capacitances and series inductances using the immittances and equations (8.64d) (8.67a), and (8.67b):

$$g_1 = g_5 = 0.618 \Rightarrow C'_1 = C'_5 = \frac{C_k}{R_0 \omega_c} = \frac{g_1}{R_0 \omega_c} = \frac{0.618}{50(2\pi)2 \times 10^9} \Rightarrow \underline{C'_1 = C'_5 = 0.9836 \text{ pF}}$$


$$g_2 = g_4 = 1.618 \Rightarrow L'_2 = L'_4 = \frac{R_0 L_k}{\omega_c} = \frac{R_0 g_2}{\omega_c} = \frac{50(1.618)}{(2\pi)2 \times 10^9} \Rightarrow \underline{L'_2 = L'_4 = 6.4378 \text{ nH}}$$

$$g_3 = 2 \Rightarrow C'_3 = \frac{C_3}{R_0 \omega_c} = \frac{g_3}{R_0 \omega_c} = \frac{2}{50(2\pi)2 \times 10^9} \Rightarrow \underline{C'_3 = 3.1831 \text{ pF}},$$

$$\text{and, per (8.64d), } g_6 = 1 \Rightarrow R'_L = R_0 R_L = R_0 g_6 = 50(1) \Rightarrow \underline{R'_L = 50 \Omega}.$$

- Further, the source resistance per (8.64c) is:  $R'_S = R_0 \Rightarrow \underline{R'_S = 50 \Omega}$ .

- The resulting LP filter circuit is:

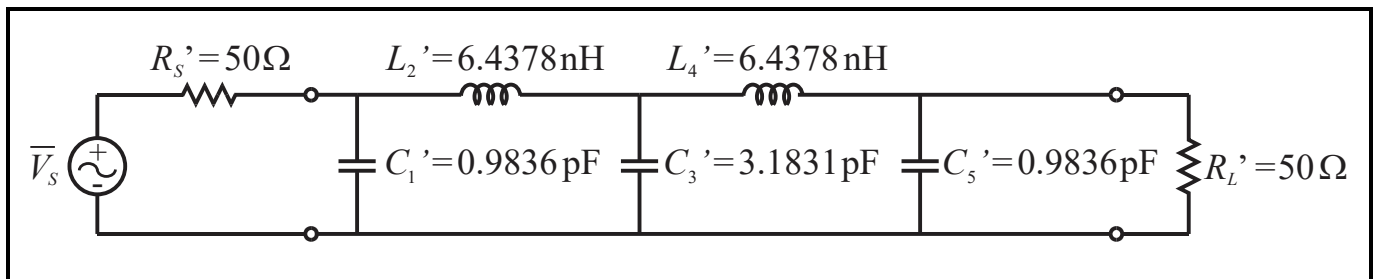

- MathCad was used to calculate the filter response as shown on the following page.
- Note that the insertion loss is less than -20 dB at 3.4 GHz (blue diamond).

### Define constants

$$VS := 1 \quad V \quad RS := 50 \quad \Omega \quad RL := 50 \quad \Omega \quad fc := 2 \cdot 10^9 \quad \text{Hz}$$

$$C1 := 0.9836 \cdot 10^{-12} \quad F \quad C5 := C1 \quad L2 := 6.4378 \cdot 10^{-9} \quad H \quad L4 := L2$$

$$C3 := 3.1831 \cdot 10^{-12} \quad F$$

Parallel impedance of RL & C5

$$Z1(f) := \left( \frac{1}{RL} + j \cdot 2 \cdot \pi \cdot f \cdot C5 \right)^{-1}$$

Series impedance of L4 & Z1

$$Z2(f) := j \cdot 2 \cdot \pi \cdot f \cdot L4 + Z1(f)$$

Parallel impedance of Z2 & C3

$$Z3(f) := \left( \frac{1}{Z2(f)} + j \cdot 2 \cdot \pi \cdot f \cdot C3 \right)^{-1}$$

Series impedance of L2 &amp; Z3

$$Z4(f) := j \cdot 2 \cdot \pi \cdot f \cdot L2 + Z3(f)$$

Input impedance of LP filter w/ load

$$Zin(f) := \left( \frac{1}{Z4(f)} + j \cdot 2 \cdot \pi \cdot f \cdot C1 \right)^{-1}$$

Voltage division to get Vld

$$Vld(f) := VS \cdot \frac{Zin(f)}{RS + Zin(f)} \cdot \frac{Z3(f)}{Z4(f)} \cdot \frac{Z1(f)}{Z2(f)}$$

$$n := 0..4000 \quad f_n := n \cdot 10^6 \quad VL_n := Vld(f_n) \quad VLdeg_n := \arg(VL_n) \cdot \frac{180}{\pi}$$

$$VLdB_n := 20 \cdot \log(|VL_n|) \quad IL_n := VLdB_n - 10 \cdot \log(0.25)$$

