

8.10 Design a three-section bandstop lumped-element filter with a 0.5 dB equal-ripple response, a bandwidth of 10% centered at 3 GHz, and an impedance of 75 Ω . What is the resulting attenuation at 3.1 GHz? Use CAD to plot the insertion loss versus frequency.

- Also, draw labeled sketch of design. **Normalize passband to 0 dB.**

➤ Per (8.75), $\Delta \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1} = 0.1 \left(\frac{3.1}{3} - \frac{3}{3.1} \right)^{-1} = 1.5246$ is the equivalent LP prototype frequency where $\omega_c = 1$ rad/s for this bandstop filter.

➤ Calculate $|\omega/\omega_c| - 1 = |1.5246/1| - 1 = 0.5246$. From Figure 8.27a, we see that a LP prototype filter of order $N=3$ has an expected attenuation of ~10.3 dB.

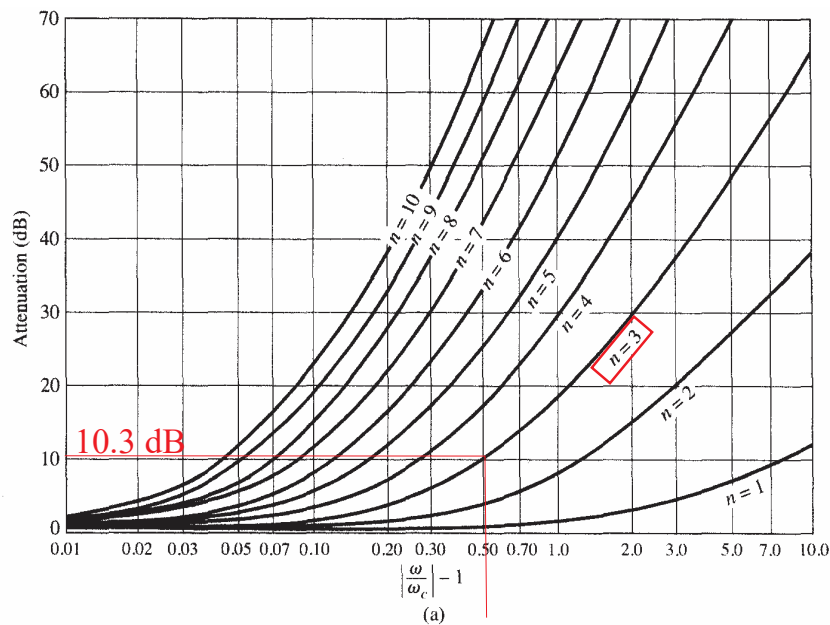


FIGURE 8.27 Attenuation versus normalized frequency for equal-ripple filter prototypes. (a) 0.5 dB ripple level.

Adapted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

➤ From Table 8.4, we get immittances: $g_1 = g_3 = 1.5963$, $g_2 = 1.0967$, and $g_4 = 1$ (matched).

TABLE 8.4 Element Values for Equal-Ripple Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10, 0.5 dB ripple)

| N | 0.5 dB Ripple | | | | | | | | | |
|-----|---------------|--------|--------|--------|--------|--------|--------|--------|--------|----------|
| | g_1 | g_2 | g_3 | g_4 | g_5 | g_6 | g_7 | g_8 | g_9 | g_{10} |
| 1 | 0.6986 | 1.0000 | | | | | | | | |
| 2 | 1.4029 | 0.7071 | 1.9841 | | | | | | | |
| 3 | 1.5963 | 1.0967 | 1.5963 | 1.0000 | | | | | | |
| 4 | 1.6703 | 1.1926 | 2.3661 | 0.8419 | 1.9841 | | | | | |
| 5 | 1.7058 | 1.2296 | 2.5408 | 1.2296 | 1.7058 | 1.0000 | | | | |
| 6 | 1.7254 | 1.2479 | 2.6064 | 1.3137 | 2.4758 | 0.8696 | 1.9841 | | | |
| 7 | 1.7372 | 1.2583 | 2.6381 | 1.3444 | 2.6381 | 1.2583 | 1.7372 | 1.0000 | | |
| 8 | 1.7451 | 1.2647 | 2.6564 | 1.3590 | 2.6964 | 1.3389 | 2.5093 | 0.8796 | 1.9841 | |
| 9 | 1.7504 | 1.2690 | 2.6678 | 1.3673 | 2.7239 | 1.3673 | 2.6678 | 1.2690 | 1.7504 | 1.0000 |
| 10 | 1.7543 | 1.2721 | 2.6754 | 1.3725 | 2.7392 | 1.3806 | 2.7231 | 1.3485 | 2.5239 | 0.8842 |

- For the filter architecture of Fig 8.25a, the necessary scaled & transformed LP shunt capacitors become a series LC using immittances $g_1 = g_3$, equations (8.76c) & (8.76d) for transformed L & C , and (8.64a) & (8.64b) for impedance scaling:

$$g_1 = 1.5963 \Rightarrow L'_1 = L'_3 = \frac{R_0}{\omega_0 \Delta L_k} = \frac{R_0}{\omega_0 \Delta g_1} = \frac{75}{(2\pi)3 \times 10^9 (0.1)1.5963} \Rightarrow \underline{L'_1 = L'_3 = 24.9256 \text{ nH}}$$

$$C'_1 = C'_3 = \frac{\Delta C_k}{\omega_0 R_0} = \frac{\Delta g_1}{\omega_0 R_0} = \frac{0.1(1.5963)}{(2\pi)3 \times 10^9 (75)} \Rightarrow \underline{C'_1 = C'_3 = 0.1129 \text{ pF}}$$

- For the filter architecture of Fig 8.25a, the necessary scaled & transformed LP series inductor becomes a parallel LC using immittance g_2 , equations (8.76a) & (8.76b) for transformed L & C , and (8.64a) & (8.64b) for impedance scaling:


$$g_2 = 1.0967 \Rightarrow L'_2 = \frac{\Delta L_k R_0}{\omega_0} = \frac{\Delta g_2 R_0}{\omega_0} = \frac{0.1(1.0967)75}{(2\pi)3 \times 10^9} \Rightarrow \underline{L'_2 = 0.4364 \text{ nH}}$$

$$C'_2 = \frac{1}{\omega_0 \Delta L_k R_0} = \frac{1}{\omega_0 \Delta g_2 R_0} = \frac{1}{(2\pi)3 \times 10^9 (0.1)1.0967(75)} \Rightarrow \underline{C'_2 = 6.4499 \text{ pF}}$$

- Per (8.64d), $g_4 = 1 \Rightarrow R'_L = R_0 R_L = R_0 g_6 = 50(1) \Rightarrow \underline{R'_L = 50 \Omega}$.

- Further, the source resistance per (8.64c) is: $R'_S = R_0 \Rightarrow \underline{R'_S = 50 \Omega}$.

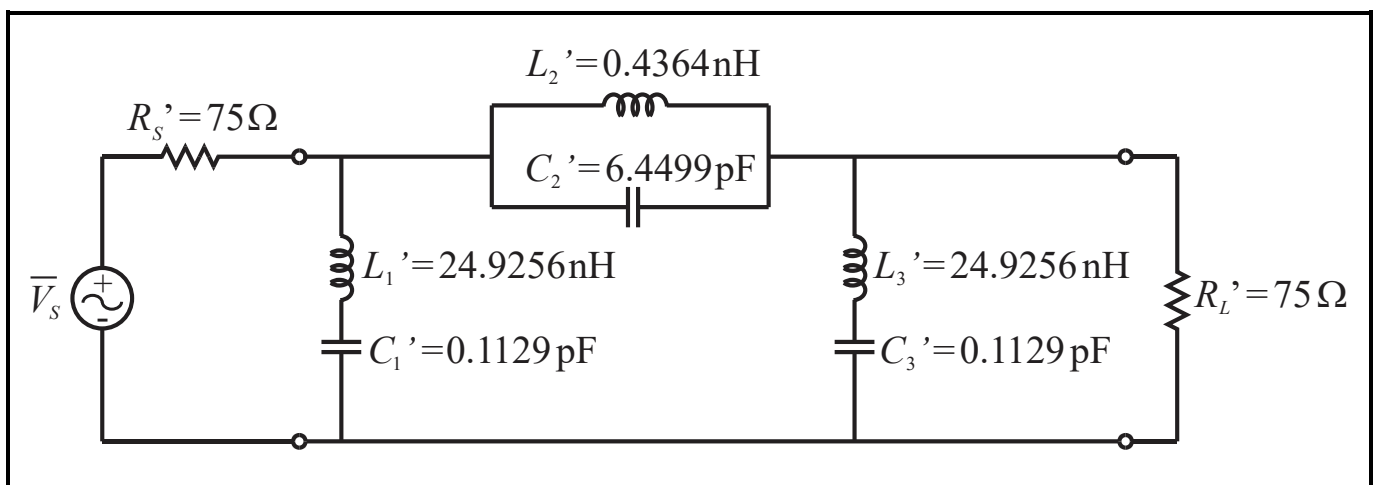- The resulting **bandstop** filter circuit is:



- See MathCad on next page for actual **filter attenuation of 10.897 dB** at 3.1 GHz which is a bit better than the predicted 10.3 dB.

Define constants

$$V_S := 1 \quad V \quad R_S := 75 \quad \Omega \quad R_L := 75 \quad \Omega \quad f_c := 3 \cdot 10^9 \quad \text{Hz}$$

$$C_1 := 0.1129 \cdot 10^{-12} \quad F \quad C_3 := C_1 \quad L_1 := 24.9256 \cdot 10^{-9} \quad H \quad L_3 := L_1$$

$$C_2 := 6.4499 \cdot 10^{-12} \quad F \quad L_2 := 0.4364 \cdot 10^{-9} \quad H$$

$$\text{Parallel } R_L // (Z_{C3} + Z_{L3}) \quad Z_1(f) := \left[\frac{1}{R_L} + \frac{1}{(j \cdot 2 \cdot \pi \cdot f \cdot L_3) + \frac{1}{(j \cdot 2 \cdot \pi \cdot f \cdot C_3)}} \right]^{-1}$$

$$\text{Series } (Z_{C2} // Z_{L2}) + Z_1 \quad Z_2(f) := \left(\frac{1}{j \cdot 2 \cdot \pi \cdot f \cdot L_2} + j \cdot 2 \cdot \pi \cdot f \cdot C_2 \right)^{-1} + Z_1(f)$$

$$\text{Parallel } Z_2 // (Z_{C1} + Z_{L1}) \quad Z_{in}(f) := \left[\frac{1}{Z_2(f)} + \frac{1}{(j \cdot 2 \cdot \pi \cdot f \cdot L_1) + \frac{1}{(j \cdot 2 \cdot \pi \cdot f \cdot C_1)}} \right]^{-1}$$

$$\text{Voltage division to get } V_{ld} \quad V_{ld}(f) := V_S \cdot \frac{Z_{in}(f)}{R_S + Z_{in}(f)} \cdot \frac{Z_1(f)}{Z_2(f)}$$

$$n := 1..6000 \quad f_n := n \cdot 10^6 \quad V_{L_n} := V_{ld}(f_n) \quad V_{Ldeg_n} := \arg(V_{L_n}) \cdot \frac{180}{\pi}$$

$$V_{LdB_n} := 20 \cdot \log(|V_{L_n}|) \quad I_{L_n} := V_{LdB_n} - 10 \cdot \log(0.25) \quad \boxed{I_{L3100} = -10.897} \quad \text{dB}$$

