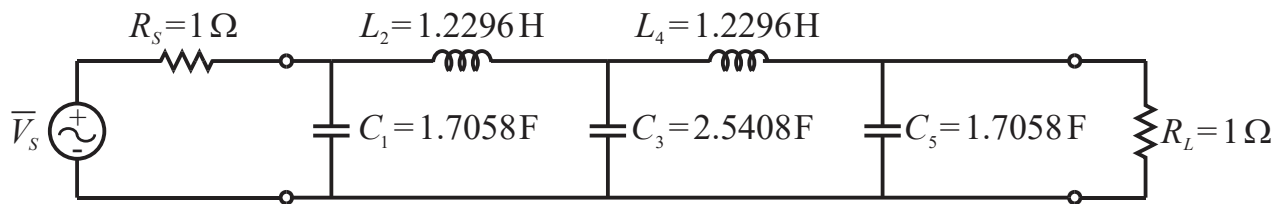


Use MWI program to design a microstrip implementation of the stepped-impedance low-pass filter designed in 8.16a on Rogers RO4003C with 1 oz. copper and 0.06" board thickness. [Hint: Use 'Dk values for characteristic impedance' option.] a) Find width  $w_{15}$ , phase velocity  $v_{15}$ , wavelength  $\lambda_{15}$ , and length of 15  $\Omega$  sections. b) Find width  $w_{120}$ , phase velocity  $v_{120}$ , wavelength  $\lambda_{120}$ , and length of 120  $\Omega$  sections. c) Find width  $w_{50}$ , phase velocity  $v_{50}$ , and wavelength  $\lambda_{50}$  for 50  $\Omega$  microstrip. d) Draw a fully-labeled top view sketch of design with 50  $\Omega$  microstrip traces (indefinite length) at input and output. For legibility, the sketch may be scaled.

\*\*\*\*\*

**8.16** Design a stepped-impedance low-pass filter having a cutoff frequency of 3 GHz and a fifth-order 0.5 dB equal-ripple response. Assume  $R_0 = 50 \Omega$ ,  $Z_\ell = 15 \Omega$ , and  $Z_h = 120 \Omega$ . (a) Find the required electrical lengths of the five sections, and

➤ For the filter architecture of Fig 8.25a, we have



➤ Using the immittances, given  $Z_0$ ,  $Z_l$  &  $Z_h$ , and equations (8.86a) & (8.86b), the electrical lengths are:

For  $C_1 = C_5 = 1.7058 \text{ F} \Rightarrow$

$$\beta l_1 = \beta l_5 = \frac{C Z_l}{R_0} = \frac{g_1 Z_l}{R_0} = \frac{1.7058(15)}{50} \Rightarrow \underline{\beta l_1 = \beta l_5 = 0.51174 \text{ rad} = 29.32^\circ}$$

For  $L_2 = L_4 = 1.2296 \text{ H} \Rightarrow$

$$\beta l_2 = \beta l_4 = \frac{L R_0}{Z_h} = \frac{g_2 R_0}{Z_h} = \frac{1.2296(50)}{120} \Rightarrow \underline{\beta l_2 = \beta l_4 = 0.5123 \text{ rad} = 29.35^\circ}$$

For  $C_3 = 2.5408 \text{ F} \Rightarrow$

$$\beta l_3 = \frac{C Z_l}{R_0} = \frac{g_3 Z_l}{R_0} = \frac{2.5408(15)}{50} \Rightarrow \underline{\beta l_3 = 0.76224 \text{ rad} = 43.67^\circ}$$

\*\*\*\*\*

a) Find width  $w_{15}$ , phase velocity  $v_{15}$ , wavelength  $\lambda_{15}$ , and length of 15  $\Omega$  sections.

For  $Z_\ell = 15 \Omega$ , MWI gives:

$$\Rightarrow \underline{w_{15} = 17.18 \text{ mm}},$$

$$\text{with a phase velocity} \Rightarrow \underline{v_{15} = 1.65 \times 10^8 \text{ m/s}}.$$

$$\text{So, the wavelength is } \lambda_\ell = \lambda_{15} = \frac{v_p}{f} = \frac{1.65 \times 10^8}{3 \times 10^9} \Rightarrow \underline{\lambda_{15} = 55.0 \text{ mm}}.$$

The length for the capacitive sections  $C_1$  and  $C_5$  are:

$$\ell_1 = \ell_5 = \frac{\beta \ell_1}{\beta} = \frac{\beta \ell_1}{2\pi / \lambda_{15}} = \frac{\beta \ell_1 (\lambda_{15})}{2\pi} = \frac{0.51174(55.4)}{2\pi} \Rightarrow \underline{\ell_1 = \ell_5 = 4.51 \text{ mm.}}$$

The length for the capacitive section  $C_3$  is:

$$\ell_3 = \frac{\beta \ell_3}{\beta} = \frac{\beta \ell_3}{2\pi / \lambda_{15}} = \frac{\beta \ell_3 (\lambda_{15})}{2\pi} = \frac{0.76224(55.4)}{2\pi} \Rightarrow \underline{\ell_3 = 6.72 \text{ mm.}}$$

b) Find width  $w_{120}$ , phase velocity  $v_{120}$ , wavelength  $\lambda_{120}$ , and length of  $120 \Omega$  sections.

For  $Z_h = 120 \Omega$ , MWI gives:

$$\Rightarrow \underline{w_{120} = 0.517 \text{ mm,}}$$

$$\text{with a phase velocity} \Rightarrow \underline{v_{120} = 1.876 \times 10^8 \text{ m/s.}}$$

$$\text{So, the wavelength is } \lambda_h = \lambda_{120} = \frac{v_p}{f} = \frac{1.876 \times 10^8}{3 \times 10^9} \Rightarrow \underline{\lambda_{120} = 62.533 \text{ mm.}}$$

The lengths for the inductive sections  $L_2$  and  $L_4$  are:

$$\ell_2 = \ell_4 = \frac{\beta \ell_2}{\beta} = \frac{\beta \ell_2}{2\pi / \lambda_{120}} = \frac{\beta \ell_2 (\lambda_{120})}{2\pi} = \frac{0.5123(62.533)}{2\pi} \Rightarrow \underline{\ell_2 = \ell_4 = 5.099 \text{ mm.}}$$

c) Find width  $w_{50}$ , phase velocity  $v_{50}$ , and wavelength  $\lambda_{50}$  for  $50 \Omega$  microstrip.

For  $Z_0 = 50 \Omega$ , MWI gives:

$$\Rightarrow \underline{w_{50} = 3.454 \text{ mm,}}$$

$$\text{with a phase velocity} \Rightarrow \underline{v_{50} = 1.786 \times 10^8 \text{ m/s.}}$$

$$\text{So, the wavelength is } \lambda_{50} = \frac{v_p}{f} = \frac{1.786 \times 10^8}{3 \times 10^9} \Rightarrow \underline{\lambda_{50} = 59.533 \text{ mm.}}$$

➤ The resulting stepped-impedance lowpass filter circuit (150% of original) is:

