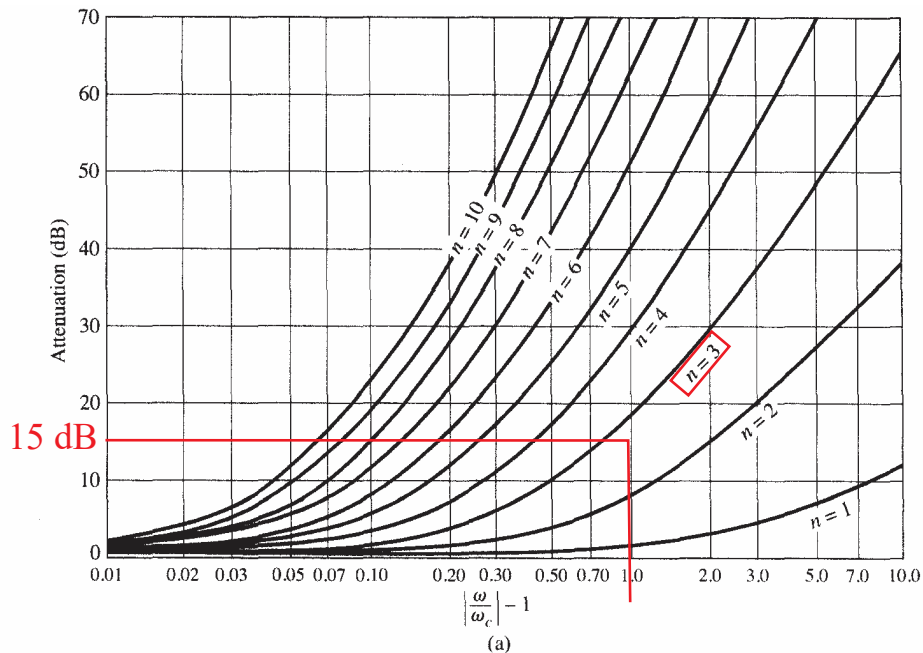


For a  $50\ \Omega$  system, design a lumped-element, 0.5 dB ripple, Chebyshev low-pass filter with a cut-off frequency of 2.4 GHz with an attenuation of at least 15 dB at 4.8 GHz using the architecture of Fig. 8.25a. a) Determine the filter order  $N$  and the low-pass filter prototype element values. b) Draw a labeled sketch of the scaled filter with component values. c) Draw a labeled sketch of the filter in phasor form with  $V_s = 1\angle 0^\circ$  V. d) Plot the amplitude response  $|V_L|$  in decibels with horizontal dashed lines at  $20\log(0.5)$  &  $20\log(0.5)-0.5$  and a vertical dashed line at 2.4 GHz for  $0 \leq f \leq 5$  GHz &  $-25\text{ dB} \leq |V_L| \leq 0$ .

a) Calculate  $|\omega/\omega_c| - 1 = |4.8/2.4| - 1 = 1$ . From Figure 8.27a, we see that a LP prototype filter of order  $N=3$  is needed to meet the 15 dB attenuation specification.



**FIGURE 8.27** Attenuation versus normalized frequency for equal-ripple filter prototypes. (a) 0.5 dB ripple level.

Adapted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

From Table 8.4, we get the immittances:

$g_0 = g_4 = 1$  (resistors),  $g_1 = g_3 = 1.5963$  (capacitors), and  $g_2 = 1.0967$  (inductor).

**TABLE 8.4** Element Values for Equal-Ripple Low-Pass Filter Prototypes ( $g_0 = 1$ ,  $\omega_c = 1$ ,  $N = 1$  to 10, 0.5 dB ripple)

$N$	0.5 dB Ripple										
	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

- b) For filter architecture of Fig 8.25a, use the immittances & equations (8.64cd), & (8.67ab) to get necessary scaled & transformed shunt inductances and series capacitances:


Per (8.64c),  $R'_s = R_0 = 50 \Rightarrow \underline{R'_s = 50 \Omega}.$

Per (8.67b),  $C'_1 = C'_3 = \frac{C_k}{R_0 \omega_c} = \frac{g_1}{R_0 \omega_c} = \frac{1.5963}{50 (2\pi) 2.4 \times 10^9} \Rightarrow \underline{C'_1 = C'_3 = 2.117 \text{ pF}.}$

Per (8.67a),  $L'_2 = \frac{R_0 L_k}{\omega_c} = \frac{R_0 g_2}{\omega_c} = \frac{50 (1.0967)}{(2\pi) 2.4 \times 10^9} \Rightarrow \underline{L'_2 = 3.636 \text{ nH}.}$


Per (8.64d),  $R'_L = R_0 R_L = R_0 g_4 = 50(1) \Rightarrow \underline{R'_L = 50 \Omega}.$

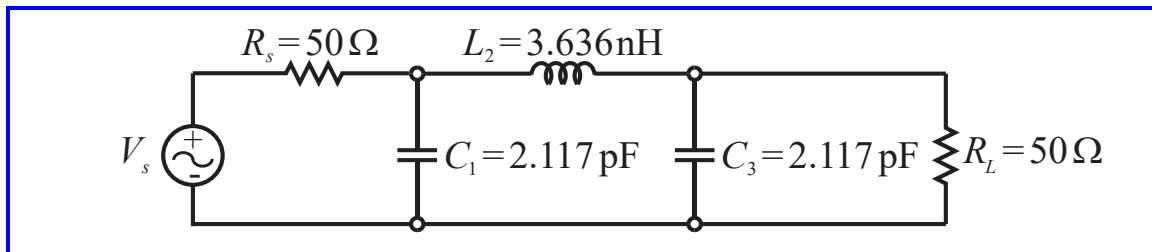➤ The resulting **Chebyshev lowpass** filter circuit with component values is:



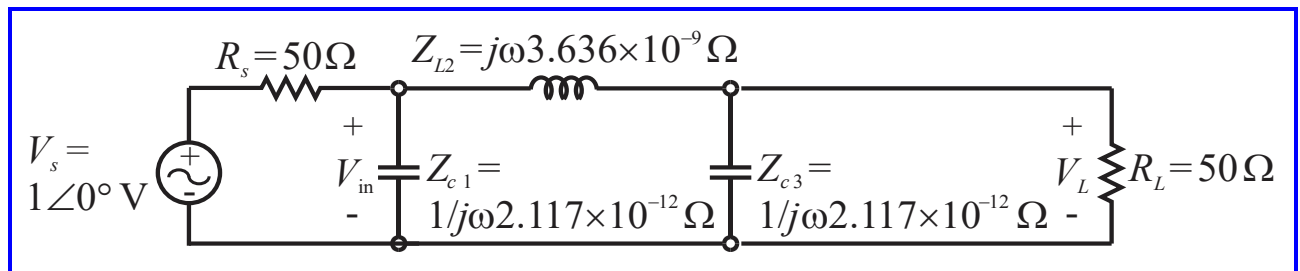- c) From circuits, use  $Z_R = R$ ,  $Z_L = j\omega L$ , and  $Z_C = 1/j\omega C$ .

The resulting **Chebyshev lowpass** filter circuit in phasor form is:



- d) Using MathCAD

<b>System impedance</b>	$Z_0 := 50 \quad \Omega$	$n := 1..500$	$f_n := n \cdot 10^7$
<b>CEbyshev lumped element design N = 3</b>		$f_c := 2.4 \cdot 10^9 \quad \text{Hz}$	
<b>Table 8.3 LPF prototype</b>	$g_0 := 1$	$g_1 := 1.5963$	$g_2 := 1.0967 \quad g_3 := g_1 \quad g_4 := 1$
$R_S := g_0 \cdot Z_0$	$C_1 := \frac{g_1}{Z_0 \cdot 2 \cdot \pi \cdot f_c}$	$L_2 := \frac{Z_0 \cdot g_2}{2 \cdot \pi \cdot f_c}$	$C_3 := C_1 \quad R_L := Z_0 \cdot g_4$
$V_S := 1 \quad \text{V}$	$R_S = 50 \quad \Omega$		$C_1 = 2.11716 \times 10^{-12} \quad \text{F}$
$L_2 = 3.63636 \times 10^{-9} \quad \text{H}$	$C_3 = 2.11716 \times 10^{-12} \quad \text{F}$	$R_L = 50 \quad \Omega$	

Parallel impedance of RL & C3 
$$Z1(f) := \left( \frac{1}{RL} + j \cdot 2 \cdot \pi \cdot f \cdot C3 \right)^{-1}$$

Series impedance of L2 & Z1 
$$Z2(f) := j \cdot 2 \cdot \pi \cdot f \cdot L2 + Z1(f)$$

Input impedance of LP filter w/ load 
$$Zin(f) := \left( \frac{1}{Z2(f)} + j \cdot 2 \cdot \pi \cdot f \cdot C1 \right)^{-1}$$

Voltage divisions to get  $V_{in}$  &  $V_{ld}$  
$$V_{in}(f) := VS \cdot \frac{Zin(f)}{RS + Zin(f)} \quad V_{ld}(f) := V_{in}(f) \cdot \frac{Z1(f)}{Z2(f)}$$

$VIN_n := V_{in}(f_n) \quad VL_n := V_{ld}(f_n) \quad VL\_dB_n := 20 \cdot \log(|VL_n|)$

$vert24 := \begin{pmatrix} 0 \\ -25 \end{pmatrix} \quad vertf := \begin{pmatrix} 2.4 \cdot 10^9 \\ 2.4 \cdot 10^9 \end{pmatrix}$

