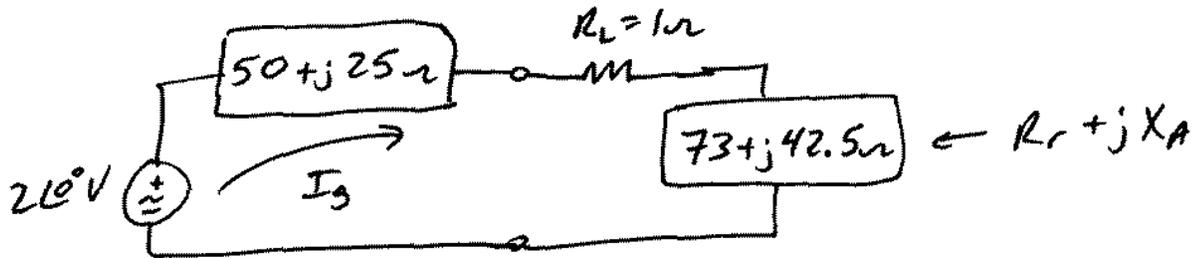


- 2.53 A $\lambda/2$ dipole, with a total loss resistance of 1 ohm, is connected to a generator whose internal impedance is $50 + j25$ ohms. Assuming that the peak voltage of the generator is 2 V and the impedance of the dipole, excluding the loss resistance, is $73 + j42.5$ ohms, find the power
- (a) supplied by the source (real) (b) radiated by the antenna
- (c) dissipated by the antenna

Eqn. Ckt.



$$I_g = \frac{2\angle 0^\circ \text{ V}}{(50 + j25) + 1 + (73 + j42.5)} = 0.01416615 \angle -28.56188^\circ \text{ A}$$

$$\begin{aligned} \text{a) } P_{\text{source}} &= \frac{1}{2} \operatorname{Re} \{ V_g I_g^* \} = \frac{1}{2} \operatorname{Re} \{ (2\angle 0^\circ) (0.01416615 \angle +28.56188^\circ) \} \\ &= \operatorname{Re} \{ 0.01244215 + j0.006773 \} \end{aligned}$$

$$\underline{\underline{P_{\text{source}} = 0.01244 \text{ W} = 12.442 \text{ mW}}}$$

$$\begin{aligned} \text{b) } P_{\text{rad}} &= \frac{1}{2} |I_g|^2 R_r = \frac{1}{2} |0.01416615|^2 (73) \\ &= \underline{\underline{0.0073 \text{ W} = 7.325 \text{ mW}}} \end{aligned}$$

$$\begin{aligned} \text{c) } P_{\text{loss}} &= \frac{1}{2} |I_g|^2 R_L = \frac{1}{2} |0.01416615|^2 (1) \\ &= \underline{\underline{0.0001 \text{ W} = 0.1003 \text{ mW}}} \end{aligned}$$