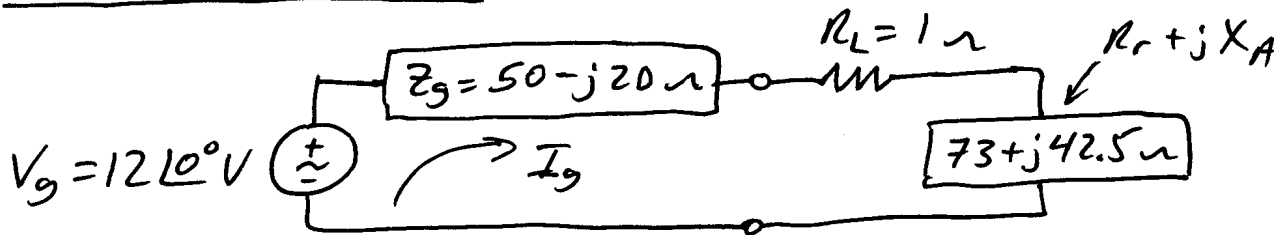


- 2.53 A $\lambda/2$ dipole, with a total loss resistance of 1 ohm, is connected to a generator whose internal impedance is $50 + j25$ ohms. Assuming that the peak voltage of the generator is 2 V and the impedance of the dipole, excluding the loss resistance, is $73 + j42.5$ ohms, find the power
- (a) supplied by the source (real) (b) radiated by the antenna
 (c) dissipated by the antenna
- Make **generator** peak voltage 12 V and impedance of $50 - j20 \Omega$. [Hint: Look at Chapter 4 section on $\lambda/2$ dipoles.]
 - Per (4-93a), $Z_{in} = 73 + j42.5 \Omega$ for a lossless $\lambda/2$ dipole.

Equivalent circuit



$$I_g = \frac{V_g}{z_{eq}} = \frac{12 \angle 0^\circ}{(50 - j20) + 1 + 73 + j42.5}$$

$$= 0.09521935 \angle -10.2845^\circ \text{ A}$$

$$a) P_{source} = \frac{1}{2} \operatorname{Re}\{V_g I_g^*\} = \frac{1}{2} \operatorname{Re}\{12 \angle 0^\circ (0.0952 \angle +10.28^\circ)\}$$

$$= \frac{1}{2} \operatorname{Re}\{1.1243 + j0.204\}$$

$$\underline{P_{source} = 0.5621 \text{ W}}$$

$$b) P_{rad} = \frac{1}{2} |I_g|^2 R_r = \frac{1}{2} (0.09521935)^2 73$$

$$\underline{P_{rad} = 0.3309 \text{ W}}$$

$$c) P_{loss} = \frac{1}{2} |I_g|^2 R_L = \frac{1}{2} (0.09521935)^2 1$$

$$\underline{P_{loss} = 4.533 \text{ mW}}$$