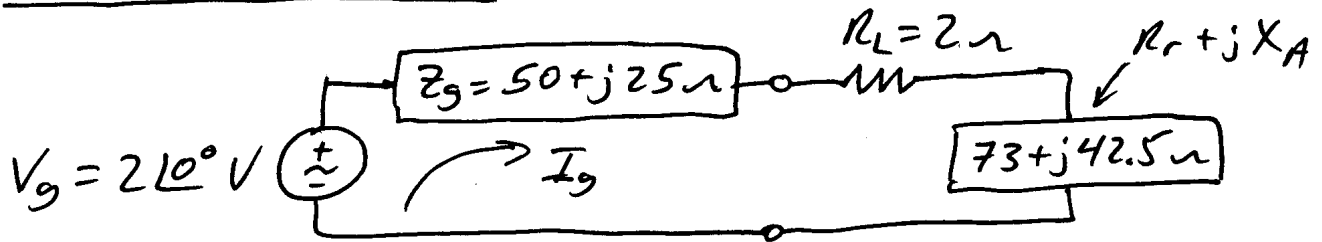


- 2.53 A $\lambda/2$ dipole, with a total loss resistance of 2 ohm, is connected to a generator whose internal impedance is $50 + j25$ ohms. Assuming that the peak voltage of the generator is 2 V and the impedance of the dipole, excluding the loss resistance, is $73 + j42.5$ ohms, find the power
- (a) supplied by the source (real) (b) radiated by the antenna
 (c) dissipated by the antenna

- Assume loss resistance is 2Ω . Hint: Look at Chapter 4 section on $\lambda/2$ dipoles.

Equivalent circuit



$$I_g = \frac{V_g}{Z_{eq}} = \frac{2\angle 0^\circ}{(50 + j25) + 2 + 73 + j42.5}$$

$$= 0.0140785 \angle -28.369^\circ \text{ A}$$

$$a) P_{source} = \frac{1}{2} \operatorname{Re}\{V_g I_g^*\} = \frac{1}{2} \operatorname{Re}\{2\angle 0^\circ (0.0140785 \angle +28.37^\circ)\}$$

$$= \operatorname{Re}\{0.01238774 + j0.00669\}$$

$$\underline{\underline{P_{source} = 12.3877 \text{ mW}}}$$

$$b) P_{rad} = \frac{1}{2} |I_g|^2 R_r = \frac{1}{2} (0.0140785)^2 73$$

$$\underline{\underline{P_{rad} = 7.2344 \text{ mW}}}$$

$$c) P_{loss} = \frac{1}{2} |I_g|^2 R_L = \frac{1}{2} (0.0140785)^2 2$$

$$\underline{\underline{P_{loss} = 0.1982 \text{ mW}}}$$