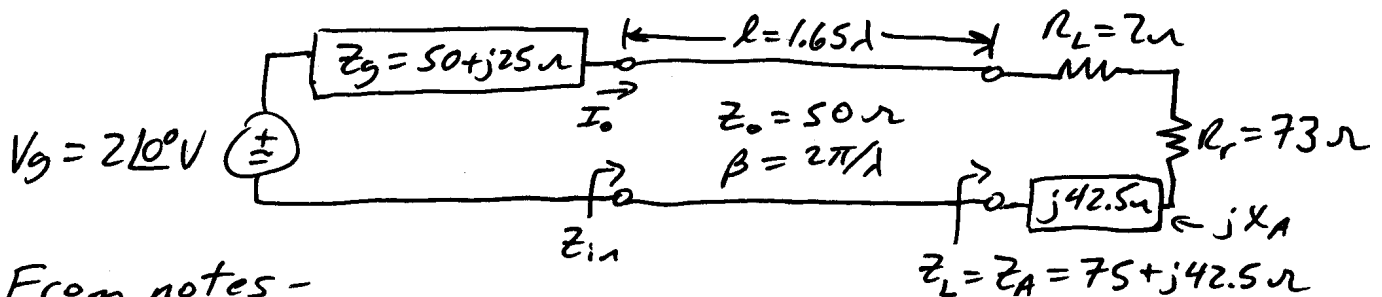



- 2.53 A  $\lambda/2$  dipole, with a total loss resistance of 2 ohm, is connected to a generator whose internal impedance is  $50 + j25$  ohms. Assuming that the peak voltage of the generator is 2 V and the impedance of the dipole, excluding the loss resistance, is  $73 + j42.5$  ohms, find the power
- supplied by the source (real)
  - radiated by the antenna
  - dissipated by the antenna
- Assume loss resistance is  $2 \Omega$  and the generator has a lossless  $50 \Omega$  transmission line of length  $1.65\lambda$  connecting it to the antenna.



From notes -

$$Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan(\beta l)}{Z_0 + j Z_L \tan(\beta l)} \right] = 50 \left[ \frac{(73 + j42.5) + j50 \tan\left(\frac{2\pi}{\lambda} 1.65\lambda\right)}{50 + j(73 + j42.5) \tan(3.3\pi)} \right]$$

$$Z_{in} = 50.58613 - j40.49062 \Omega$$

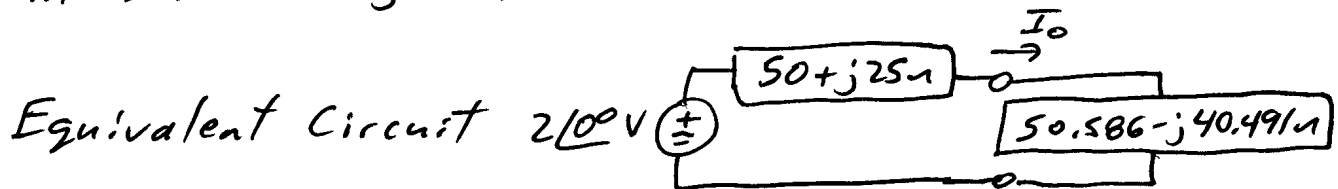

$$I_0 = \frac{2\angle 0^\circ}{(50 + j25) + (50.586 - j40.491)} = 0.0196518 \angle -8.755^\circ \text{ A}$$

$$a) P_{source} = \frac{1}{2} \text{Re}\{V_g I_0^*\} = \frac{1}{2} \text{Re}\{2\angle 0^\circ (0.01965) \angle -8.755^\circ\}$$

$$\underline{\underline{P_{source} = 19.4228 \text{ mW}}}$$

For a lossless TL,  $P_{in} = P_{ant}$ ,  $P_{loss} = \frac{R_L}{R_r + R_L} P_{ant}$ , &  $P_r = \frac{R_r}{R_r + R_L} P_{ant}$

$$P_{ant} = P_{in} = \frac{1}{2} |I_0|^2 R_{in} = \frac{1}{2} (0.01965)^2 50.586 = 9.768 \text{ mW}$$

$$b) P_{rad} = \frac{73}{73+2} (9.768) \Rightarrow \underline{\underline{P_{rad} = 9.5075 \text{ mW}}}$$

$$c) P_{loss} = \frac{2}{73+2} (9.768) \Rightarrow \underline{\underline{P_{loss} = 0.2605 \text{ mW}}}$$