


For the match of problem 2, **analytically** find the input impedance  $Z_{in}$ , reflection coefficient  $\Gamma_{in}$ , and VSWR at 195, 200, & 205 MHz on the feeding transmission line just past the inductor toward the generator assuming  $Z_A$  remains constant. Tabulate results- col. 1 frequency, col. 2  $Z_{in}$  (rectangular format), col. 3  $\Gamma$  (polar format), and col. 4 VSWR.

\*\*\*\*\*

- 2) You have an antenna with input impedance  $Z_A = 12.5 + j40 \Omega$  at 200 MHz. Match it to a feeding transmission line ( $Z_0 = 50 \Omega$  &  $u = 2.5 \times 10^8$  m/s) using a discrete inductor connected in series as close to the antenna as possible. Draw a fully labeled sketch of the final design.

➤ The wavelength is  $\lambda = c/f = 2.5 \times 10^8 / 200 \times 10^6 = 1.25$  m = 125 cm.

<snip>

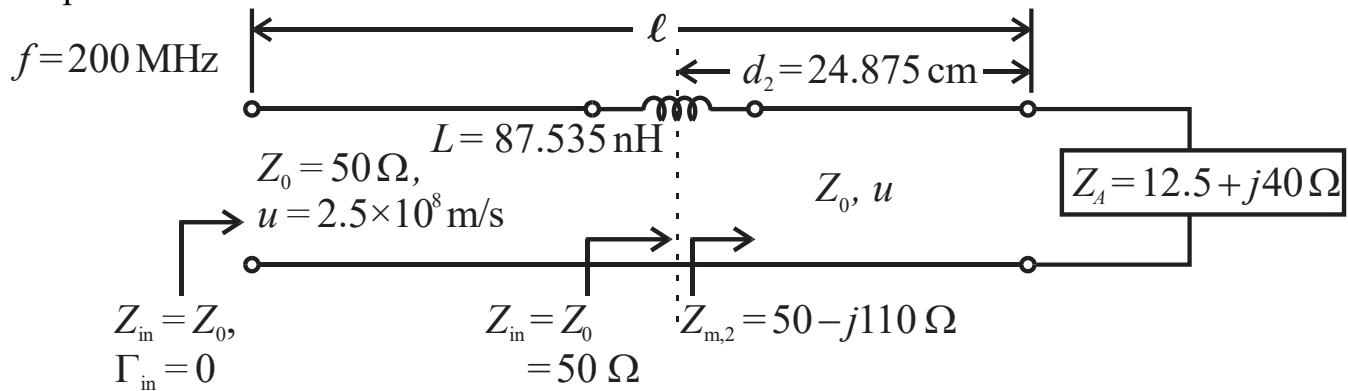

**Figure 1** Matching antenna using discrete series capacitor.

\*\*\*\*\*

First, analytically calculate the reflection coefficient at the antenna. It is assumed to be constant with respect to frequency. [Note: All calculations checked using MathCad.]

$$\Gamma_A = \frac{Z_A - Z_0}{Z_A + Z_0} = \frac{(12.5 + j40) - 50}{(12.5 + j40) + 50} \Rightarrow \Gamma_A = 0.7389 \angle 100.533^\circ$$

Next, find the reflection coefficient at the match point ( $d_2 = 24.875$  cm) for each frequency.

$$\Gamma_{in,f} = \Gamma_A e^{-j2\beta d_2} = \Gamma_A e^{-j2\left(\frac{2\pi f}{u}\right)d_2} = (0.7389 \angle 100.533^\circ) e^{-j\left(\frac{4\pi f}{2.5 \times 10^8}\right)0.24875}$$

$$\text{At 195 MHz, } \Gamma_{\text{low}} = (0.7389 \angle 100.533^\circ) e^{-j\left(\frac{4\pi 195 \times 10^6}{2.5 \times 10^8}\right)0.24875} \Rightarrow \Gamma_{\text{low}} = 0.7389 \angle 39.165^\circ$$

$$\text{At 200 MHz, } \Gamma_{\text{ctr}} = (0.7389 \angle 100.533^\circ) e^{-j\left(\frac{4\pi 200 \times 10^6}{2.5 \times 10^8}\right)0.24875} \Rightarrow \Gamma_{\text{ctr}} = 0.7389 \angle -42.747^\circ$$

$$\text{At 205 MHz, } \Gamma_{\text{high}} = (0.7389 \angle 100.533^\circ) e^{-j\left(\frac{4\pi 205 \times 10^6}{2.5 \times 10^8}\right)0.24875} \Rightarrow \Gamma_{\text{high}} = 0.7389 \angle -46.329^\circ$$

Then, calculate the input impedance at the match point for each frequency.

$$Z_{in,f} = Z_0 \left( \frac{1 + \Gamma_{in,f}}{1 - \Gamma_{in,f}} \right) = 50 \left( \frac{1 + \Gamma_{in,f}}{1 - \Gamma_{in,f}} \right)$$

$$Z_{m,low} = 50 \left( \frac{1 + \Gamma_{low}}{1 - \Gamma_{low}} \right) = 50 \left( \frac{1 + (0.7389 \angle 39.165^\circ)}{1 - (0.7389 \angle 39.165^\circ)} \right) \Rightarrow \underline{Z_{m,low} = 56.727 - j116.609 \Omega}$$

$$Z_{m,ctr} = 50 \left( \frac{1 + \Gamma_{ctr}}{1 - \Gamma_{ctr}} \right) = 50 \left( \frac{1 + (0.7389 \angle -42.747^\circ)}{1 - (0.7389 \angle -42.747^\circ)} \right) \Rightarrow \underline{Z_{m,ctr} = 49.272 - j108.855 \Omega}$$

$$Z_{m,high} = 50 \left( \frac{1 + \Gamma_{high}}{1 - \Gamma_{high}} \right) = 50 \left( \frac{1 + (0.7389 \angle -46.329^\circ)}{1 - (0.7389 \angle -46.329^\circ)} \right) \Rightarrow \underline{Z_{m,high} = 43.198 - j101.699 \Omega}$$

Calculate the inductor impedance for each frequency.

$$Z_{ind,low} = j2\pi f_{low} L = j2\pi(195 \times 10^6) 87.535 \times 10^{-9} \Rightarrow \underline{Z_{ind,low} = j107.25 \Omega}$$

$$Z_{ind,ctr} = j2\pi f_{ctr} L = j2\pi(200 \times 10^6) 87.535 \times 10^{-9} \Rightarrow \underline{Z_{ind,low} = j110 \Omega}$$

$$Z_{ind,high} = j2\pi f_{high} L = j2\pi(205 \times 10^6) 87.535 \times 10^{-9} \Rightarrow \underline{Z_{ind,low} = j112.75 \Omega}$$

Calculate the input impedance,  $Z_{in,f} = Z_{cap,f} + Z_{m,f}$ , after matching for each frequency.

$$Z_{in,low} = j107.25 + (56.727 - j116.609) \Rightarrow \underline{Z_{in,low} = 56.727 - j9.359 \Omega}$$

$$Z_{in,ctr} = j110 + (49.272 - j108.855) \Rightarrow \underline{Z_{in,ctr} = 49.727 + j1.145 \Omega}$$

$$Z_{in,high} = j112.175 + (43.198 - j101.699) \Rightarrow \underline{Z_{in,high} = 43.198 + j11.050 \Omega}$$

Calculate the input reflection coefficient after matching for each frequency.

$$\Gamma_{in,f} = \frac{Z_{in,f} - Z_0}{Z_{in,f} + Z_0} = \frac{Z_{in,f} - 50}{Z_{in,f} + 50}$$

$$\Gamma_{in,low} = \frac{(56.727 - j9.359) - 50}{(56.727 - j9.359) + 50} \Rightarrow \underline{\Gamma_{in,low} = 0.10758 \angle -49.281.89^\circ}$$

$$\Gamma_{in,ctr} = \frac{(49.727 + j1.145) - 50}{(49.727 + j1.145) + 50} \Rightarrow \underline{\Gamma_{in,ctr} = 0.01366 \angle 121.79^\circ}$$

$$\Gamma_{in,high} = \frac{(43.198 + j11.05) - 50}{(43.198 + j11.05) + 50} \Rightarrow \underline{\Gamma_{in,high} = 0.13826 \angle 114.85^\circ}$$

Calculate the VSWR after matching for each frequency.

$$\text{VSWR}_{\text{low}} = \frac{1 + |\Gamma_{\text{low}}|}{1 - |\Gamma_{\text{low}}|} = \frac{1 + 0.10758}{1 - 0.10758} \Rightarrow \underline{\text{VSWR}_{\text{low}} = 1.241}$$

$$\text{VSWR}_{\text{ctr}} = \frac{1 + |\Gamma_{\text{ctr}}|}{1 - |\Gamma_{\text{ctr}}|} = \frac{1 + 0.01366}{1 - 0.01366} \Rightarrow \underline{\text{VSWR}_{\text{ctr}} = 1.028}$$

$$\text{VSWR}_{\text{high}} = \frac{1 + |\Gamma_{\text{high}}|}{1 - |\Gamma_{\text{high}}|} = \frac{1 + 0.13826}{1 - 0.13826} \Rightarrow \underline{\text{VSWR}_{\text{high}} = 1.321}$$

Tabulate results

$f$ (MHz)	$Z_{\text{in}}$ ( $\Omega$ )	$\Gamma$	VSWR
195	$56.727 - j9.359$	$0.10758 \angle -49.28^\circ$	1.241
200	$49.272 + j1.145$	$0.01366 \angle 121.79^\circ$	1.028
205	$43.198 + j11.05$	$0.13826 \angle 114.85^\circ$	1.321