

At 600 MHz, match an antenna ($Z_A = 20 - j50 \Omega$) to a feeding transmission line ($Z_0 = 50 \Omega$ & $u = 2.4 \times 10^8$ m/s) using a discrete capacitor connected in series as close to the antenna as possible. Draw a fully labeled sketch of final design.

➤ The wavelength is $\lambda = c/f = 2.4 \times 10^8 / 600 \times 10^6 = 0.4$ m = 40 cm.

Steps

- 1) Calculate the normalized impedance $z_A = Z_A / Z_0 = (20 - j50) / 50 \Rightarrow \underline{z_A = 0.4 - j1 \Omega/\Omega}$ and plot on **Smith chart** (see Figure 2).
- 2) Draw circle, centered on Smith chart, through z_A point. This circle of constant $|\Gamma|$ includes the locus of all possible z_{in} (and y_{in}) along the transmission line with this load.
- 3) The two match points are $z_{m,i} = 1 \pm j1.85 \Omega/\Omega$. To use a discrete series capacitor for matching, **select $z_{m,1} = 1 + j1.85 \Omega/\Omega$** as it has an inductive reactance. Note, the match point impedance is $Z_{m,1} = z_{m,1} Z_0 = (1 + j1.85) 50 = 50 + j92.5 \Omega$.
- 4) Find the distance d_1 from z_A to $z_{m,1}$ using scales on Smith chart, $d_1 = (0.131 + 0.184) \lambda \Rightarrow \underline{d_1 = 0.315\lambda}$ or $d_1 = 0.315 (40 \text{ cm}) \Rightarrow \underline{d_1 = 12.6 \text{ cm}}$.
- 5) At d_1 , add a discrete capacitor in series with reactance $Z_{cap} = -j/\omega C = -j92.5 \Omega$. Solving yields $C = 1/[(2\pi 600 \times 10^6) 92.5] = 2.86766 \times 10^{-7}$ F $\Rightarrow \underline{C = 2.87 \text{ pF}}$.
- 6) As shown on Figure 1, everywhere toward the source from the location of C will be matched, i.e., $Z_{in} = 50 \Omega$.

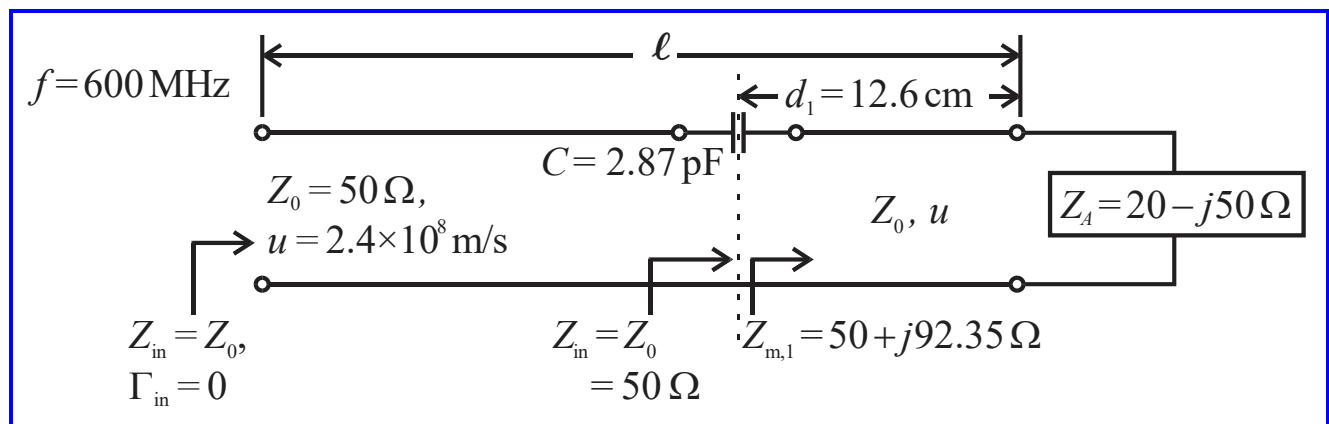


Figure 1 Matching antenna using discrete series capacitor.

Simple Smith Chart

$Z_0 = 50 \Omega$
 $f = 600 \text{ MHz}$
 $\lambda = 40 \text{ cm}$

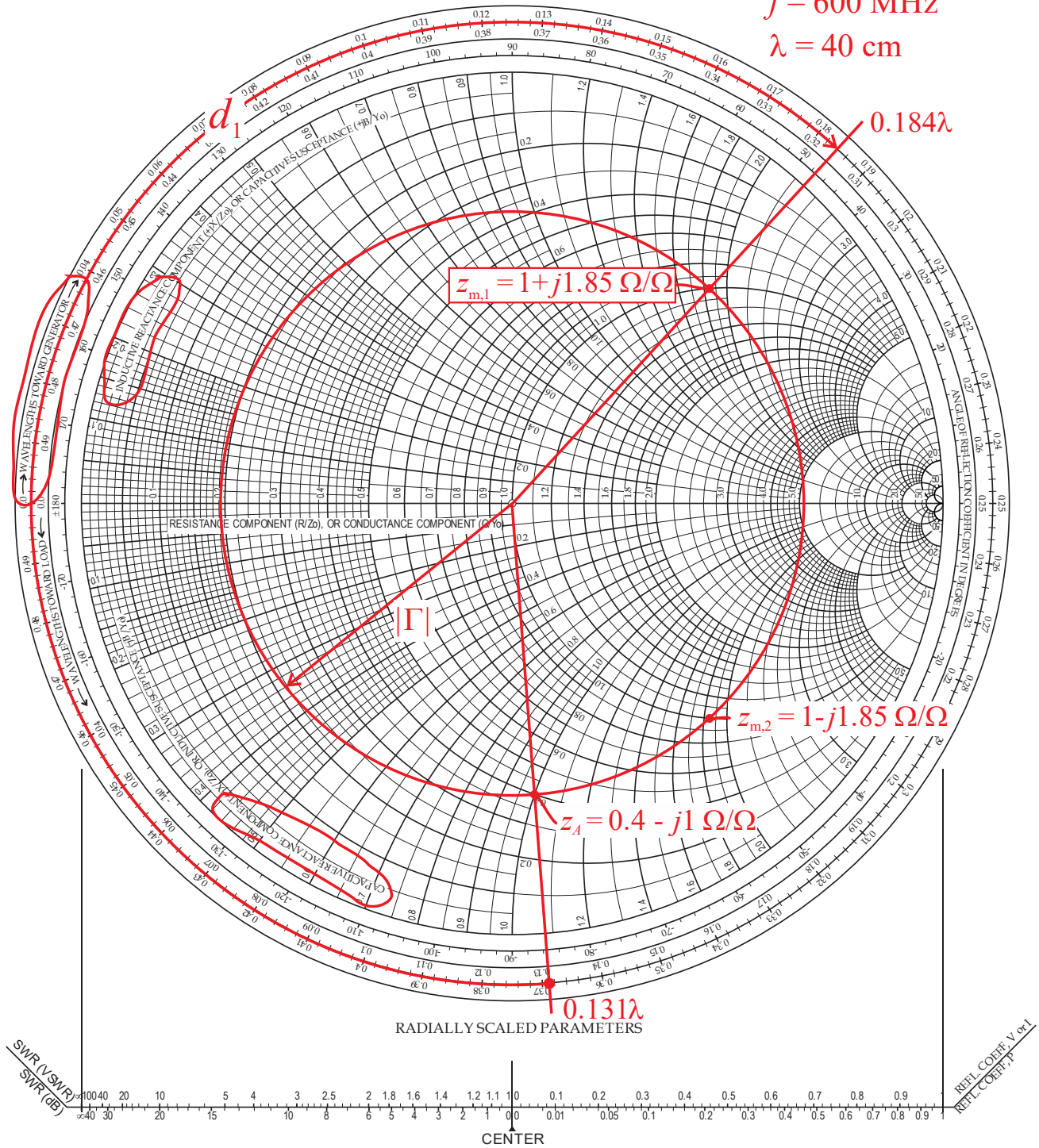


Figure 2 Smith chart for matching an antenna using discrete series capacitor.