

Other Matching Techniques Examples

Example of matching an antenna using a discrete parallel component

We have a Yagi-Uda antenna where the input impedance of the driven element is found to be $Z_A = 40 + j 80 \Omega$. We wish to match it to a feeding transmission line ($Z_0 = 50 \Omega$ & $u = 2.5 \times 10^8$ m/s) at 500 MHz using a discrete capacitor connected in parallel.

➤ The wavelength is $\lambda = u/f = 2.5 \times 10^8 / 500 \times 10^6 = 0.5$ m.

Steps

- 1) Calculate normalized impedance $z_A = Z_A/Z_0 = (40 + j 80)/50 \Rightarrow \underline{z_A = 0.8 + j 1.6 \Omega/\Omega}$ and plot on **Smith chart** (see Figure 2).
- 2) Draw circle, centered on Smith chart, through z_A point. This circle of constant $|\Gamma|$ includes the locus of all possible z_{in} (and y_{in}) along the transmission line with this load.
- 3) Go $\lambda/4$ (180°) around the circle of constant $|\Gamma|$ from z_A point to $\underline{y_A = 0.25 - j 0.5 \text{ S/S}}$ point and plot.
- 4) Note, the two match points are $y_{m,i} = 1 \pm j1.8 \text{ S/S}$. In order to use a discrete capacitor for matching, **select $y_{m,2} = 1 - j1.8 \text{ S/S}$** as it has an inductive susceptance. Note, $Y_{m,2} = y_{m,2}/Z_0 = (1 - j1.8)/50 = 0.02 - j0.036 \text{ S}$.
- 5) Find distance d_2 from y_A to $y_{m,2}$ using scales on Smith chart, $d_2 = 0.077\lambda + 0.317\lambda \Rightarrow \underline{d_2 = 0.394\lambda}$ or, in meters, $d_2 = 0.394(0.5) \Rightarrow \underline{d_2 = 0.197 \text{ m}}$.
- 6) At d_2 , add a discrete capacitor in parallel with susceptance $Y_{cap} = j\omega C = +j0.036 \text{ S}$. Solving for C yields $C = 0.036 / (2\pi 500 \times 10^6) = 1.1459 \times 10^{-11} \text{ F} \Rightarrow \underline{C = 11.459 \text{ pF}}$.
- 7) As shown on Figure 1, everywhere toward the source from the location of C will be matched, i.e., $Z_{in} = 50 \Omega$.

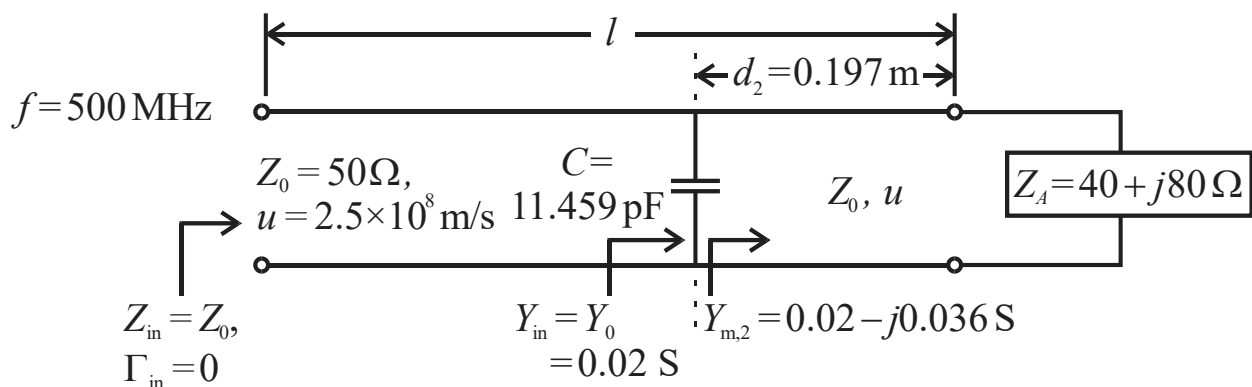


Figure 1 Matching antenna using discrete parallel capacitor.

Simple Smith Chart

$Z_0 = 50 \Omega$
 $f = 500 \text{ MHz}$
 $\lambda = 0.5 \text{ m}$

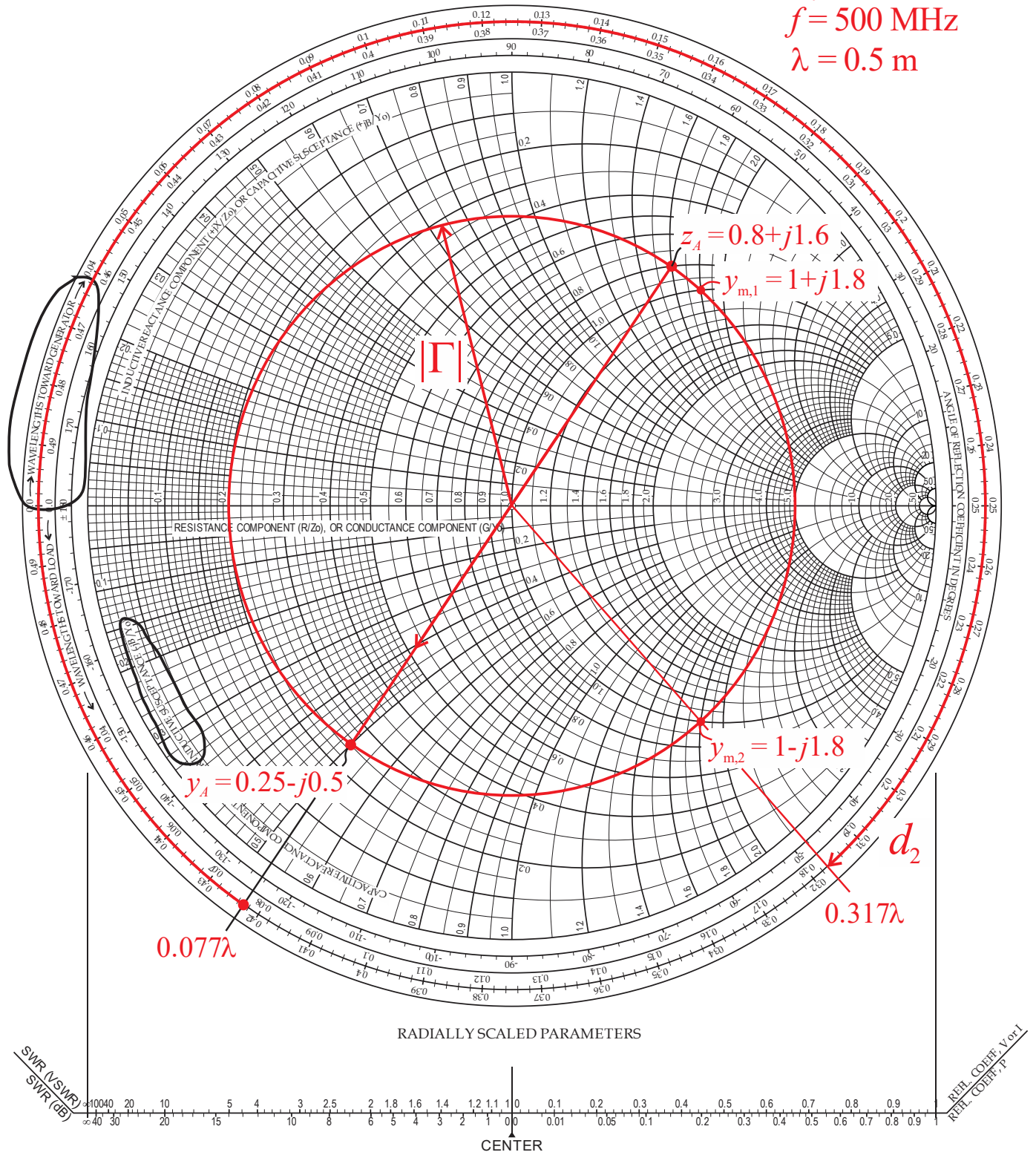


Figure 2 Smith chart for matching antenna using discrete parallel capacitor.

Example of matching an antenna using a discrete series component

We have a Yagi-Uda antenna where the input impedance of the driven element is found to be $Z_A = 17.5 + j 30 \Omega$. We wish to match it to a feeding transmission line ($Z_0 = 50 \Omega$ & $u = 2.4 \times 10^8$ m/s) at 120 MHz using a discrete inductor connected in series.

➤ The wavelength is $\lambda = u/f = 2.4 \times 10^8 / 120 \times 10^6 = 2$ m.

Steps

- 1) Calculate normalized impedance $z_A = Z_A/Z_0 = (17.5 + j 30)/50 \Rightarrow \underline{z_A = 0.35 + j 0.6 \Omega/\Omega}$ and plot on **Smith chart** (see Figure 4).
- 2) Draw circle, centered on Smith chart, through z_A point. This circle of constant $|\Gamma|$ includes the locus of all possible z_{in} along the transmission line with this load.
- 3) The two match points are $z_{m,i} = 1 \pm j1.5 \Omega/\Omega$. To use a discrete series inductor for matching, **select $z_{m,2} = 1 - j1.5 \Omega/\Omega$** as it has a capacitive reactance. Note, $Z_{m,2} = z_{m,2} Z_0 = (1 - j1.5) 50 = 50 - j75 \Omega$.
- 4) Find distance d_2 from z_A to $z_{m,2}$ using scales on Smith chart, $d_2 = 0.3241\lambda - 0.0921\lambda \Rightarrow \underline{d_2 = 0.232\lambda}$ or, in meters, $d_2 = 0.232(2) \Rightarrow \underline{d_2 = 0.464 \text{ m}}$.
- 5) At d_2 , add a discrete inductor in series with reactance $Z_{ind} = j\omega L = j75 \Omega$. Solving for L yields $L = 75/(2\pi 120 \times 10^6) = 9.947 \times 10^{-8}$ H $\Rightarrow \underline{L = 99.47 \text{ nH}}$.
- 6) As shown on Figure 3, everywhere toward the source from the inductor will see an input impedance of $Z_{in} = Z_0 = 50 \Omega$.

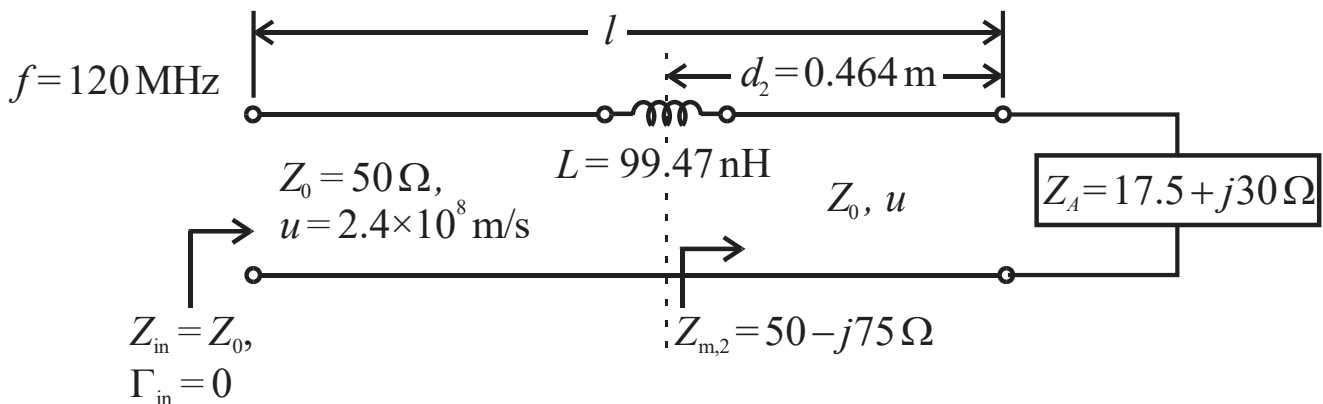


Figure 3 Matching antenna using discrete series inductor.

Simple Smith Chart

$Z_0 = 50 \Omega$
 $f = 120 \text{ MHz}$
 $\lambda = 2 \text{ m}$

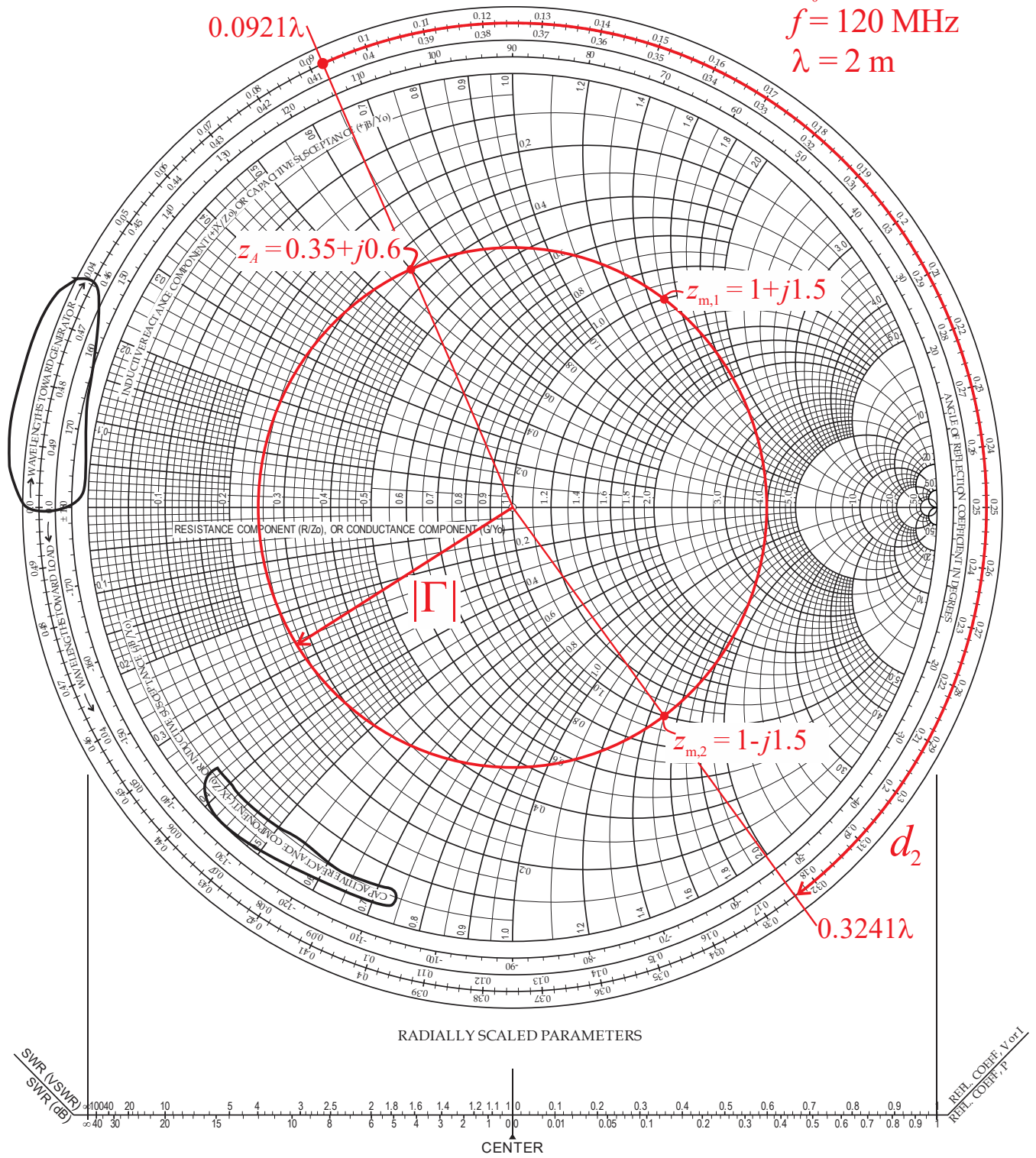


Figure 4 Smith chart for matching an antenna using discrete series inductor.

Example of matching an antenna using a shunt single-stub tuner

We have a horn antenna with an input impedance of $Z_A = 154.8 - j402 \Omega$. We wish to match it to a feeding transmission line ($Z_0 = 300 \Omega$ & $u = 2.8 \times 10^8$ m/s) at 800 MHz using a short circuit stub made from the same transmission line connected in parallel as close to the antenna as possible.

➤ The wavelength is $\lambda = u/f = 2.8 \times 10^8 / 800 \times 10^6 = 0.35$ m = 35 cm.

Steps

- 1) Calculate the normalized impedance for the horn $z_A = Z_A / Z_0 = (154.8 - j402) / 300 \Rightarrow \underline{z_A = 0.516 - j1.34 \Omega/\Omega}$ and plot on **Smith chart** (see Figure 6).
- 2) Draw circle, centered on Smith chart, through z_A point. This circle of constant $|\Gamma|$ includes the locus of all possible z_{in} (and y_{in}) along the transmission line with this load.
- 3) Go $\lambda/4$ (180°) around the circle of constant $|\Gamma|$ from z_A point to normalized admittance $\underline{y_A = 0.25 + j0.65 \text{ S/S}}$ point and plot.
- 4) Note, the two match points are $y_{m,i} = 1 \pm j2 \text{ S/S}$. Select match point $\underline{y_{m,1} = 1 + j2 \text{ S/S}}$ as being closest to y_A .
- 5) Find distance d_1 from y_A to $y_{m,1}$ using scales on Smith chart, $d_1 = 0.1875\lambda - 0.0946\lambda \Rightarrow \underline{d_1 = 0.0929\lambda}$ or, in centimeters, $d_1 = 0.0929(35) \Rightarrow \underline{d_1 = 3.2515 \text{ cm}}$.
- 6) For match point $y_{m,1}$, design a short circuit terminated shunt single stub with normalized susceptance $y_{\text{stub}} = -j2 \text{ S/S}$, i.e., start at the short circuit point ($y_{SC} = \infty$) move length l_1 in the "WAVELENGTHS TOWARD GENERATOR" direction to the $-j2$ point on outer edge of the Smith chart. Here, $l_1 = 0.3238\lambda - 0.25\lambda \Rightarrow \underline{l_1 = 0.0738\lambda}$ or, in centimeters, $l_1 = 0.0738(35) \Rightarrow \underline{l_1 = 2.583 \text{ cm}}$.
- 7) As shown on Figure 5, everywhere toward the source from the stub will be matched, i.e., $Y_{in} = Y_0 = 1/300 \text{ S}$ or $Z_{in} = Z_0 = 300 \Omega$.

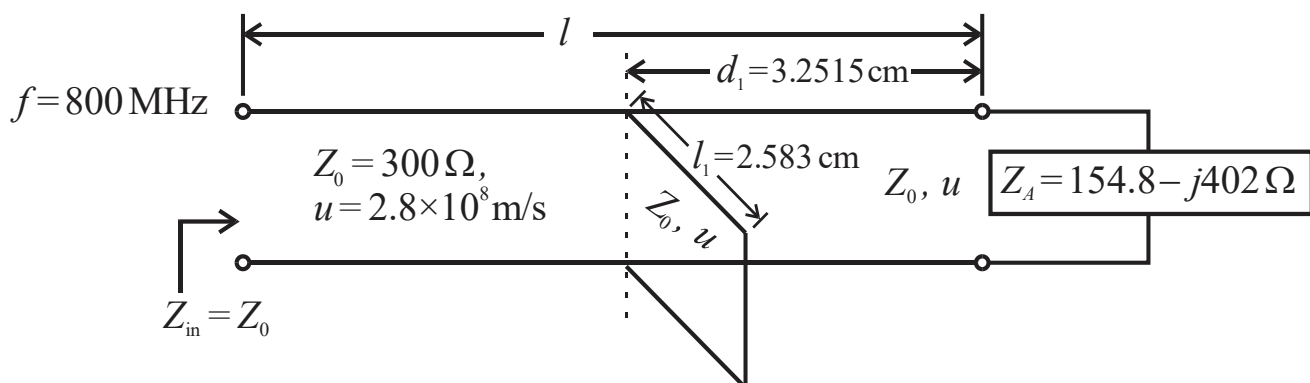


Figure 5 Matching a horn antenna using a short-circuit shunt single stub.

Simple Smith Chart

$Z_0 = 300 \Omega$
 $f = 800 \text{ MHz}$
 $\lambda = 0.35 \text{ m}$

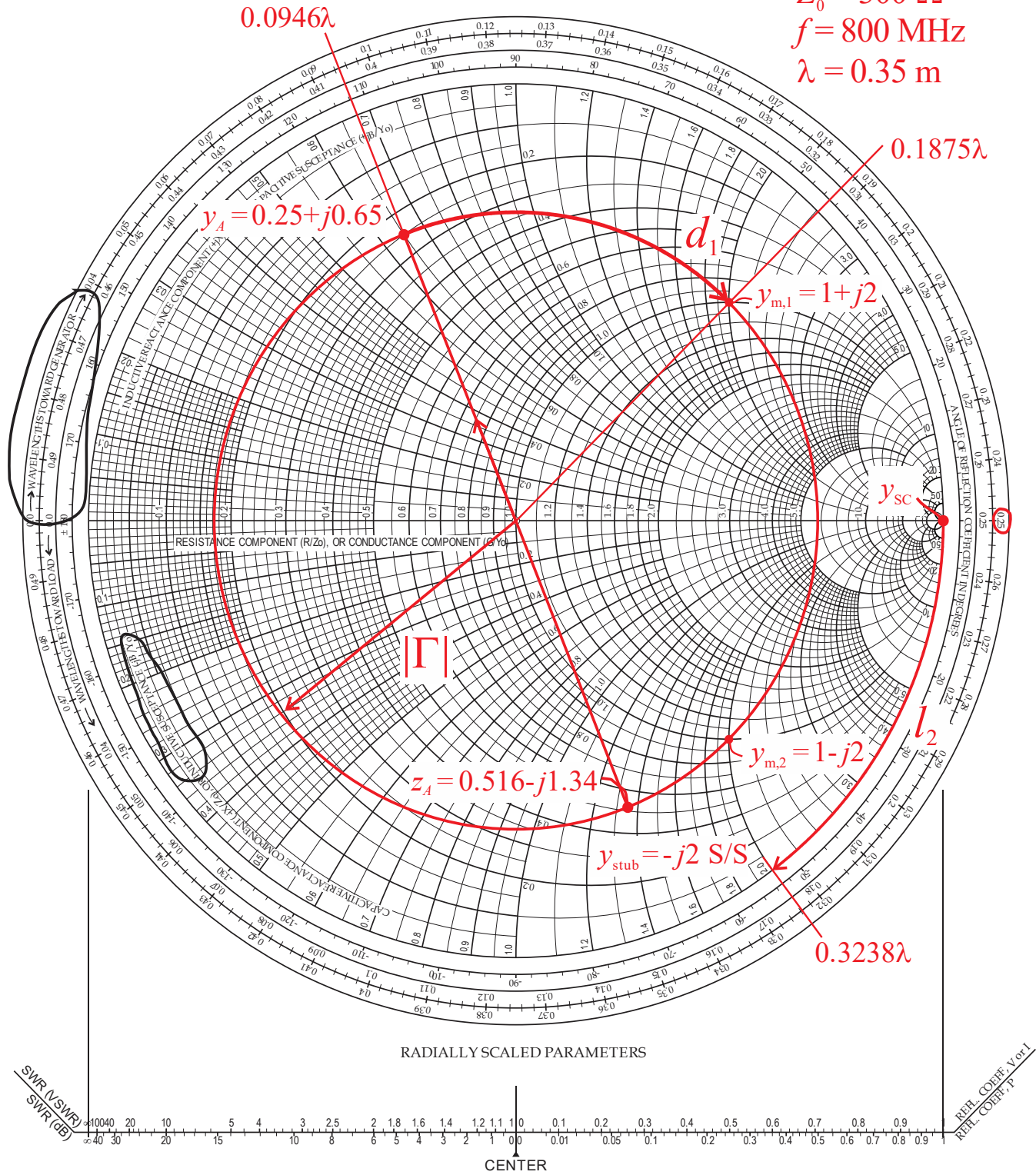


Figure 6 Smith chart for matching a horn antenna using a shunt single stub.

Example of matching an antenna using a quarter-wavelength transformer (QWT)

At 1.2 GHz, a dipole antenna has an input impedance $Z_A = 75 + j52.5 \Omega$. We wish to match it to a 50Ω planar transmission line (TL), fabricated on a printed circuit board (PCB) with a dielectric of 0.031" thickness and relative permittivity 2.2, using a planar TL QWT on the same PCB. To be able to assume that the planar TL is essentially lossless, all traces must be greater 3 mm in width. Connect the QWT as close to the dipole as possible.

- Using Table 11.1 and equations (11.21b) & (11.21c) from *Elements of Electromagnetics* (7e) by Sadiku, a lossless planar TL has a phase velocity $u = 1/(\mu\epsilon)^{0.5}$ and characteristic impedance $Z_0 = \eta d/w$ where η is the intrinsic impedance of the dielectric, d is the dielectric thickness, and w is the trace width.
- For a 50Ω planar TL on this PCB, the planar trace width is $w_{50} = \eta d/Z_0 = (376.7303/(2.2)^{0.5})0.031(25.4)/50 \Rightarrow \underline{w_{50} = 4.000 \text{ mm}}$, the phase velocity is $u = 1/(\mu_0 2.2 \epsilon_0)^{0.5} = c/(2.2)^{0.5} \Rightarrow \underline{u = 2.0212 \times 10^8 \text{ m/s}}$, and the wavelength is $\lambda = u/f = 2.0212 \times 10^8 / 1.2 \times 10^9 \Rightarrow \underline{\lambda = 0.16843 \text{ m} = 168.433 \text{ mm}}$.
- Note, u and λ do NOT depend on planar TL dimensions. Therefore, $u = u'$ and $\lambda = \lambda'$.

Steps

- 1) Calculate the normalized impedance for the dipole $z_A = Z_A/Z_0 = (75 + j52.5)/50 \Rightarrow \underline{z_A = 1.5 + j1.05 \Omega/\Omega}$ and plot on **Smith chart** (see Figure 8).
- 2) Draw circle, centered on Smith chart, through z_A point. This circle of constant $|\Gamma|$ includes the locus of all possible z_{in} (and y_{in}) along the transmission line with this load.
- 3) There are two match points on the circle where it intersects the real axis; $r_{m,1} = r_{max} = 2.5$ ($R_{max} = 2.5(50) = 125 \Omega$) and $r_{m,2} = r_{min} = 0.4$ ($R_{min} = 0.4(50) = 20 \Omega$). In order to select a match point, skip ahead to use the equation from step 5) and the above information-
 - For $R_{max} = 125 \Omega$, $Z'_{0,max} = \sqrt{Z_0 R_{max}} = \sqrt{50(125)} \Rightarrow Z'_{0,max} = 79.057 \Omega$ and $w_{max} = (376.73/(2.2)^{0.5})0.031(25.4)/79.1 \Rightarrow \underline{w_{max} = 2.530 \text{ mm}}$ (too narrow).
 - For $R_{min} = 20 \Omega$, $Z'_{0,min} = \sqrt{Z_0 R_{min}} = \sqrt{50(20)} \Rightarrow Z'_{0,min} = 31.623 \Omega$ and $w_{min} = (376.73/(2.2)^{0.5})0.031(25.4)/31.6 \Rightarrow \underline{w_{min} = 6.324 \text{ mm}}$ (OK). **Use R_{min} match point.**
- 4) Find the distance d_2 using scales on Smith chart, $d_2 = 0.5\lambda - 0.192\lambda \Rightarrow \underline{d_2 = 0.308\lambda}$ or, in millimeters, $d_2 = 0.308(168.433) \Rightarrow \underline{d_2 = 51.877 \text{ mm}}$.
- 5) Starting at d_2 , insert a QWT with a characteristic impedance $Z'_{0,min} = \sqrt{Z_0 R_{min}} = \sqrt{50(20)} \Rightarrow \underline{Z'_{0,min} = 31.623 \Omega}$, width $\underline{w_{min} = 6.324 \text{ mm}}$, and length $\lambda'/4 = 168.433/4 \Rightarrow \underline{\lambda'/4 = 42.108 \text{ mm}}$.
- 6) As shown on Fig. 7, everywhere toward the source from the QWT sees $Z_{in} = Z_0 = 50 \Omega$.

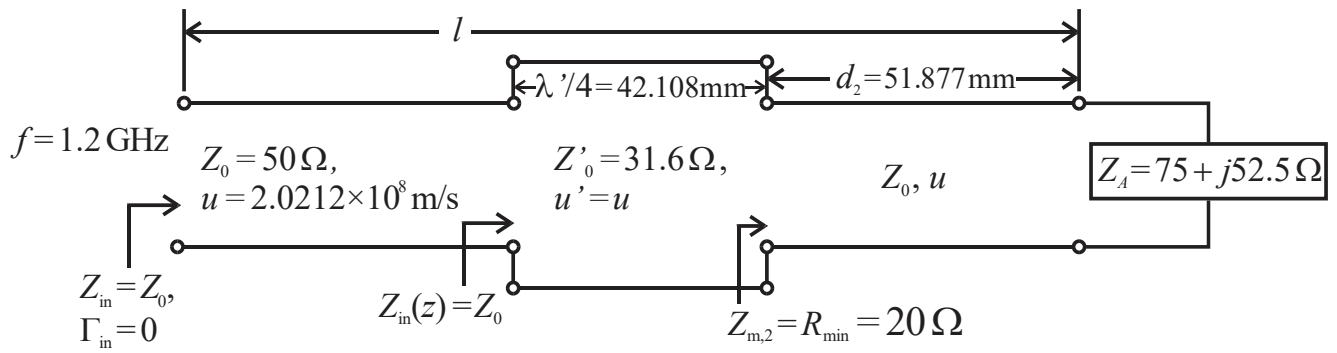


Figure 7 Matching a dipole using a QWT.

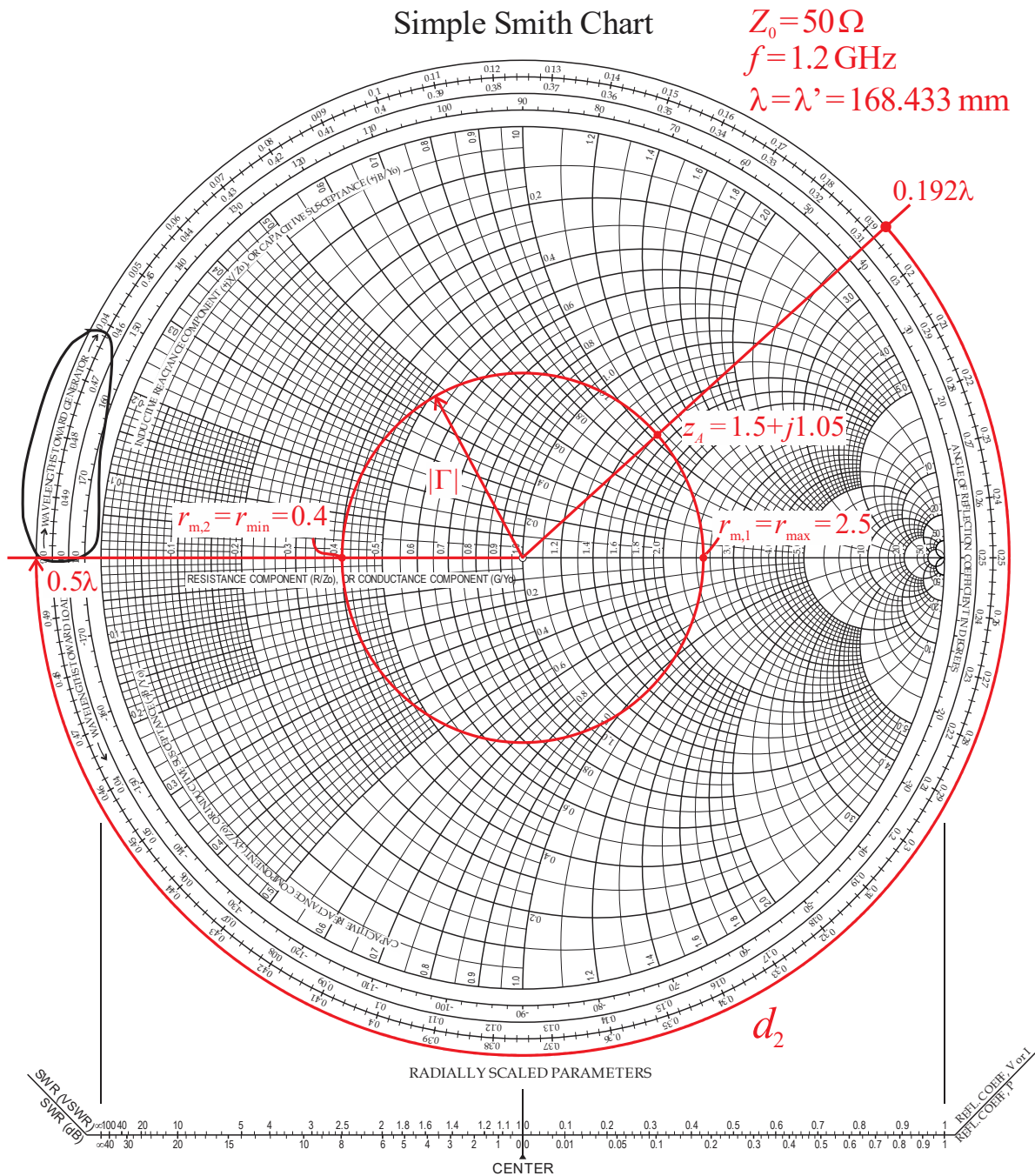


Figure 8 Smith chart for matching dipole using a QWT.