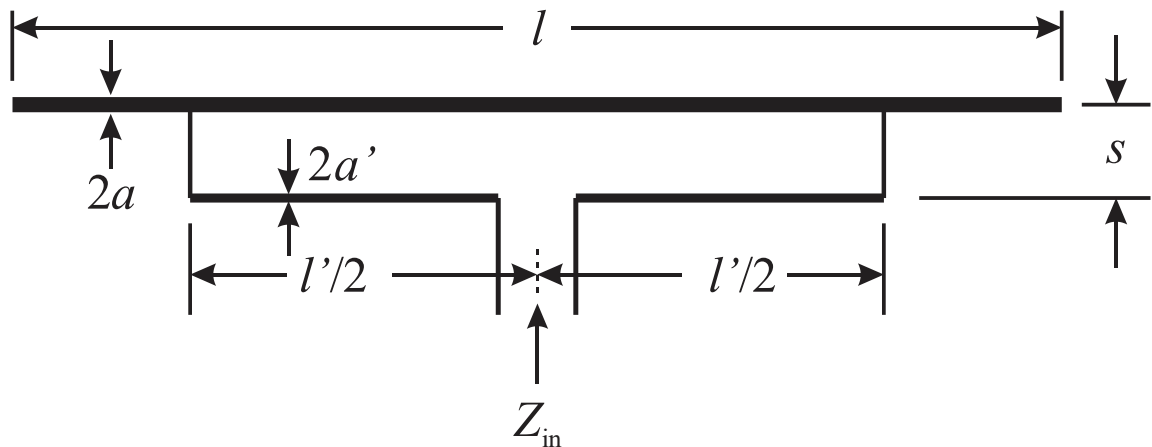


## Matching Techniques For Driving Yagi-Uda Antennas: T-Match


[Sections 9.5, 9.6, & 9.8 of *Antenna Theory, Analysis and Design* (4e) by Balanis]

### T-Match:




- The T-Match is a shunt-matching technique that can be used to feed a dipole or the **driven element** ( $l_2$ ) of a Yagi-Uda antenna. It uses a second shorter dipole that is placed a small distance  $s$  ( $s \ll \lambda$ ) from the driven element (parallel, and centered in the plane of the Yagi-Uda antenna).
- As it is symmetrical and balanced, it is typically used to connect twin-lead transmission lines to Yagi-Uda antennas.
- Design analysis and procedure follows that for the folded dipole.
- Due to mutual coupling with the reflector and director elements, the design of the T-Match is approximate. In practice, length adjustments will usually be required.
- The characteristic impedance of the transmission line portion of the T-Match is given by  $Z_0 = \frac{\eta}{2\pi} \cosh^{-1} \left( \frac{s^2 - a^2 - a'^2}{2aa'} \right)$ , where  $\eta = \sqrt{\frac{\mu}{\epsilon_{eff}}}$  is the intrinsic impedance of the material wherein the T-Match exists.

# Model:

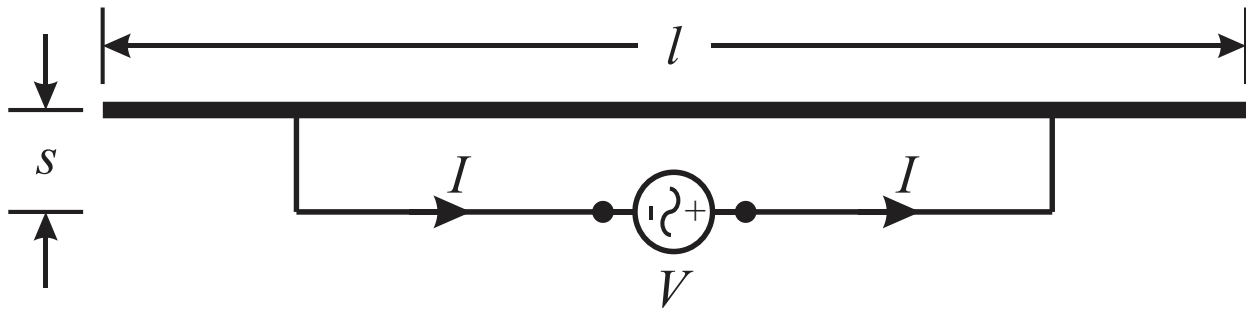


||

## Transmission line mode

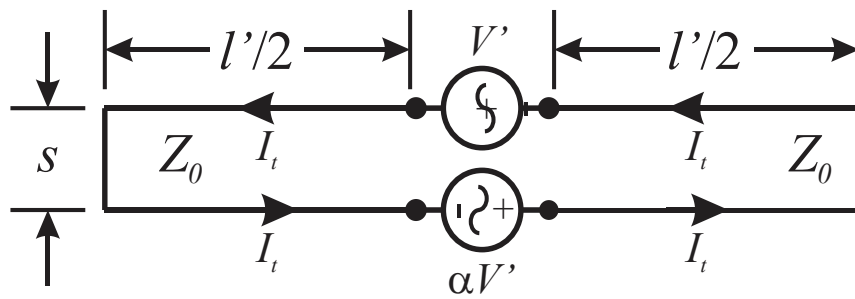


+


## Antenna mode

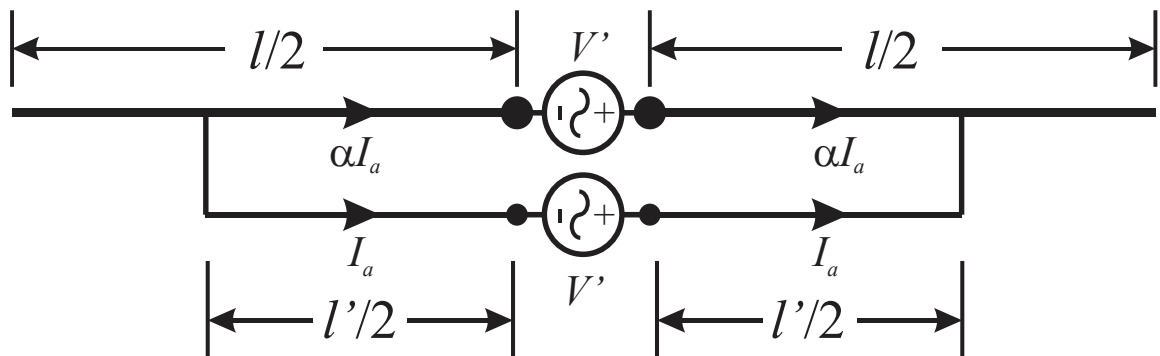

Transmission line mode

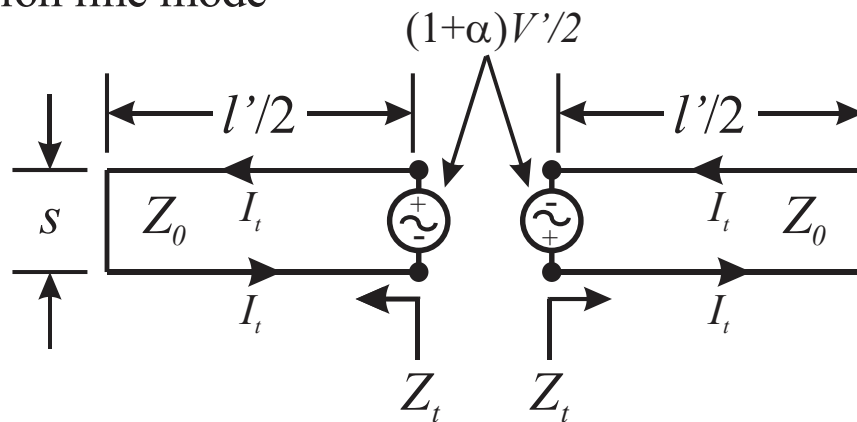

Antenna mode (symmetric about feed)

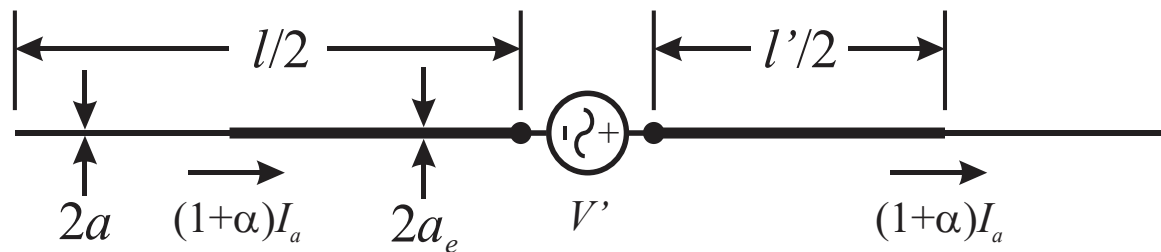

Above  $V' = \frac{V}{1+\alpha}$ , and we define a **current divisor factor**  $\alpha$ —

$$\alpha = \frac{\cosh^{-1}\left(\frac{v^2 - u^2 + 1}{2v}\right)}{\cosh^{-1}\left(\frac{v^2 + u^2 - 1}{2vu}\right)} \quad \begin{array}{l} \alpha > 1 \text{ when } a > a' \\ \alpha = 1 \text{ when } a = a' \\ \alpha < 1 \text{ when } a < a' \end{array}$$

where  $u = \frac{a}{a'}$  and  $v = \frac{s}{a'}$ . The current divisor factor  $\alpha$  has a big impact on the magnitude of  $Z_{in}$  (i.e., when  $\alpha$  increases  $|Z_{in}|$  increases and vice versa). In addition to the relationship between  $a$  and  $a'$  (above),  $\alpha$  is **inversely** related to the spacing  $s$  (i.e., if  $s$  decreases, then  $\alpha$  increases, and vice versa).

## Transmission line mode impedance

Definition of transmission line mode input impedance

$$Z_t = \frac{\left(\frac{1+\alpha}{2}\right)V'}{I_t} = jZ_0 \tan(kl'/2)$$

where  $k = \beta = 2\pi/\lambda$ .

Notes:

- For  $0 < l' < 0.5\lambda$ , we get  $Z_0 \tan(kl'/2) > 0$ , i.e., **inductive** reactance. This is nearly always the case encountered when using a T-Match with a dipole or the driven element in a Yagi-Uda antenna.
- If  $l' = 0.5\lambda$ , then  $Z_t = jZ_0 \tan(\pi/2) \rightarrow \infty$ .

## Antenna mode impedance and current

- The antenna impedance  $Z_a$  of the dipole or driven element is usually found numerically using a Method of Moments (MoM) program for a dipole that has radius  $a_e$  (the equivalent radius of the two wires) over the inner length  $l'$ , corresponding to location of T-Match, and radius  $a$  for the tips of the dipole extending beyond the T-Match. **Note:** If T-Match is used with the driven element of a Yagi-Uda antenna,  $Z_a$  should be determined with the dipole (driven element) modeled as part of the overall Yagi-Uda antenna.
- Per Table 9.3, the equivalent radius for two closely spaced (center-to-center distance  $s$ ) wires of radii  $a$  and  $a'$  is determined by-

$$\ln(a_e) \approx \ln(a') + \frac{1}{(1+u)^2} (u^2 \ln u + 2u \ln v) \quad \Rightarrow \quad \underline{a_e \approx a' e^{\frac{u^2 \ln u + 2u \ln v}{(1+u)^2}}}$$

- Definition of antenna mode input impedance-

$$Z_a = \frac{V'}{(1+\alpha)I_a}$$

## Total impedance and current for T-Match

The current at the terminals of the T-Match is

$$I = I_t + I_a = \frac{\left(\frac{1+\alpha}{2}\right)V'}{Z_t} + \frac{V'}{(1+\alpha)Z_a}$$

$$I = V' \left[ \frac{1+\alpha}{2Z_t} + \frac{1}{(1+\alpha)Z_a} \right] = \frac{V'}{1+\alpha} \left[ \frac{1+\alpha}{2Z_t} + \frac{1}{(1+\alpha)Z_a} \right]$$

$$= V' \left[ \frac{1}{2Z_t} + \frac{1}{(1+\alpha)^2 Z_a} \right] = V' \left[ \frac{(1+\alpha)^2 Z_a + 2Z_t}{2(1+\alpha)^2 Z_a Z_t} \right]$$

Solving for the input admittance and impedance, yields

$$Y_{\text{in}} = \frac{I}{V} = \frac{1}{2Z_t} + \frac{1}{(1+\alpha)^2 Z_a} \Rightarrow Y_{\text{in}} = \frac{Y_t}{2} + \frac{Y_a}{(1+\alpha)^2}$$

and

$$Z_{\text{in}} = \frac{V}{I} = \frac{1}{Y_{\text{in}}} \Rightarrow Z_{\text{in}} = \frac{2(1+\alpha)^2 Z_a Z_t}{(1+\alpha)^2 Z_a + 2Z_t}$$

For the case that  $l' \approx \lambda/2$  (half-wave dipole), the transmission line impedance  $|Z_t| \gg |Z_a|$ . Then, the input impedance becomes

$$Z_{\text{in}} \approx (1+\alpha)^2 Z_a$$

If  $a = a'$ , the current division factor  $\alpha = 1$  and we get

$$Z_{\text{in}} \approx 4Z_a$$

as was the case for the folded dipole.

Note: If  $Z_a$  has an inductive reactance (i.e.,  $X_a > 0$ ), it may not be possible to achieve a realizable match using a standard T-Match as  $Z_t$  will also have an inductive reactance. In that case, either the length  $l$  needs to be shortened to make  $Z_a$  have a capacitive reactance (i.e.,  $X_a < 0$ ) or a modified T-Match may be used.

## Design Process for T-Match in a Yagi-Uda antenna

- We desire to match a given Yagi-Uda antenna to a feeding transmission line characteristic impedance  $Z_{0,\text{feed}}$ . Typically, a specification in terms of the VSWR is given.
- 1) Select a driven element length  $l_2$  (takes the place of  $l$  used on prior pages) so that  $l_1 < l_2 < l_3$  as well as values for  $a'$ ,  $s$ , and  $l'$ . These values may be changed later.
    - Diameter of feed  $2a'$ - usually you will want this to be less than the Yagi-Uda element diameters  $2a$  to make  $\alpha > 1$ .
    - T-Match spacing  $s$ - make less than  $s_{12}/4$ , more than 1 cm (practical construction), and less than 5 cm (don't want the characteristic impedance  $Z_0$  of the T-Match section to be too large).
    - T-Match length  $l'$ - make less than half of the initial driven element length  $l_2$ , i.e.,  $l' \leq l_2/2$ , to avoid overly disturbing the current distribution on  $l_2$ .
  - 2) Calculate the characteristic impedance  $Z_0$  of the transmission line portion of the T-Match-

$$Z_0 = \frac{\eta}{2\pi} \cosh^{-1} \left( \frac{s^2 - a^2 - a'^2}{2aa'} \right)$$

where  $\eta = \sqrt{\frac{\mu}{\epsilon_{\text{eff}}}}$  is the intrinsic impedance of the material wherein the T-Match exists.

- 3) Calculate the transmission line mode input impedance  $Z_t$ -

$$Z_t = jZ_0 \tan(kl'/2) \text{ where } k = \beta = 2\pi/\lambda.$$

- 4) Calculate the parameters  $u$ ,  $v$ , and  $\alpha$ -

$$u = \frac{a}{a'}, \quad v = \frac{s}{a'}, \quad \text{and } \alpha = \frac{\cosh^{-1} \left( \frac{v^2 - u^2 + 1}{2v} \right)}{\cosh^{-1} \left( \frac{v^2 + u^2 - 1}{2vu} \right)} \begin{array}{l} \alpha > 1 \text{ when } a > a' \\ \alpha = 1 \text{ when } a = a'. \\ \alpha < 1 \text{ when } a < a' \end{array}$$

- 5) Calculate the equivalent radius  $a_e$  for the section of the driven element corresponding to the T-Match-

$$a_e \approx a' e^{\frac{u^2 \ln u + 2u \ln v}{(1+u)^2}}.$$

- 6) Find the input impedance (i.e., use NEC-2) of the antenna mode  $Z_a$  of the driven element as part of the Yagi-Uda antenna. It is modeled as a dipole that has radius  $a_e$  over the inner length  $l'$ , corresponding to location of T-Match, and radius  $a$  for the tips extending beyond the T-Match.

- 7) Find the overall input impedance -

$$Z_{in} = \frac{2(1 + \alpha)^2 Z_a Z_t}{(1 + \alpha)^2 Z_a + 2Z_t}.$$

- 8) Determine if  $Z_{in}$  meets your specification. If so, stop design process. If not, consider/try:

➤ If  $Z_{in}$  and  $Z_a$  have inductive reactances (i.e.,  $X > 0$ ), it may be necessary to **shorten**  $l_2$  to make  $Z_a$  have a smaller inductive reactance or capacitive reactance (i.e.,  $X_a < 0$ ) to achieve an acceptable  $Z_{in}$ .

➤ Consider changing  $l'$  toward the length suggested by

$$l' = \frac{2}{k} \tan^{-1} \left[ \frac{1}{2Z_0 \operatorname{Im} \left( \frac{Y_a}{(1 + \alpha)^2} \right)} \right]$$

to better offset the antenna mode reactance, and repeat steps 2) through 8). If necessary,  $l_2$ ,  $a'$ , and  $s$  can be varied.

➤ Remember, the magnitude of the input impedance  $|Z_{in}|$  is greatly affected by  $\alpha$  (i.e., when  $\alpha$  increases,  $|Z_{in}|$  increases, and vice versa). In turn,  $\alpha$  is inversely related to  $s$  (i.e., if  $s$  decreases,  $\alpha$  increases, and vice versa).

➤ See [http://montoya.sdsmt.edu/ee483\\_583/notes/matching\\_tips.pdf](http://montoya.sdsmt.edu/ee483_583/notes/matching_tips.pdf) for further tips.