

EE 483/583 Antennas for Wireless Communications (Spring 2022)

Homework 9

Wednesday, March 23, 2022

- 1) Match the channel 10 six-element Yagi-Uda antenna from the previous assignment with the boom omitted to a 100Ω twin-lead transmission line using a **T-match** so that the VSWR is less than 1.1 at the center frequency. At each step, discuss and justify design changes/choices. Accurately sketch final design. In a table, summarize the original (unmatched) and final Yagi-Uda input impedance, input reflection coefficient (polar format), VSWR, gain (dBi), and front-to-back ratio (dB). Comment on how the final design compares with the original.
 - Use NEC-2 to find the antenna-mode input impedance(s). Include the input file(s) and relevant excerpts of the output file(s). Assume $c = 2.998 \times 10^8$ m/s.
- 2) An antenna has input impedance $Z_A = 37.5 - j 75 \Omega$ at 100 MHz. Match it to a feeding transmission line ($Z_0 = 75 \Omega$ & $u = 2.25 \times 10^8$ m/s) using a discrete inductor connected in parallel as close to the antenna as possible. Draw a fully labeled sketch of the final design.
- 3) An antenna has input impedance $Z_A = 37.5 - j 75 \Omega$ at 100 MHz. Match it to a feeding transmission line ($Z_0 = 75 \Omega$ & $u = 2.25 \times 10^8$ m/s) using a stub of the same transmission line with a short-circuit termination. Place the stub as close to the antenna as possible and make the stub as short as possible. Draw a fully labeled sketch of the final design.
- 4) An antenna has input impedance $Z_A = 50 - j 45 \Omega$ at 1 GHz. Match it to a feeding transmission line ($Z_0 = 50 \Omega$ & $u = 2.1 \times 10^8$ m/s) using a quarterwave transformer (QWT) placed as close to the antenna as possible. Assume the wavelength λ' of the QWT is 92% of λ for the feeding transmission line. Draw a fully labeled sketch of the final design.
- 5) EE 583 only: For the match of problem 2, analytically find the input impedance Z_{in} , reflection coefficient Γ , and VSWR at 95, 100, & 105 MHz on the feeding transmission just past the inductor toward the generator assuming Z_A remains constant. Tabulate results- col. 1 frequency, col. 2 Z_{in} (rectangular format), col. 3 Γ (polar format), and col. 4 VSWR.

Due Monday, March 28, 2022.

Notes:

- For each problem using a Smith chart, include a *separate, fully labeled* one.