

EE 483/583 Antennas for Wireless Communications Quiz #8 (Spring 2024)

Name KEY

Instructions: Open book and notes. Place answers in indicated spaces and **show & explain all work** for credit.

Match a Yagi-Uda antenna ($Z_A = 12.5 + j37.5 \Omega$) operating at 600 MHz to a 75Ω feeding transmission line ($u = 2.4 \times 10^8$ m/s) using a discrete inductor connected in **parallel** and placed as close to the antenna as possible. As part of the solution process, find the normalized antenna admittance y_A and impedance z_A , normalized match point admittances (circle match point used), wavelength λ on transmission line, distance d from the antenna to the match point (x.xxx λ & cm), inductor admittance Y_L (not normalized), and inductor value L . **Fully label** the Smith chart and draw a fully-labeled sketch of the final design in box provided [**all dimensions in cm**].

➤ The wavelength is $\lambda = u/f = 2.4 \times 10^8 / 600 \times 10^6 = 0.4$ m \Rightarrow $\lambda = 40$ cm.

Steps

- 1) Calculate normalized impedance $z_A = Z_A / Z_0 = (12.5 + j37.5) / 75 \Rightarrow$ $z_A = 0.167 + j0.5 \Omega/\Omega$ and plot on **Smith chart**.
- 2) Draw circle, centered on Smith chart, through z_A point. This circle of constant $|\Gamma|$ includes the locus of all possible z_{in} (and y_{in}) along the transmission line with this load.
- 3) Go $\lambda/4$ (180°) around the circle of constant $|\Gamma|$ from z_A point to $y_A = 1/z_A = 1/(0.167 + j0.5)$ point and plot \Rightarrow $y_A = 0.6 - j1.8$ S/S.
- 4) Note, the two match points are $y_{m,i} = 1 \pm j2.4$ S/S. In order to use a discrete inductor for matching, select $y_{m1} = 1 + j2.4$ S/S as it has a capacitive susceptance. Note, $Y_{m1} = y_{m1} / Z_0 = (1 + j2.4) / 75 = 0.01333 + j0.032$ S.
- 5) Find distance d_1 from y_A to y_{m1} using scales on Smith chart, $d_1/\lambda = 0.1746 + 0.1947 = 0.3693$ or, in centimeters, $d_1 = 0.3693(40) \Rightarrow$ $d_1 = 14.772$ cm.
- 6) At d_1 , add a discrete inductor in parallel with susceptance $Y_L = -j0.032$ S $= -j/\omega L$. Solving for L yields $L = 1/[2\pi 600 \times 10^6 (0.032)] = 8.28932 \times 10^{-9}$ H \Rightarrow $L = 8.29$ nH.
- 7) As shown on circuit, everywhere toward the source from the location of L will be matched, i.e., $Z_{in} = Z_0 = 75 \Omega$.

$$z_A = \underline{0.167 + j0.5 \Omega/\Omega}$$

$$y_A = \underline{0.6 - j1.8 \text{ S/S}}$$

$$y_{m1} = \underline{1 + j2.4 \text{ S/S}}$$


$$y_{m2} = \underline{1 - j2.4 \text{ S/S}}$$

$$\lambda = \underline{40 \text{ cm}}$$

$$d = \underline{d_1 = 0.3693\lambda = 14.772 \text{ cm}}$$

$$Y_L = \underline{-j0.032 \text{ S}}$$

$$L = \underline{8.29 \text{ nH}}$$

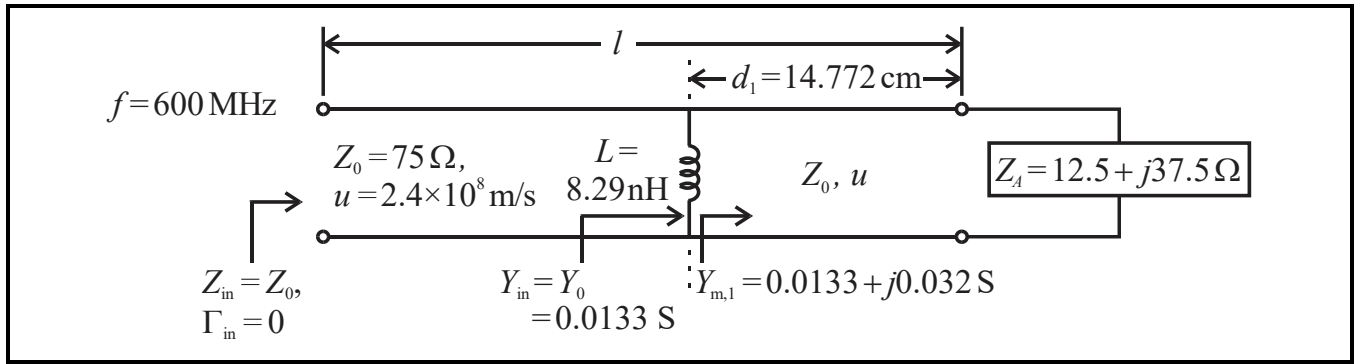

Simple Smith Chart

