

3.3 cont.

What about stability for unilateral ($S_{12} = 0$) two-port networks?

Here, $\Gamma_{IN} = S_{11}$ & $\Gamma_{OUT} = S_{22}$

and $K \rightarrow \infty$ & $\Delta = S_{11}S_{22}$

which leads to the requirement that

$|S_{11}| < 1$ and $|S_{22}| < 1$ for

a unilateral two-port to be unconditionally stable

What if Γ_L and/or Γ_S selection results in $|\Gamma_{IN}| > 1$ (Z_{in} has negative resistance) and/or $|\Gamma_{OUT}| > 1$ (Z_{out} has negative resistance)?

We can still achieve an unconditionally stable two-port by resistively loading the input and/or output to make $\text{Re}(Z_{in}) > 0$ and/or $\text{Re}(Z_{out}) > 0$.

Cost? Lower gain
Lower efficiency
worse noise figure
worse VSWR

Not acceptable for
Narrowband designs,
may be acceptable
for broadband
applications

3.4 Constant-Gain Circles : Unilateral Case 20

Unilateral means $S_{12} \approx 0$, $\Gamma_{in} = S_{11}$, & $\Gamma_{out} = S_{22}$.

Then, the transducer power gain G_T becomes

$$G_{Tu} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$


$$= G_S G_0 G_L$$

$\uparrow \quad \quad \quad \nwarrow \quad \quad \quad \nearrow$
 $G_S \quad G_0 \quad G_L$

$G_S \sim$ gain/loss of input matching network

$G_0 \sim$ gain of transistor

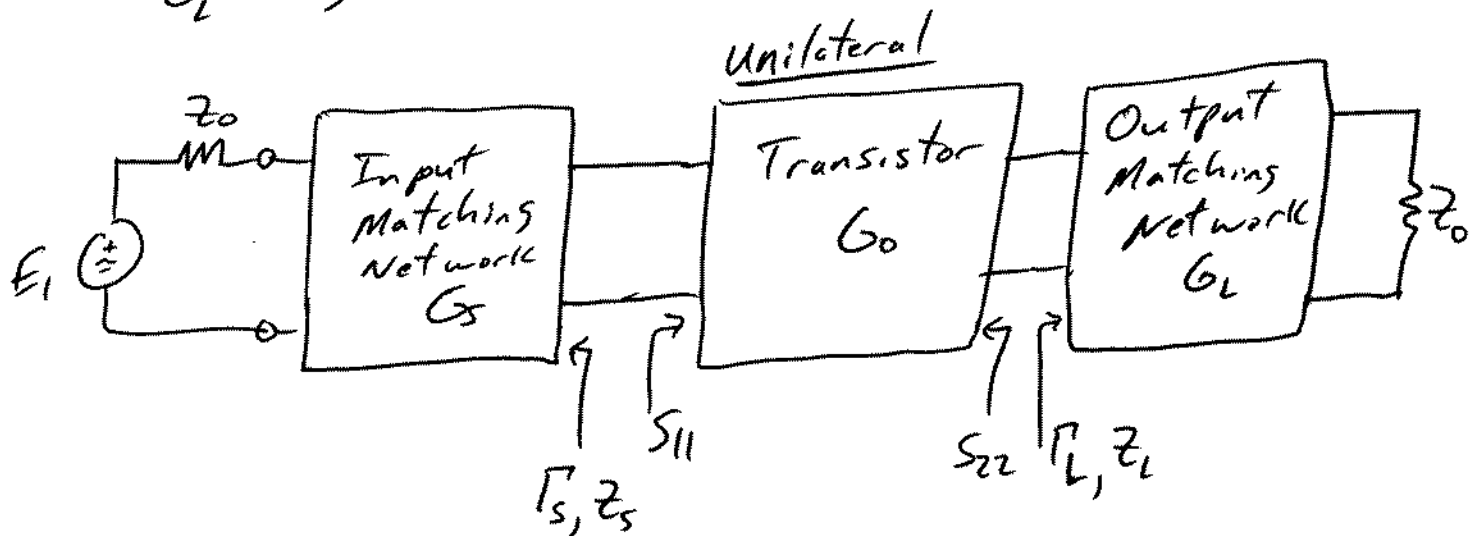$G_L \sim$ gain/loss of output matching network



In decibels

$$G_{Tu}(\text{dB}) = G_S(\text{dB}) + G_0(\text{dB}) + G_L(\text{dB})$$

3.4 cont.

21

Maximum transducer power gain $G_{TU, \max}$ for $|S_{11}| < 1$ + $|S_{22}| < 1$ occurs when

$$\Gamma_S = S_{11}^* \text{ and } \Gamma_L = S_{22}^*$$

$$\hookrightarrow G_{S, \max} = \frac{1}{1 - |S_{11}|^2}$$


$$G_{L, \max} = \frac{1}{1 - |S_{22}|^2}$$

and

$$\begin{aligned} G_{TU, \max} &= G_{S, \max} G_0 G_{L, \max} \\ &= \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2} \end{aligned}$$

Further, since $\Gamma_S = S_{11}^* = \Gamma_{IN}^*$ and $\Gamma_L = S_{22}^* = \Gamma_{OUT}^*$ for the unilateral case
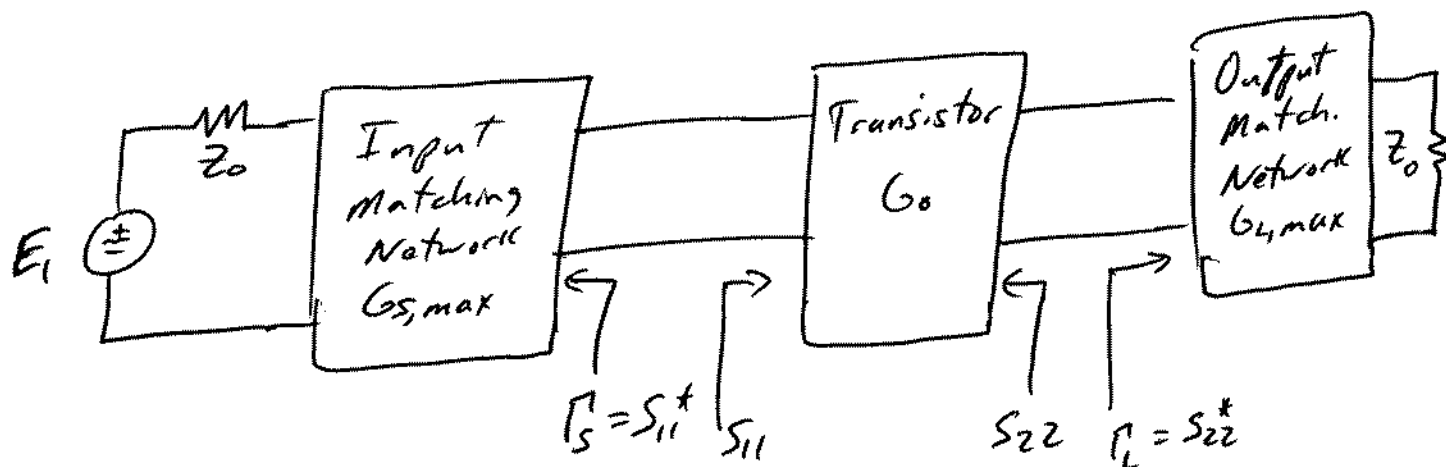
$$G_{TU, \max} = G_{PU, \max} = G_{AU, \max}$$



3.4 cont.

Unconditionally Stable Case, $|S_{ii}| < 1$

Let's consider $G_i = \frac{1 - |\Gamma_i|^2}{|1 - S_{ii}\Gamma_i|^2}$

where $i = S$ w/ $i i = 11$ (Input Matching network)
 $i = L$ w/ $i i = 22$ (Output Matching network)

We have seen that $G_{i,max} = \frac{1}{1 - |S_{ii}|^2}$

when $\Gamma_i = S_{ii}^*$ (optimum termination).

$G_{i,min} = 0$ when $|\Gamma_i| = 1$ (everything reflected,
 on outside edge of Smith Chrt)

Therefore, $0 \leq G_i \leq G_{i,max}$

Now, in an actual design, achieving $\Gamma_i = S_{ii}^*$ might be difficult or undesirable for another reason.

Therefore, it is of great interest to know the values of Γ_i which result in constant values of G_i (less than $G_{i,max}$) & it turns out that these Γ_i fall on circles on the Smith Chart, e.g., constant G_S circles about S_{11}^* and constant G_L circles about S_{22}^*

3.4 cont.

23

$$\begin{aligned} \text{Normalized gain factor} \equiv g_i &= \frac{G_i}{G_{i,\max}} = G_i (1 - |S_{ii}|^2) \\ &= \frac{1 - |\Gamma_i|^2}{|1 - S_{ii}\Gamma_i|^2} (1 - |S_{ii}|^2) \end{aligned}$$

where $0 \leq g_i \leq 1$.

The constant g_i circle equation is

$$|\Gamma_i - C_{g_i}| = r_{g_i}$$

where

$$\text{Circle center} \equiv C_{g_i} = \frac{g_i S_{ii}^*}{1 - |S_{ii}|^2 (1 - g_i)} \quad \text{or complex \# on } \Gamma_i \text{ plane}$$

$$\text{Circle radius} \equiv r_{g_i} = \frac{\sqrt{1 - g_i} (1 - |S_{ii}|^2)}{1 - |S_{ii}|^2 (1 - g_i)}$$

$$\text{Note: } \angle C_{g_i} = \angle S_{ii}^*$$

$$\text{Note: } G_i = 1 = 0\text{dB} \quad \text{or} \quad g_{i,0\text{dB}} = 1 - |S_{ii}|^2$$

circle always passes thru $\Gamma_i = 0$
(center of Smith Chart)

$$\text{and } r_{g_{i,0\text{dB}}} = |C_{g_{i,0\text{dB}}}| = \frac{|S_{ii}|}{1 + |S_{ii}|^2}$$

Typical Procedure for drawing G_i circles on an impedance Smith Chart

- 1) Plot S_{ii}^* on Smith Chart and calculate

$$G_{i,\max} = \frac{1}{1-|S_{ii}|^2} \quad G_{i,\max}(\text{dB}) = 10 \log_{10} G_{i,\max}$$

- 2) Select values of $G_i^{\#}$ in the range $0 \leq G_i \leq G_{i,\max}$ where you wish to draw circles of Γ_i which result in constant G_i . Then, calculate corresponding normalized gains $g_i = \frac{G_i}{G_{i,\max}}$.

- 3) Calculate $C_{g_i} = \frac{g_i S_{ii}^*}{1-|S_{ii}|^2(1-g_i)}$

for each g_i

- 4) Calculate $r_{g_i} = \frac{\sqrt{1-g_i} (1-|S_{ii}|^2)}{1-|S_{ii}|^2(1-g_i)}$

for each g_i

- 5) Plot circles on Smith Chart(s)

† Note: $G_i(\text{dB}) = 10 \log_{10} G_i$

So $G_i = 10^{\frac{G_i(\text{dB})}{10}}$

Example- Let's base our unilateral constant gain circles example on an Advanced Semiconductor, Inc. MLN2037F NPN silicon RF power transistor operating at 1 GHz.

Using the datasheet, the S parameters at 1 GHz are:

$$S_{11} = 0.8128 \angle 156^\circ, \quad S_{12} \approx 0 \text{ (assumed)}$$

$$S_{21} = 1.81 \angle 55^\circ, \quad S_{22} = 0.3801 \angle -136^\circ$$

Input Matching Network- circles of constant G_s on Γ_s Smith Chart

1) Plot $S_{11}^* = 0.8128 \angle -156^\circ$ on Γ_s Smith Chart (see following page) where

$$G_{s,\max} = \frac{1}{1 - |S_{11}|^2} = \frac{1}{1 - 0.8128^2}$$

$$= 2.9467566 = 4.6934 \text{ dB}$$

2) Let's plot $G_s = 3, 2, 1, 0$, and -1 dB. To simplify the process, use MathCad (see following pages) to compute the corresponding G_s and g_s . The results are summarized in Table 1.

3) Calculate corresponding C_{g_s} using MathCad. The results are summarized in Table 1.


4) Calculate corresponding r_{g_s} using MathCad. The results are summarized in Table 1.

Table 1 Circles of constant G_s information

G_s (dB)	3	2	1	0	-1
G_s	1.9953	1.5849	1.2589	1	0.7943
g_s	0.6771	0.53784	0.42722	0.33936	0.26956
$ C_{g_s} $	0.6996	0.6293	0.5586	0.4894	0.4234
$\angle C_{g_s}$	-156°	-156°	-156°	-156°	-156°
r_{g_s}	0.24513	0.3321	0.41318	0.48945	0.56052

5) Plot Γ_s circles for constant G_s (dB) on Smith Chart (used CorelDraw).

Γ_s Smith Chart

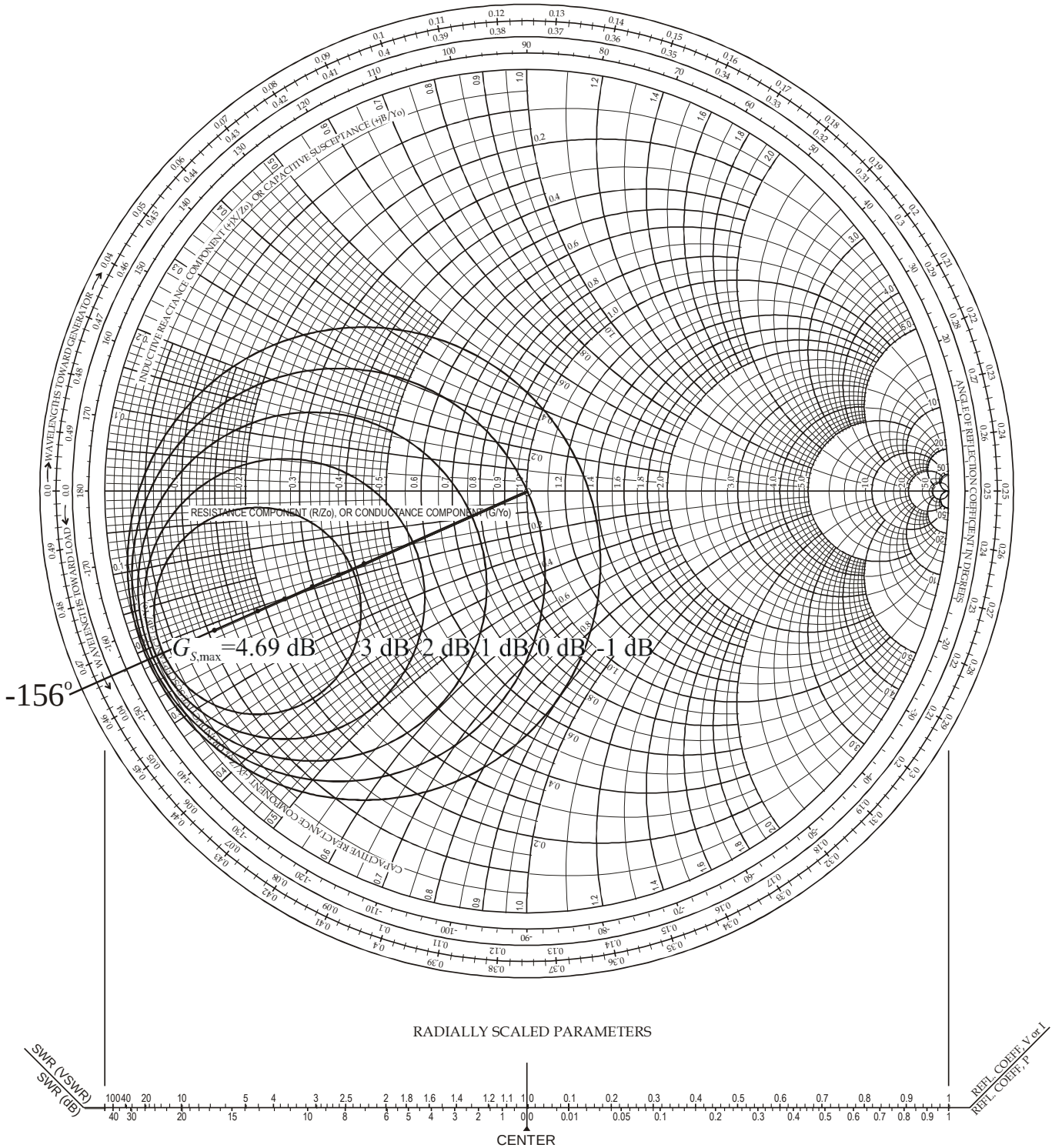

Output Matching Network- circles of constant G_L on Γ_L Smith Chart

1) Plot $S_{22}^* = 0.3801 \angle 136^\circ$ on Γ_S Smith Chart (see following page) where

$$G_{L,\max} = \frac{1}{1 - |S_{22}|^2} = \frac{1}{1 - 0.3801^2}$$

$$= 1.16887 = 0.67768 \text{ dB}$$

2) Let's plot $G_L = 0, -1, -2, \text{ and } -3 \text{ dB}$. To simplify the process, use MathCad (see following pages) to compute the corresponding G_L and g_L . The results are summarized in Table 2.

3) Calculate corresponding C_{g_L} using MathCad. The results are summarized in Table 2.


4) Calculate corresponding r_{g_L} using MathCad. The results are summarized in Table 2.

Table 2 Circles of constant G_L information

G_L (dB)	0	-1	-2	-3
G_L	1	0.7943	0.631	0.5012
g_L	0.85552	0.67957	0.5398	0.4288
$ C_{g_L} $	0.33212	0.2708	0.2198	0.1776
$\angle C_{g_L}$	136°	136°	136°	136°
r_{g_L}	0.33212	0.50779	0.62171	0.70476

5) Plot Γ_L circles for constant G_L (dB) on Smith Chart (used CorelDraw).

Γ_L Smith Chart

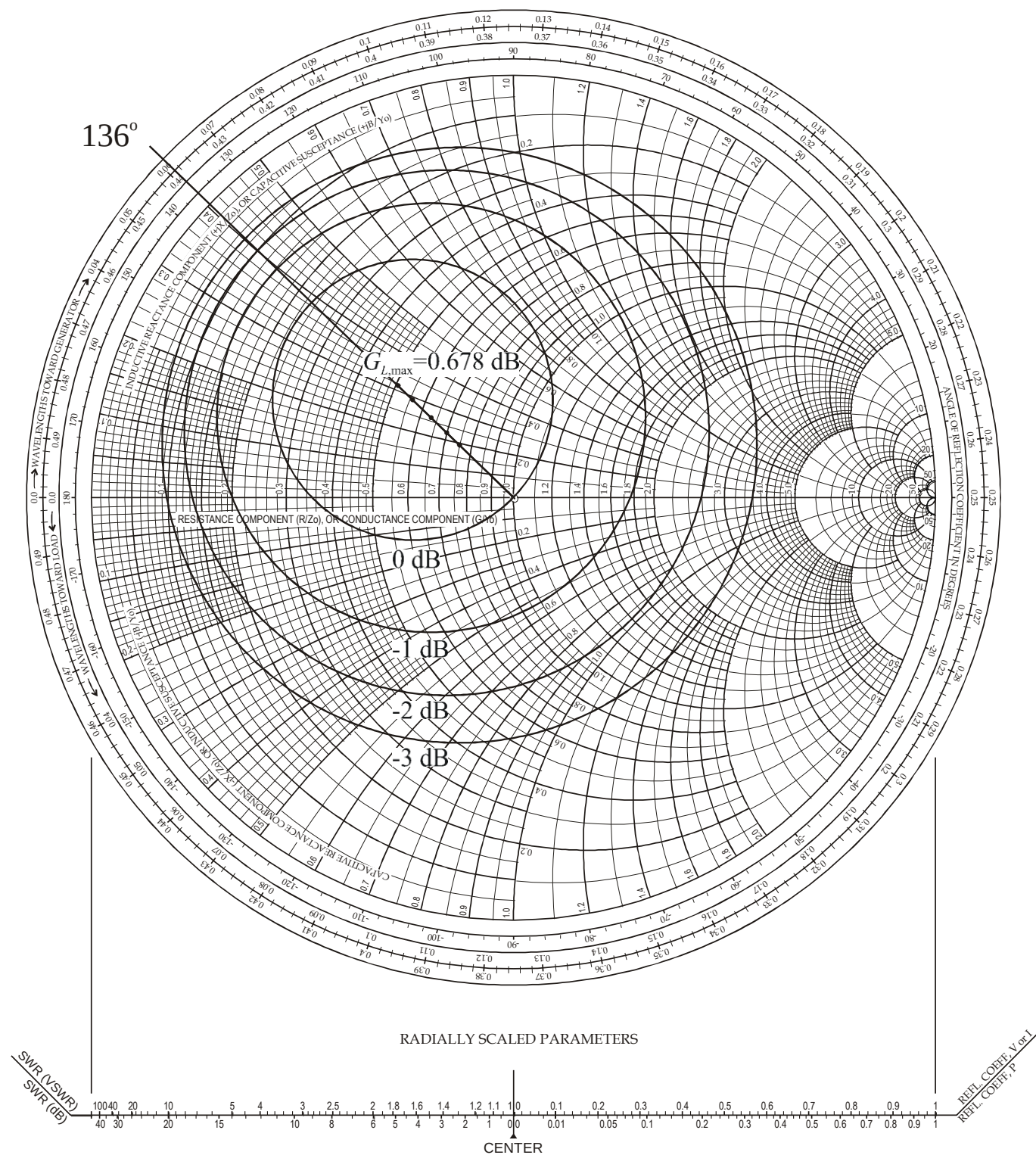

Unilateral gain circles example for MLN2037F at 1 GHz

$$S_{11} := 0.8128 \cdot e^{j \cdot 156 \cdot \frac{\pi}{180}} \quad S_{12} := 0$$

$$S_{21} := 1.81 \cdot e^{j \cdot 55 \cdot \frac{\pi}{180}} \quad S_{22} := 0.3801 \cdot e^{j \cdot -136 \cdot \frac{\pi}{180}}$$

First, calculate GS circle information

$$GS_{\max} := \frac{1}{1 - (|S_{11}|)^2} \quad GS_{\max dB} := 10 \cdot \log(GS_{\max}) \quad GS_{\max} = 2.94676$$

$$GS_{\max dB} = 4.69344 \text{ dB}$$

$$GS_{3dB} := 10^{\frac{3}{10}} \quad GS_{3dB} = 1.9953 \quad gS_{3dB} := \frac{GS_{3dB}}{GS_{\max}} \quad gS_{3dB} = 0.6771$$

$$GS_{2dB} := 10^{\frac{2}{10}} \quad GS_{2dB} = 1.5849 \quad gS_{2dB} := \frac{GS_{2dB}}{GS_{\max}} \quad gS_{2dB} = 0.53784$$

$$GS_{1dB} := 10^{\frac{1}{10}} \quad GS_{1dB} = 1.2589 \quad gS_{1dB} := \frac{GS_{1dB}}{GS_{\max}} \quad gS_{1dB} = 0.42722$$

$$GS_{0dB} := 10^{\frac{0}{10}} \quad GS_{0dB} = 1 \quad gS_{0dB} := \frac{GS_{0dB}}{GS_{\max}} \quad gS_{0dB} = 0.33936$$

$$GS_{-1dB} := 10^{\frac{-1}{10}} \quad GS_{-1dB} = 0.7943 \quad gS_{-1dB} := \frac{GS_{-1dB}}{GS_{\max}} \quad gS_{-1dB} = 0.26956$$

$$CgS3dB := \frac{gS_3dB \cdot \overline{S11}}{1 - (|S11|)^2 \cdot (1 - gS_3dB)}$$

$$rgS3dB := \frac{\sqrt{1 - gS_3dB} \cdot [1 - (|S11|)^2]}{1 - (|S11|)^2 \cdot (1 - gS_3dB)}$$

$$|CgS3dB| = 0.6996$$

$$\arg(CgS3dB) \cdot \frac{180}{\pi} = -156$$

$$rgS3dB = 0.24513$$

$$CgS2dB := \frac{gS_2dB \cdot \overline{S11}}{1 - (|S11|)^2 \cdot (1 - gS_2dB)}$$

$$rgS2dB := \frac{\sqrt{1 - gS_2dB} \cdot [1 - (|S11|)^2]}{1 - (|S11|)^2 \cdot (1 - gS_2dB)}$$

$$|CgS2dB| = 0.6293$$

$$\arg(CgS2dB) \cdot \frac{180}{\pi} = -156$$

$$rgS2dB = 0.3321$$

$$CgS1dB := \frac{gS_1dB \cdot \overline{S11}}{1 - (|S11|)^2 \cdot (1 - gS_1dB)}$$

$$rgS1dB := \frac{\sqrt{1 - gS_1dB} \cdot [1 - (|S11|)^2]}{1 - (|S11|)^2 \cdot (1 - gS_1dB)}$$

$$|CgS1dB| = 0.5586$$

$$\arg(CgS1dB) \cdot \frac{180}{\pi} = -156$$

$$rgS1dB = 0.41318$$

$$CgS0dB := \frac{gS_0dB \cdot \overline{S11}}{1 - (|S11|)^2 \cdot (1 - gS_0dB)}$$

$$rgS0dB := \frac{\sqrt{1 - gS_0dB} \cdot [1 - (|S11|)^2]}{1 - (|S11|)^2 \cdot (1 - gS_0dB)}$$

$$|CgS0dB| = 0.4894$$

$$\arg(CgS0dB) \cdot \frac{180}{\pi} = -156$$

$$rgS0dB = 0.48945$$

$$CgSm1dB := \frac{gS_m1dB \cdot \overline{S11}}{1 - (|S11|)^2 \cdot (1 - gS_m1dB)}$$

$$rgSm1dB := \frac{\sqrt{1 - gS_m1dB} \cdot [1 - (|S11|)^2]}{1 - (|S11|)^2 \cdot (1 - gS_m1dB)}$$

$$|CgSm1dB| = 0.4234$$

$$\arg(CgSm1dB) \cdot \frac{180}{\pi} = -156$$

$$rgSm1dB = 0.56052$$

Next, calculate GL circle information

$$GL_{\max} := \frac{1}{1 - (|S_{22}|)^2} \quad GL_{\max dB} := 10 \cdot \log(GL_{\max}) \quad GL_{\max} = 1.16887$$

$$GL_{\max dB} = 0.67768 \text{ dB}$$

$$GL_{0dB} := 10^{\frac{0}{10}} \quad GL_{0dB} = 1 \quad gL_{0dB} := \frac{GL_{0dB}}{GL_{\max}} \quad gL_{0dB} = 0.85552$$

$$GL_{m1dB} := 10^{\frac{-1}{10}} \quad GL_{m1dB} = 0.7943 \quad gL_{m1dB} := \frac{GL_{m1dB}}{GL_{\max}} \quad gL_{m1dB} = 0.67957$$

$$GL_{m2dB} := 10^{\frac{-2}{10}} \quad GL_{m2dB} = 0.631 \quad gL_{m2dB} := \frac{GL_{m2dB}}{GL_{\max}} \quad gL_{m2dB} = 0.5398$$

$$GL_{m3dB} := 10^{\frac{-3}{10}} \quad GL_{m3dB} = 0.5012 \quad gL_{m3dB} := \frac{GL_{m3dB}}{GL_{\max}} \quad gL_{m3dB} = 0.4288$$

$$CgL0dB := \frac{gL_0dB \cdot \overline{S22}}{1 - (|S22|)^2 \cdot (1 - gL_0dB)}$$

$$rgL0dB := \frac{\sqrt{1 - gL_0dB} \cdot [1 - (|S22|)^2]}{1 - (|S22|)^2 \cdot (1 - gL_0dB)}$$

$$|CgL0dB| = 0.3321$$

$$\arg(CgL0dB) \cdot \frac{180}{\pi} = 136$$

$$rgL0dB = 0.33212$$

$$CgLm1dB := \frac{gL_m1dB \cdot \overline{S22}}{1 - (|S22|)^2 \cdot (1 - gL_m1dB)}$$

$$rgLm1dB := \frac{\sqrt{1 - gL_m1dB} \cdot [1 - (|S22|)^2]}{1 - (|S22|)^2 \cdot (1 - gL_m1dB)}$$

$$|CgLm1dB| = 0.2708$$

$$\arg(CgLm1dB) \cdot \frac{180}{\pi} = 136$$

$$rgLm1dB = 0.50779$$

$$CgLm2dB := \frac{gL_m2dB \cdot \overline{S22}}{1 - (|S22|)^2 \cdot (1 - gL_m2dB)}$$

$$rgLm2dB := \frac{\sqrt{1 - gL_m2dB} \cdot [1 - (|S22|)^2]}{1 - (|S22|)^2 \cdot (1 - gL_m2dB)}$$

$$|CgLm2dB| = 0.2198$$

$$\arg(CgLm2dB) \cdot \frac{180}{\pi} = 136$$

$$rgLm2dB = 0.62171$$

$$CgLm3dB := \frac{gL_m3dB \cdot \overline{S22}}{1 - (|S22|)^2 \cdot (1 - gL_m3dB)}$$

$$rgLm3dB := \frac{\sqrt{1 - gL_m3dB} \cdot [1 - (|S22|)^2]}{1 - (|S22|)^2 \cdot (1 - gL_m3dB)}$$

$$|CgLm3dB| = 0.1776$$

$$\arg(CgLm3dB) \cdot \frac{180}{\pi} = 136$$

$$rgLm3dB = 0.70476$$

Potentially Unstable Case, $|S_{ii}| > 1$

* Still unilateral ($S_{12} \approx 0$)

* In practice, this would be unusual for a transistor.

When $|S_{ii}| > 1$, it is possible for

$$G_i = \frac{1 - |\Gamma_i|^2}{|1 - S_{ii}\Gamma_i|^2} \rightarrow \infty \text{ when } \Gamma_{ic} = \frac{1}{S_{ii}}$$

$\uparrow$ critical Γ_i

Note: $i = S$ w/ $ii = 11$ (Input)
 $i = L$ w/ $ii = 22$ (Output)

This implies that $\text{Re}\{Z_{ic}\}$ or positive resistance exactly cancels the negative $\text{Re}\{Z_{ii}\}$

$$\text{where } Z_{ic} = Z_0 \frac{1 + \Gamma_{ic}}{1 - \Gamma_{ic}} + Z_{ii} = Z_0 \frac{1 + S_{ii}}{1 - S_{ii}}$$



Zero input/output loop resistance!

Plots

1) Obviously, $G_{i,\max} = \infty$ and occurs at $\Gamma_{ic} = \frac{1}{S_{ii}}$ and this point is along the $\frac{1}{S_{ii}^*}$ line

2) Select values of G_i where you wish to draw circles of Γ_i which result in constant G_i .

$$G_i = 10^{\frac{G_i(\text{dB})}{10}}$$

3.4 cont.

2) cont. calculate corresponding normalized gain

factor $g_i = G_i (1 - |S_{ii}|^2) = \frac{1 - |\Gamma_i|^2}{|1 - S_{ii}\Gamma_i|^2} (1 - |S_{ii}|^2)$

Note! g_i can now be a negative number!

3) Calculate $C_{g_i} = \frac{g_i S_{ii}^*}{1 - |S_{ii}|^2 (1 - g_i)}$ for each g_i

4) Calculate $r_{g_i} = \frac{\sqrt{1 - g_i} (1 - |S_{ii}|^2)}{1 - |S_{ii}|^2 (1 - g_i)}$ for each g_i

5) Plot circles on Γ_i Smith Chart(s)

How do I know if a particular Γ_i is in the stable region?

Need $\left\{ \begin{array}{l} \text{Re}\{z_s\} > |\text{Re}(z_{sw})| \text{ and/or} \\ \text{Re}\{z_L\} > |\text{Re}(z_{out})| \end{array} \right.$


where $z_s = z_0 \frac{1 + \Gamma_s}{1 - \Gamma_s}$ and $z_L = z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$

$z_{IN} = z_0 \frac{1 + S_{11}}{1 - S_{11}}$ and $z_{out} = z_0 \frac{1 + S_{22}}{1 - S_{22}}$

$\Rightarrow$ For plotting on Smith Chart, divide by z_0 .

Rather than doing complicated calculations, the normalized resistance circle passing thru $\Gamma_{ic} = \frac{1}{S_{ii}}$ defines the boundary between the stable (all larger normalized resistances) and unstable regions on the Smith Chart

e.g.

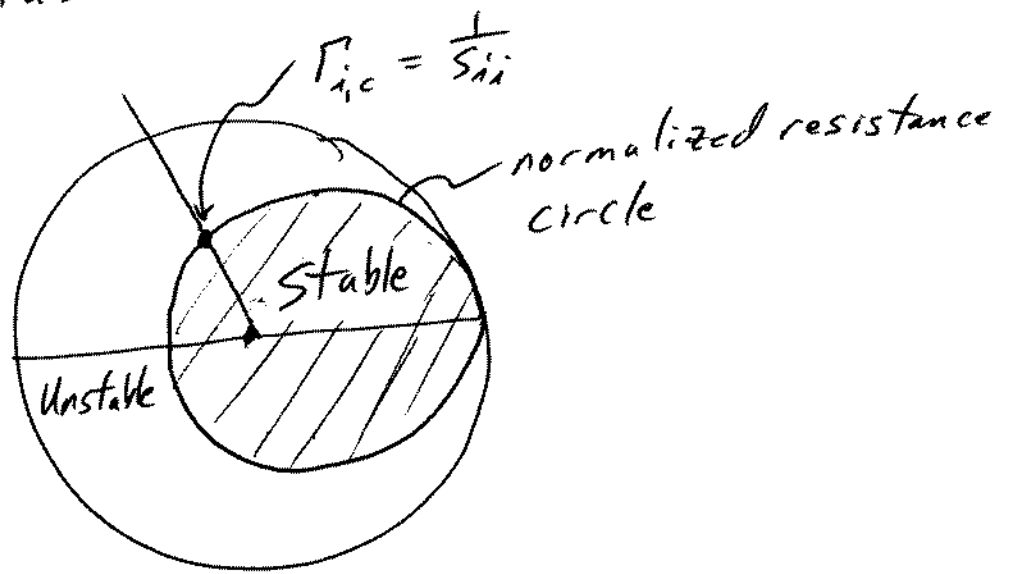

3.5 Unilateral Figure of Merit

What if $S_{12} \neq 0$, but we wish to assume (i.e., set $S_{12} = 0$) so we can take advantage of all the simplifications and constant gain circles? How can we tell how good our results will be in this case?

We'll compare the magnitude ratio of G_T w/ the unilateral G_{TU} (ideally equal to 1)

$$\frac{G_T}{G_{TU}} = \frac{1}{|1 - X|^2}$$

where $X = \frac{S_{12} S_{21} \Gamma_S \Gamma_L}{(1 - S_{11} \Gamma_S)(1 - S_{22} \Gamma_L)}$ $\leftarrow$ complex #

This ratio is bounded as

$$\frac{1}{(1 + |X|)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1 - |X|)^2}$$

One case of particular interest is $G_{TU, \max}$ which occurs when $\Gamma_S = S_{11}^*$ and $\Gamma_L = S_{22}^*$

For $G_{TU, \max}$

$$\frac{1}{(1+U)^2} < \frac{G_T}{G_{TU, \max}} < \frac{1}{(1-U)^2}$$

where $U = \frac{|S_{12}| |S_{21}| |S_{11}| |S_{22}|}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)} \equiv \text{Unilateral Figure of Merit}$

→ Easier to calculate than X

3.5 cont.

Example - Let's revisit our earlier examples
w/ the MLN2037F NPN Silicon RF
power transistor operating at 16 MHz
w/ $\Gamma_S = 0.8 \angle -150^\circ$ and $\Gamma_L = 0.3 \angle 140^\circ$

and

$$S_{11} = 0.8128 \angle 156^\circ \quad S_{12} = 0.0944 \angle 63^\circ$$

$$S_{21} = 1.81 \angle 55^\circ \quad S_{22} = 0.3801 \angle -136^\circ$$

Here

$$X = \frac{(0.0944 \angle 63^\circ)(1.81 \angle 55^\circ)(0.8 \angle -150^\circ)(0.3 \angle 140^\circ)}{[1 - (0.8128 \angle 156^\circ)(0.8 \angle -150^\circ)][1 - (0.3801 \angle -136^\circ)(0.3 \angle 140^\circ)]}$$

$$= 0.12859607 \angle 119.403205^\circ$$

and

$$\frac{1}{(1 + 0.1286)^2} < \frac{G_T}{G_{Tn}} < \frac{1}{(1 - 0.1286)^2}$$

$$0.7850963 < \frac{G_T}{G_{Tn}} < 1.316924786$$

$$-1.05077 \text{ dB} < \frac{G_T}{G_{Tn}} < 1.19561 \text{ dB}$$

↗ Max. Error is $\sim \pm 1.1 \text{ dB}$
(Not too good)

Example cont. -

What if we let $\Gamma_S = S_{11}^* = 0.8128 \angle -156^\circ$
and $\Gamma_L = S_{22}^* = 0.3801 \angle +136^\circ$ {the $G_{TU, \max}$ case}?

Now

$$U = \frac{(0.0944)(1.81)(0.8128)(0.3801)}{(1 - 0.8128^2)(1 - 0.3801^2)}$$

$$U = 0.181821068$$

$$\frac{1}{(1 + 0.18182)^2} < \frac{G_T}{G_{TU, \max}} < \frac{1}{(1 - 0.18182)^2}$$

$$0.71597283 < \frac{G_T}{G_{TU, \max}} < 1.4938377$$

$$-1.451 \text{ dB} < \frac{G_T}{G_{TU, \max}} < 1.743 \text{ dB}$$

↑
Max. error is worse under this assumption.

⇒ All in all, the unilateral assumption for the MLN2037F @ 1 GHz is pretty poor.

Unilateral Figure of Merit example for MLN2037F at 1 GHz

$$S_{11} := 0.8128 \cdot e^{j \cdot 156 \cdot \frac{\pi}{180}}$$

$$S_{12} := 0.0944 \cdot e^{j \cdot 63 \cdot \frac{\pi}{180}}$$

$$S_{21} := 1.81 \cdot e^{j \cdot 55 \cdot \frac{\pi}{180}}$$

$$S_{22} := 0.3801 \cdot e^{j \cdot -136 \cdot \frac{\pi}{180}}$$

$$\Gamma_S := 0.8 \cdot e^{j \cdot -150 \cdot \frac{\pi}{180}}$$

$$\Gamma_L := 0.3 \cdot e^{j \cdot 140 \cdot \frac{\pi}{180}}$$

$$X := \frac{S_{12} \cdot S_{21} \cdot \Gamma_S \cdot \Gamma_L}{(1 - S_{11} \cdot \Gamma_S)(1 - S_{22} \cdot \Gamma_L)}$$

$$|X| = 0.128596 \quad \arg(X) \cdot \frac{180}{\pi} = 119.4032$$

$$\frac{1}{(1 + |X|)^2} = 0.7851$$

$$\frac{1}{(1 - |X|)^2} = 1.31692$$

$$10 \cdot \log \left[\frac{1}{(1 + |X|)^2} \right] = -1.05077 \quad \text{dB}$$

$$10 \cdot \log \left[\frac{1}{(1 - |X|)^2} \right] = 1.19561 \quad \text{dB}$$

$$U := \frac{|S_{12}| \cdot |S_{21}| \cdot |S_{11}| \cdot |S_{22}|}{[1 - (|S_{11}|)^2][1 - (|S_{22}|)^2]}$$

$$\boxed{U = 0.181821}$$

$$\frac{1}{(1 + U)^2} = 0.71597$$

$$\frac{1}{(1 - U)^2} = 1.49384$$

$$10 \cdot \log \left[\frac{1}{(1 + U)^2} \right] = -1.45103 \quad \text{dB}$$

$$10 \cdot \log \left[\frac{1}{(1 - U)^2} \right] = 1.74303 \quad \text{dB}$$