

Chapter 3 Microwave Transistor

Amplifier Design

3.1 Introduction

Design Considerations include


- * stability
 - * power gain
 - * bandwidth
 - * noise
 - * dc
- } chapter 3

Stability — unconditionally stable
→ stable for all passive loads / terminations

 \ potentially unstable
 → care must be taken w/ passive terminations


Unilateral Transistors — $S_{12} = 0$ (or is negligible)

Else
Bilateral Transistor

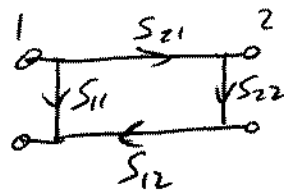

3.2 Power Gain Equations

2

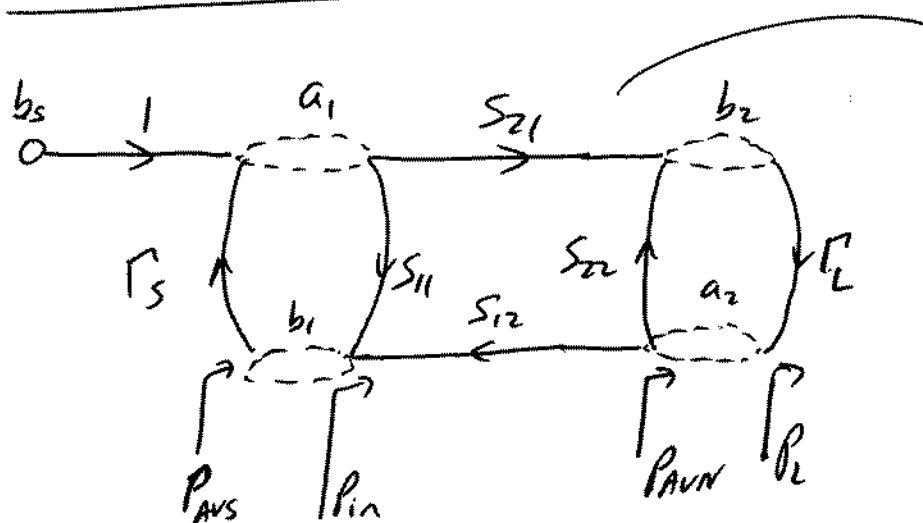

S parameters
of the transistor

$$P_L \equiv \text{Power delivered to load} = \frac{1}{2} |b_2|^2 - \frac{1}{2} |a_2|^2$$

$$P_{AVN} \equiv \text{Power available from network} = P_L | \Gamma_L = \Gamma_S^* |$$

$$P_{IN} \equiv \text{Power input to network} = \frac{1}{2} |a_1|^2 - \frac{1}{2} |b_1|^2$$

$$P_{AVS} \equiv \text{Power available from source} = P_{IN} | \Gamma_L = \Gamma_{out}^* |$$

$$\begin{aligned} \text{Transducer Power Gain} \equiv G_T &= \frac{P_L}{P_{AVS}} = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{IN} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2} \\ &= \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out} \Gamma_L|^2} \end{aligned}$$


$$\text{(Operating) Power Gain} \equiv G_P = \frac{P_L}{P_{IN}} = \frac{1}{1 - |\Gamma_{IN}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

$$\text{Available Power Gain} \equiv G_A = \frac{P_{AVN}}{P_{AVS}} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \Gamma_S|^2} |S_{21}|^2 \frac{1}{1 - |\Gamma_{out}|^2}$$

$$\Gamma_{IN} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \quad + \quad \Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$

3.2 cont.

Transistor

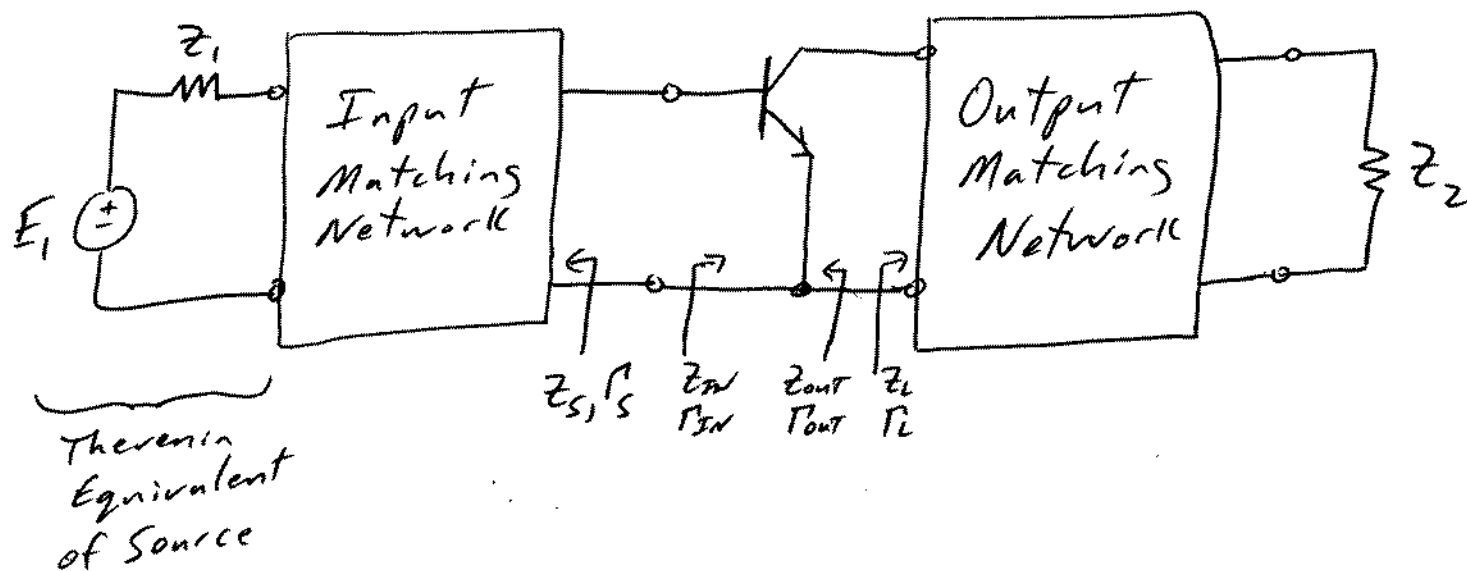

* Typically, $Z_1 = Z_2 = 50\Omega$

* If the matching networks are passive,

$$|\Gamma_S| < 1 \text{ and } |\Gamma_L| < 1$$

$$\Rightarrow \operatorname{Re}(Z_S) > 0 \text{ and } \operatorname{Re}(Z_L) > 0$$

* It is possible for $|\Gamma_{IN}| > 1$ and/or $|\Gamma_{OUT}| > 1$ to result for certain S parameters, even when $|\Gamma_S| + |\Gamma_L|$ are less than one.

↳ possible instability (oscillations)

Example- With an Advanced Semiconductor, Inc. MLN2037F NPN silicon RF power transistor (data sheets attached) in the microwave amplifier below, determine Γ_{IN} , Γ_{OUT} , G_T , G_P , and G_A at 1 GHz when $\Gamma_S = 0.8\angle -150^\circ$ and $\Gamma_L = 0.3\angle 140^\circ$.

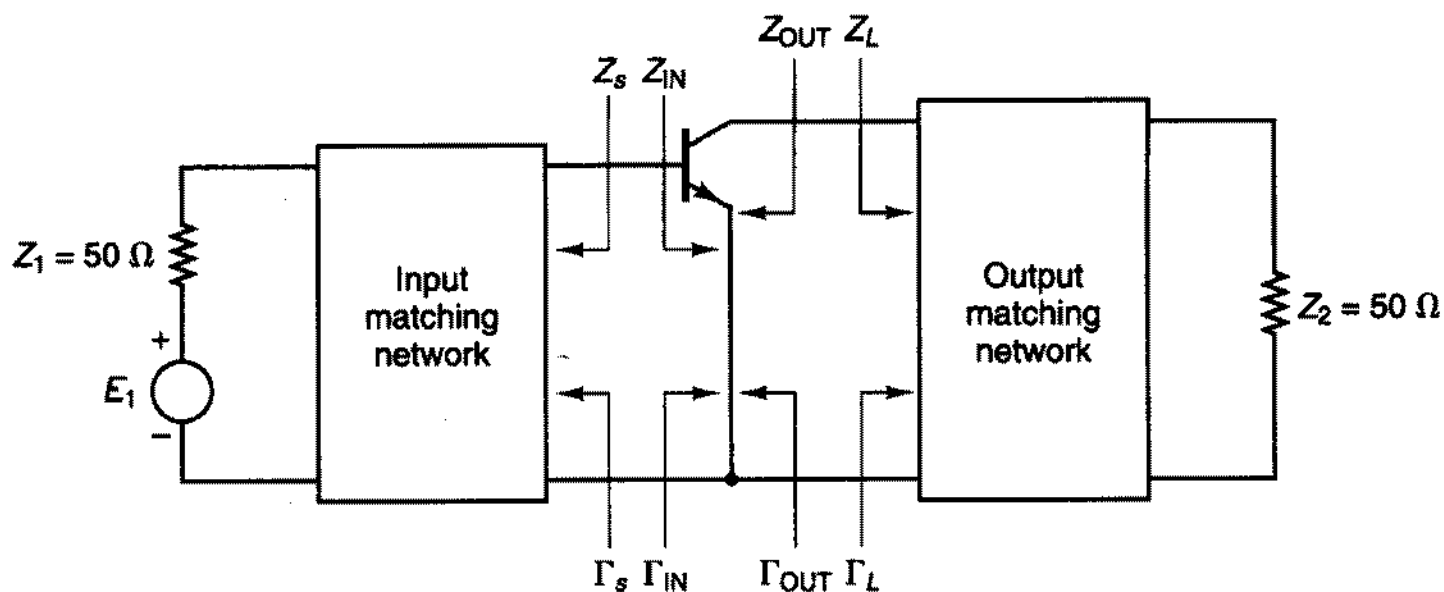


Figure 3.2.2 A microwave amplifier diagram.

From page 2/2 of the data sheet:

$$S_{11} = 0.8128\angle 156^\circ, \quad S_{12} = 0.0944\angle 63^\circ$$

$$S_{21} = 1.81\angle 55^\circ, \quad S_{22} = 0.3801\angle -136^\circ$$

$$(3.2.5) \quad \Gamma_{IN} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$= (0.8128\angle 156^\circ) + \frac{(0.0944\angle 63^\circ)(1.81\angle 55^\circ)(0.3\angle 140^\circ)}{1 - (0.3801\angle -136^\circ)(0.3\angle 140^\circ)}$$

$$= 0.8128\angle 156^\circ + 0.05784\angle -101.486^\circ$$

$$\Gamma_{IN} = 0.80226\angle 160.036^\circ$$

$$\begin{aligned}
 (3.2.6) \quad \Gamma_{out} &= S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S} \\
 &= (0.3801 \angle -136^\circ) + \frac{(0.0944 \angle 63^\circ)(1.81 \angle 55^\circ)(0.8 \angle -150^\circ)}{1 - (0.8128 \angle 156^\circ)(0.8 \angle -150^\circ)} \\
 &= (0.3801 \angle -136^\circ) + (0.380 \angle -21.11^\circ)
 \end{aligned}$$

$$\underline{\Gamma_{out} = 0.40897 \angle -78.578^\circ}$$

$$\begin{aligned}
 (3.2.1) \quad G_T &= \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2} \quad \text{Transducer Power Gain} \\
 &= \frac{1 - 0.8^2}{|1 - (0.8023 \angle 160^\circ)(0.8 \angle -150^\circ)|^2} (1.81^2) \frac{1 - 0.3^2}{|1 - (0.3801 \angle -136^\circ)(0.3 \angle 140^\circ)|^2} \\
 &= (2.433)(3.2761)(1.159) \\
 \underline{G_T = 9.2355} &= 10 \log_{10} (9.2355) = 9.6546 \text{ dB}
 \end{aligned}$$

Similarly

$$\begin{aligned}
 (3.2.2) \quad G_T &= \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out} \Gamma_L|^2} \\
 &= \frac{1 - 0.8^2}{|1 - (0.8128 \angle 156^\circ)(0.8 \angle -150^\circ)|^2} (1.81)^2 \frac{1 - 0.3^2}{|1 - (0.4091 \angle -78.6^\circ)(0.3 \angle 140^\circ)|^2} \\
 &= (2.781)(3.2761)(1.014) \\
 \underline{G_T = 9.2355} &= 9.6546 \text{ dB}
 \end{aligned}$$

$$(3.2.3) \quad G_p = \frac{1}{1 - |\Gamma_{IN}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} \quad \text{Operating Power Gain}$$

$$= \frac{1}{1 - 0.80226^2} (1.81)^2 \frac{1 - 0.3^2}{|1 - (0.384 \angle -136^\circ)(0.3 \angle 140^\circ)|^2}$$

$$= (2.806)(3.2761)(1.159)$$

$$\underline{\underline{G_p = 10.650 = 10.2734 \text{ dB}}}$$

$$(3.2.4) \quad G_A = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1}{1 - |\Gamma_{OUT}|^2} \quad \text{Available Power Gain}$$

$$= \frac{1 - 0.8^2}{|1 - (0.8128 \angle 156^\circ)(0.8 \angle -150^\circ)|^2} (1.81)^2 \frac{1}{1 - 0.409^2}$$

$$= (2.781)(3.2761)(1.201)$$

$$\underline{\underline{G_A = 10.9402 = 10.3903 \text{ dB}}}$$

Note: * G_p is $10.2734 - 9.6546 = 0.6188 \text{ dB}$ larger than G_T . This implies that $P_{IN} < P_{AVS}$ (common sense).

* Also, note that all three gains are w/in a 1dB range $\Rightarrow$ fairly good matchings.

NPN SILICON RF POWER TRANSISTOR

DESCRIPTION:

The **ASI MLN2037F** is Designed for Class A Linear Applications up to 2.0 GHz.


FEATURES:

- Class A Operation
- $P_G = 5.0$ dB at 5.0 W/2.0 GHz
- **Omnigold™** Metalization System
- Common Emitter

MAXIMUM RATINGS

I_C	10 A
V_{CB}	60 V
V_{CE}	35 V
P_{DISS}	140 W @ $T_C = 25^\circ\text{C}$
T_J	-65°C to $+200^\circ\text{C}$
T_{STG}	-65°C to $+150^\circ\text{C}$
θ_{JC}	5.5°C/W

PACKAGE STYLE .250 2L FLG

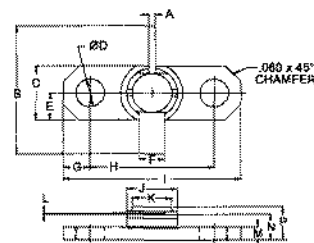

DIM	MINIMUM inches / mm	MAXIMUM inches / mm
A	.028 / 0.71	.032 / 0.81
B	.740 / 18.80	
C	.245 / 6.22	.255 / 6.48
D	.128 / 3.25	.132 / 3.35
E		.125 / 3.18
F	.110 / 2.79	.117 / 2.97
G		.117 / 2.97
H	.560 / 14.22	.570 / 14.48
J	.790 / 20.07	.810 / 20.57
K	.225 / 5.72	.235 / 5.97
L	.105 / 4.19	.105 / 4.70
M	.003 / 0.08	.007 / 0.18
N	.058 / 1.47	.068 / 1.73
P	.119 / 3.02	.135 / 3.43
	.148 / 3.76	.167 / 4.75

ORDER CODE: ASI10635

CHARACTERISTICS $T_C = 25^\circ\text{C}$

SYMBOL	TEST CONDITIONS	MINIMUM	TYPICAL	MAXIMUM	UNITS
BV_{CEO}	$I_C = 50$ mA	35			V
BV_{CER}	$I_C = 50$ mA $R_{BE} = 10 \Omega$	60			V
BV_{EBO}	$I_E = 10$ mA	4.0			V
I_{CES}	$V_E = 28$ V			5	mA
h_{FE}	$V_{CE} = 5.0$ V $I_C = 1.0$ A	10		100	---
C_{ob}	$V_{CB} = 28$ V $f = 1.0$ MHz			15	pF
P_G	$V_{CE} = 20$ V $I_{CQ} = 800$ mA $f = 2.0$ GHz $P_{OUT} = 5.0$ W	5.0			dB

ADVANCED SEMICONDUCTOR, INC.

7525 ETHEL AVENUE • NORTH HOLLYWOOD, CA 91605 • (818) 982-1200 • FAX (818) 765-3004

REV. C

1/2

Specifications are subject to change without notice.



MLN2037F

TYPICAL S PARAMETERS:

 $Z_0 = 50 \Omega$ $V_{CE} = 15 \text{ V}$, $I_C = 160 \text{ mA}$, $T_A = 25^\circ\text{C}$

FREQ.	S21			S12		S11		S22	
GHz	dB	Mag	Ang	Mag	Ang	Mag	Ang	Mag	Ang
0.20	16.40	6.60	90	0.0281	42	0.8709	-173	0.2511	-138
0.50	9.00	2.81	71	0.0467	52	0.8709	170	0.4027	-144
1.00	5.20	1.81	55	0.0944	63	0.8128	156	0.3801	-136
1.50	1.40	1.17	42	0.1548	62	0.7673	141	0.5888	-139
2.00	-0.60	0.93	24	0.2344	52	0.7762	112	0.6998	-171

ADVANCED SEMICONDUCTOR, INC.

REV. C


7525 ETHEL AVENUE • NORTH HOLLYWOOD, CA 91605 • (818) 982-1200 • FAX (818) 765-3004

2/2

Specifications are subject to change without notice.

3.3 Stability Considerations

9

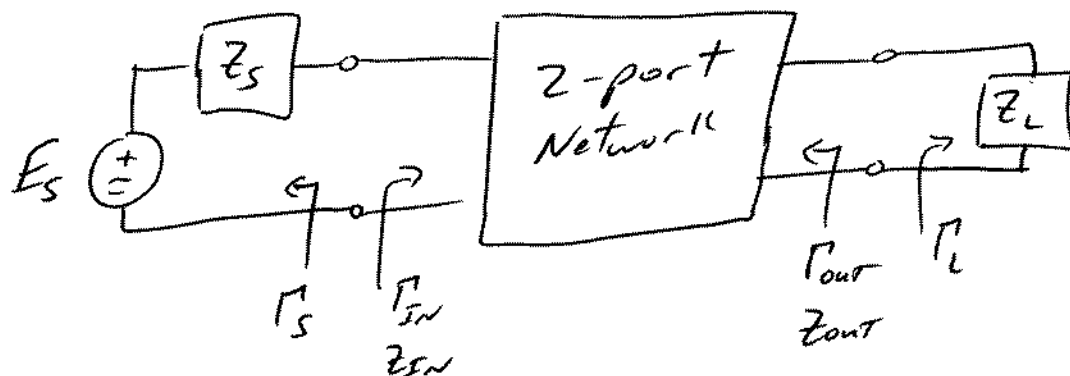

Unconditionally Stable when

$$|\Gamma_s| < 1$$

$$|\Gamma_L| < 1$$

} $\Rightarrow$ passive source + load

$$|\Gamma_{IN}| = \left| S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right| < 1$$

} $\Rightarrow \text{Re}\{Z_{IN}\} > 0$
 $\text{Re}\{Z_{OUT}\} > 0$

and

$$|\Gamma_{OUT}| = \left| S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s} \right| < 1$$

$\rightarrow$ all Γ are with respect to characteristic impedance Z_0

$\rightarrow$ for a unilateral two-port network ($S_{12} = 0$),

$$|\Gamma_{IN}| = |S_{11}| < 1$$

$$|\Gamma_{OUT}| = |S_{22}| < 1$$

3.3 cont.

10

What if the two-port network (e.g. transistor) is potentially unstable?

⇒ Be very helpful to know which values of Γ_S and Γ_L would result in a stable amplifier and which would not.

Start by finding Γ_S & Γ_L values which result in $|\Gamma_{in}|=1$ and $|\Gamma_{out}|=1$, the boundary between the stable regions and unstable regions. Setting the $|\Gamma_{in}|$ and $|\Gamma_{out}|$ equation equal to one, results in (see Appendix A)

$$\left. \begin{aligned} & \left| \Gamma_L - \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| \\ \text{and} & \left| \Gamma_S - \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right| \end{aligned} \right\} \text{stability circles}$$

where $\Delta = S_{11} S_{22} - S_{12} S_{21}$.

The first stability circle is the output stability circle where $|\Gamma_{in}|=1$ which yields Γ_L values. The second circle is the input stability circle where $|\Gamma_{out}|=1$ which yields Γ_S values.

3.3 cont.

11

Using the stability circle equations, we can find the radii and centers of the circles:

Output Stability Circle; Γ_L where $|\Gamma_{in}| = 1$

$$\text{radius } r_L = \left| \frac{S_{12} S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| \quad \leftarrow \text{real positive \#}$$



$$\text{center } C_L = |C_L| \angle C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \quad \leftarrow \text{complex \#}$$

Input Stability Circle; Γ_S where $|\Gamma_{out}| = 1$

$$r_S = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right| \quad \leftarrow \text{real positive \#}$$

$$C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \quad \leftarrow \text{complex \#}$$

↑ We'll plot these circles on Γ_L &/or Γ_S complex planes (e.g. Smith Charts), taking particular note of the regions where $|\Gamma_L| \leq 1$ and $|\Gamma_S| \leq 1$ (passive). where we are inside the standard Smith Chart circle.

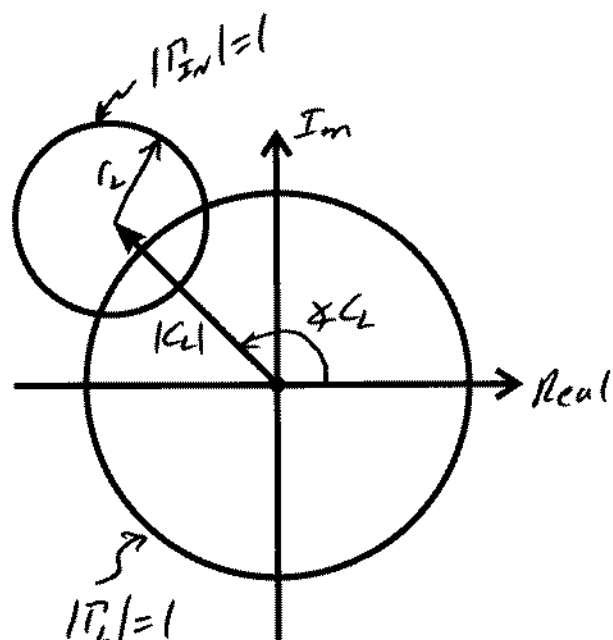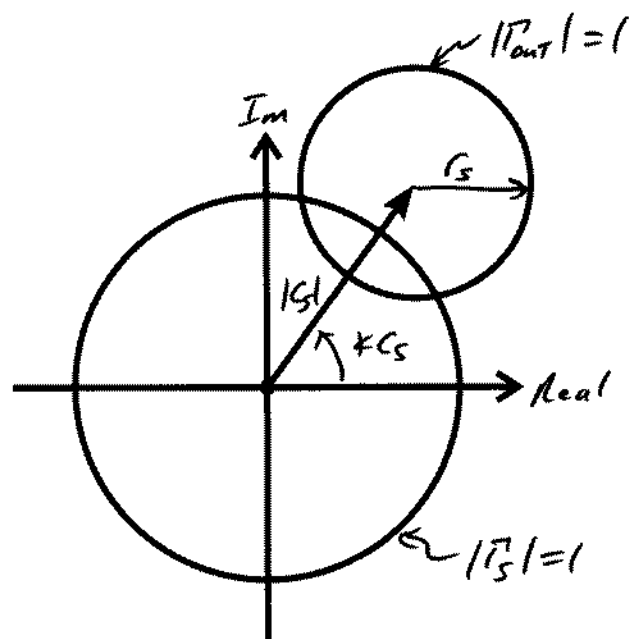 Γ_L complex plane Γ_S complex plane

How can we determine stable regions (i.e., $|\Gamma_{IN}| < 1$ and $|\Gamma_{OUT}| < 1$)?

Method to determine stable regions

- 1) Choose a point for Γ_L ^{inside/} outside the $|\Gamma_{IN}| = 1$ circle.
- 2) Calculate $|\Gamma_{IN}| = \left| S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right|$
- 3) If $|\Gamma_{IN}| < 1$, then the region inside/outside the $|\Gamma_{IN}| = 1$ circle is stable. If not, the region inside/outside the $|\Gamma_{IN}| = 1$ circle (where Γ_L point is located) is unstable.
- 4) Repeat for Γ_S and $|\Gamma_{OUT}| = 1$ circle.

3.3 cont.

A particularly easy set of points to test are $\Gamma_L = 0$ (matched load, $Z_L = Z_0$) where

$|\Gamma_{in}| = |S_{11}|$, Is $|S_{11}| < 1$? Yes $\rightarrow \Gamma_L = 0$ point in stable region

No $\rightarrow \Gamma_L = 0$ point in unstable region


and

$\Gamma_S = 0$ (matched source, $Z_S = Z_0$) where


$|\Gamma_{out}| = |S_{22}|$, Is $|S_{22}| < 1$? Yes $\rightarrow \Gamma_S = 0$ point in stable region

No $\rightarrow \Gamma_S = 0$ point in unstable region


for example,

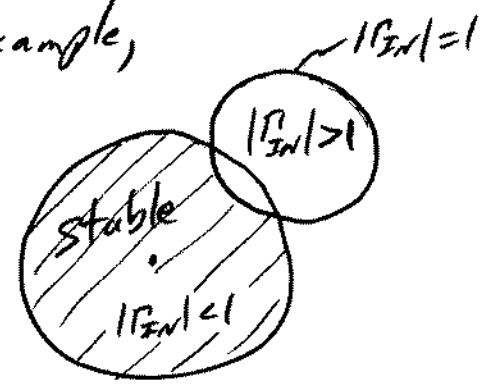


Γ_L plane
 $|S_{11}| < 1$

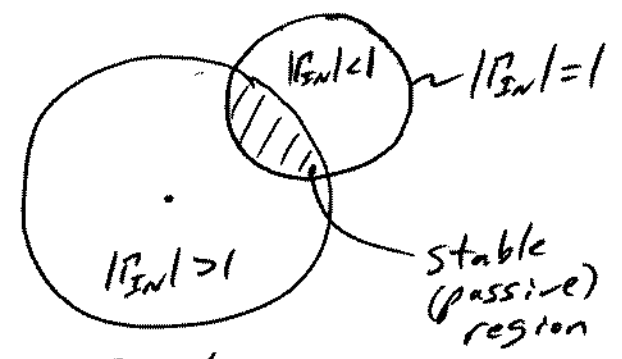

Γ_L plane
 $|S_{11}| > 1$

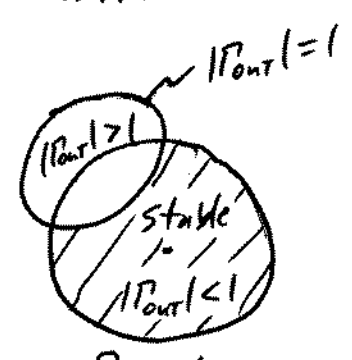

Γ_S plane
 $|S_{22}| < 1$

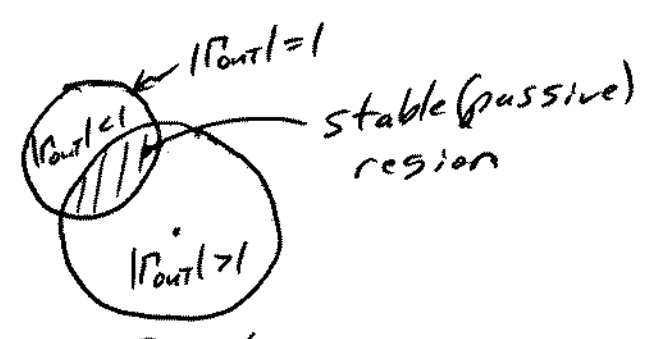

Γ_S plane
 $|S_{22}| > 1$

Note, if $|S_{11}| > 1$ or $|S_{22}| > 1$, the network can NOT be unconditionally stable since $|Γ_{IN}|$ or $|Γ_{OUT}| > 1$ will be greater than 1, even when $Γ_L$ or $Γ_S$ are zero (matched!).

Necessary & sufficient conditions for a two-port to be unconditionally stable.

$$① \quad K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{12} S_{21}|} > 1$$

$$② \quad 1 - |S_{11}|^2 > |S_{12} S_{21}|$$

$$③ \quad 1 - |S_{22}|^2 > |S_{12} S_{21}|$$

where $\Delta = S_{11} S_{22} - S_{12} S_{21}$

OR

$$① \quad K > 1$$

$$② \quad |\Delta| < 1$$

} Easier!

If these conditions are NOT met, the two-port is potentially unstable.

Example- Let's revisit our earlier example with an Advanced Semiconductor, Inc. MLN2037F NPN silicon RF power transistor operating at 1 GHz with $\Gamma_S = 0.8 \angle -150^\circ$ and $\Gamma_L = 0.3 \angle 140^\circ$.

Using the datasheet, the S parameters at 1 GHz are:

$$S_{11} = 0.8128 \angle 156^\circ, \quad S_{12} = 0.0944 \angle 63^\circ$$

$$S_{21} = 1.81 \angle 55^\circ, \quad S_{22} = 0.3801 \angle -136^\circ$$

We calculated:

$$\Gamma_{IN} = 0.80226 \angle 160.036^\circ \text{ and } \Gamma_{OUT} = 0.40897 \angle -78.578^\circ.$$

Output Stability Circle (Γ_L values for $|\Gamma_{IN}|=1$)

$$\begin{aligned} \text{First, calculate } \Delta &= S_{11} S_{22} - S_{12} S_{21} \\ &= (0.8128 \angle 156^\circ)(0.3801 \angle -136^\circ) \\ &\quad - (0.0944 \angle 63^\circ)(1.81 \angle 55^\circ) \end{aligned}$$

$$\Delta = 0.37328 \angle -6.9548^\circ$$

$$\begin{aligned} (3.3.7) \quad r_L &= \left| \frac{S_{12} S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{(0.0944 \angle 63^\circ)(1.81 \angle 55^\circ)}{0.3801^2 - 0.37328^2} \right| \\ &= \left| \frac{0.170864 \angle 118^\circ}{0.005138} \right| = |33.235 \angle 118^\circ| \end{aligned}$$

$$r_L = 33.235$$

$$(3.3.8) \quad c_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} = \frac{[(0.3801 \angle -136^\circ) - (0.3733 \angle -7^\circ)(0.8128 \angle -156^\circ)]^*}{0.3801^2 - 0.37328^2}$$

complex conjugate operator

$$c_L = (34.21368 \angle +94.5682^\circ)$$

Input Stability Circle (Γ_S values where $|\Gamma_{out}|=1$)

$$(3.3.9) \quad \Gamma_S = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right| = \left| \frac{(0.0944 \angle 63^\circ)(1.81 \angle 55^\circ)}{0.8128^2 - 0.373^2} \right|$$

$$= |0.32776 \angle 118^\circ|$$

$$\underline{\underline{\Gamma_S = 0.32776}}$$

$$(3.3.10) \quad C_S = \frac{[S_{11} - \Delta S_{22}^*]^*}{|S_{11}|^2 - |\Delta|^2}$$

$$= \frac{[(0.8128 \angle 156^\circ) - (0.373 \angle -7^\circ)(0.3801 \angle +136^\circ)]^*}{0.8128^2 - 0.373^2}$$

$$= \frac{0.68934 \angle -161.353^\circ}{0.8128^2 - 0.373^2}$$

$$\underline{\underline{C_S = 1.32232 \angle -161.3533^\circ}}$$

Circle plots on next pages. Note that both $|S_{11}| < 1$ and $|S_{22}| < 1$. So, $\Gamma_L + \Gamma_L = 0$ are stable.

Unconditionally stable?


$$(1) \quad K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{12} S_{21}|} = \frac{1 - 0.8128^2 - 0.3801^2 + 0.373^2}{2 |(0.0944 \angle 63^\circ)(1.81 \angle 55^\circ)|}$$

$$= 0.978 \not> 1 \quad \underline{\underline{\text{NOT unconditionally stable}}}$$

$$(2) \quad |\Delta| = 0.373 < 1 \quad \leftarrow \text{This condition is met}$$

Output Stability Circle

17 (3/4)

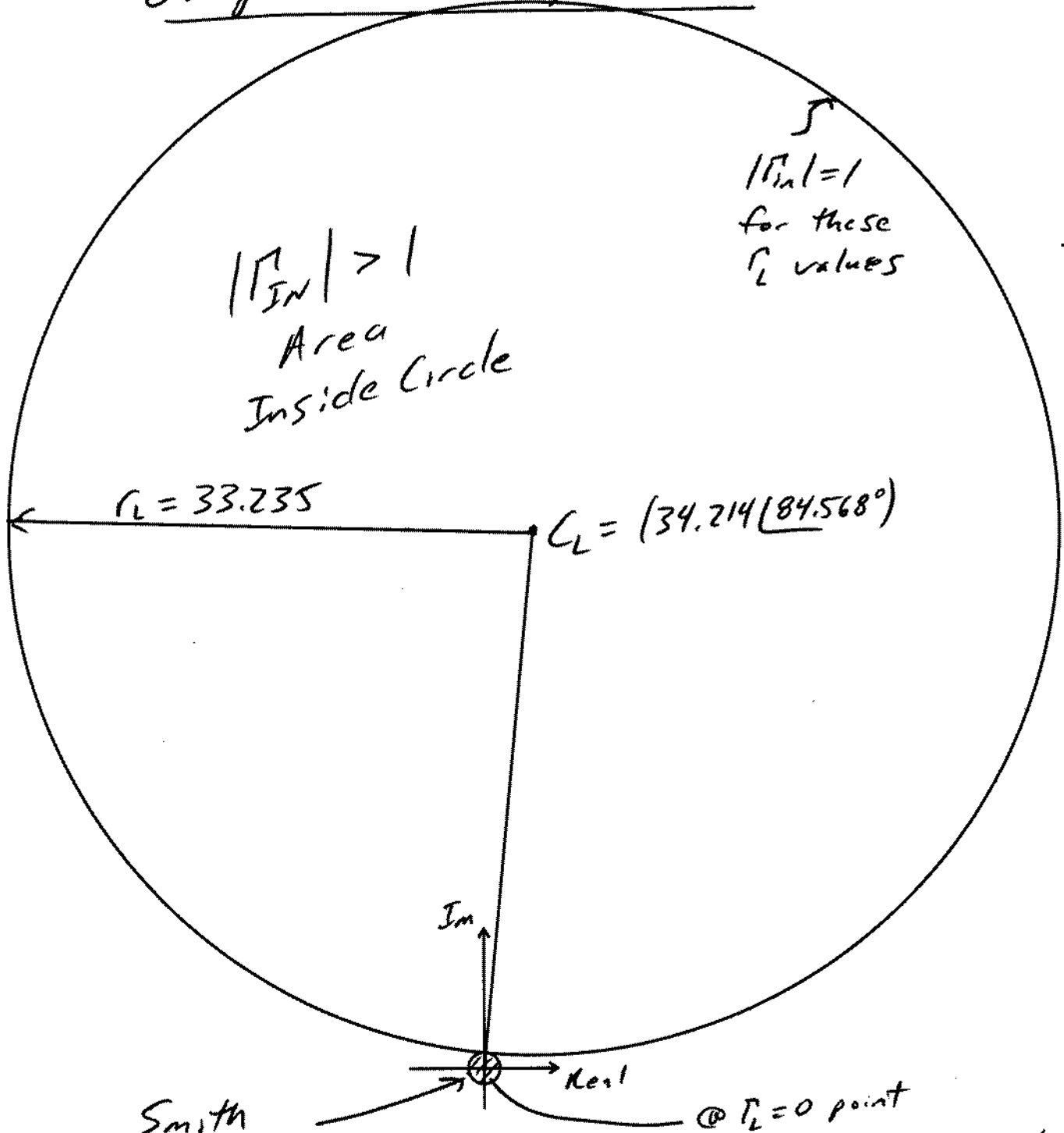


Smith Chart
 $|\Gamma_L| = 1$ circle

@ $\Gamma_L = 0$ point

$|\Gamma_{IN}| = |S_{11}| = 0.8128 < 1$
STABLE


Close-up

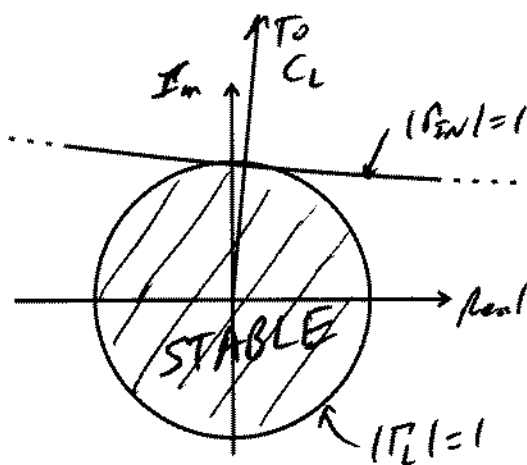

Note that
Output stability
circle & Γ_L
Smith Chart
intersect!

Input Stability Circle

→ On Γ_S complex plane

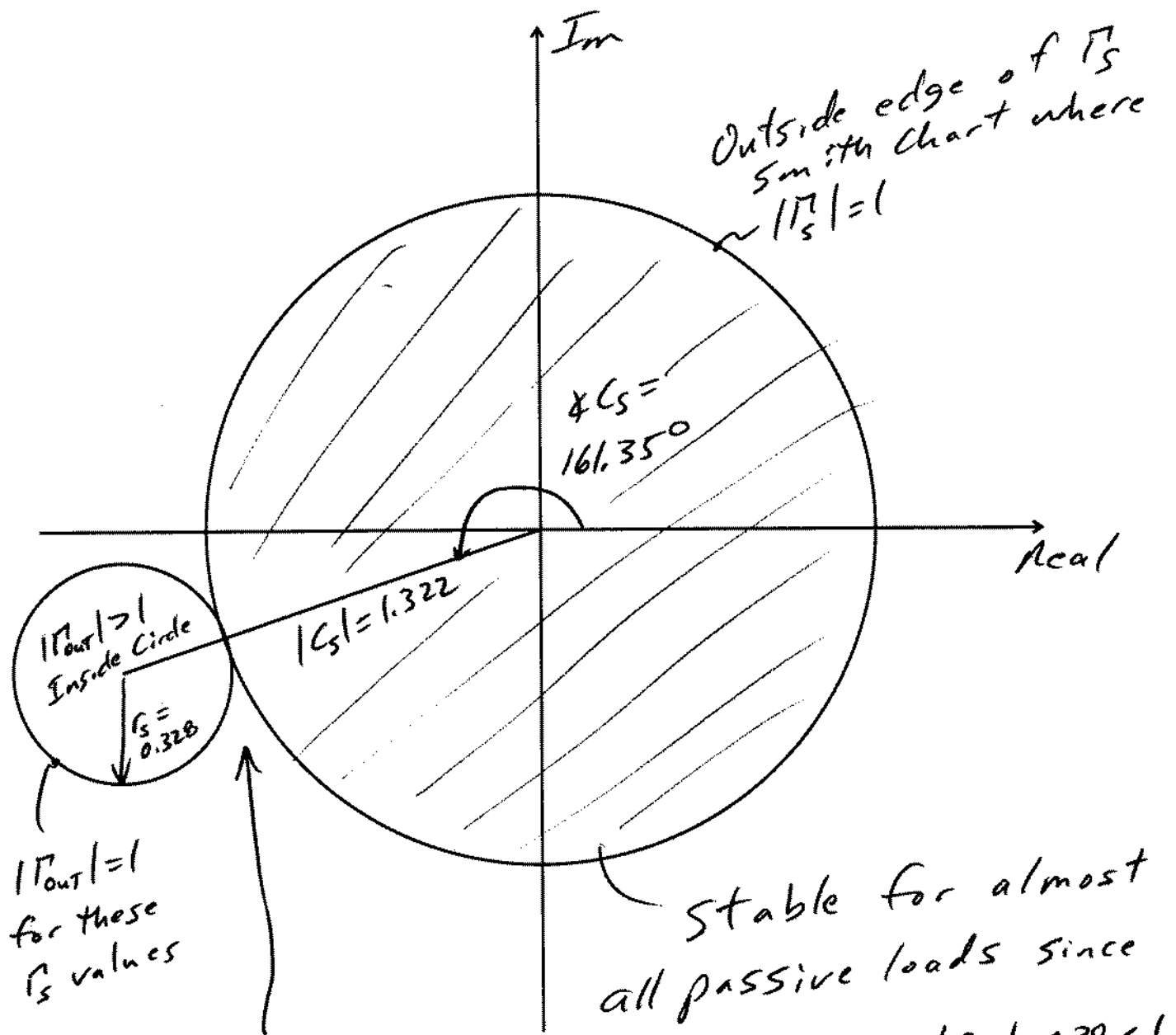

Note that input stability circle + Γ_S Smith Chart intersect (barely)!