

3.6 Simultaneous Conjugate Match: Bilateral Case


40

→ Now $S_{12} \neq 0$

↖ Possible for unconditionally stable 2-ports.

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$
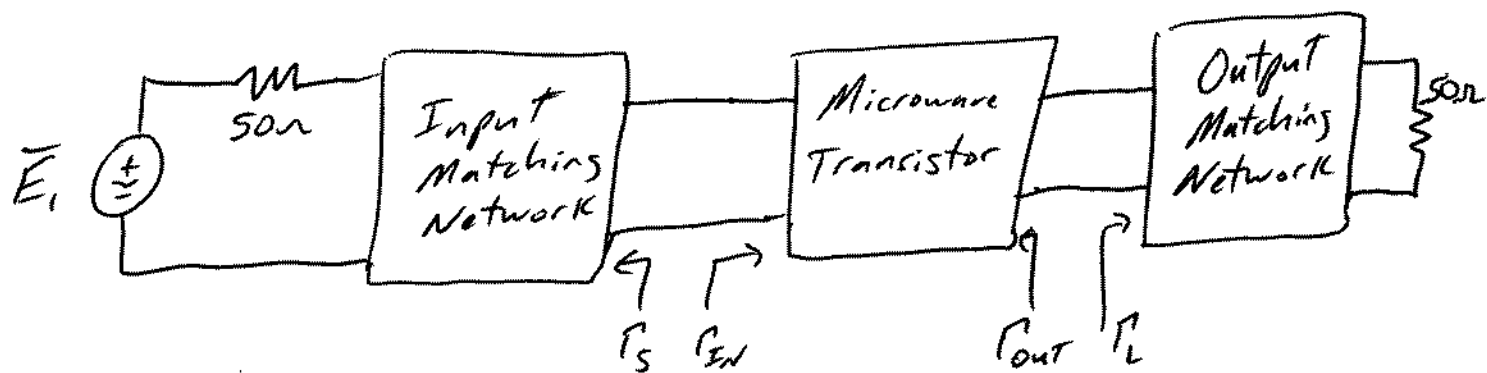
$$\Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$



for maximum transducer power gain $G_{T,max}$

we need $\Gamma_S = \Gamma_{IN}^*$ and $\Gamma_L = \Gamma_{OUT}^*$

i.e., simultaneous complex conjugate match.

Using this requirement and the above Γ_{in} & Γ_{out} equations, leads to the desired Γ_S & Γ_L values

for $G_{T,max}$:

$$\Gamma_{MS} = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$

and

$$\Gamma_{ML} = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

[Note: Use the "-" solutions for Γ_{MS} & Γ_{ML} for an unconditionally stable 2-port network.]

3.6 cont.

where $B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$

$$B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$\Delta = S_{11} S_{22} - S_{21} S_{12}$$

$$C_1 = S_{11} - \Delta S_{22}^*$$

$$C_2 = S_{22} - \Delta S_{11}^*$$

Appendix E covers how we choose between the $\pm$ solutions for Γ_{ms} + Γ_{ml} .

For Γ_{ms} , if $|\frac{B_1}{2C_1}| > 1$ + $B_1 > 0$ $\rightarrow$ "-" gives $|\Gamma_{ms}| < 1$
 $\rightarrow$ "+" gives $|\Gamma_{ms}| > 1$

if $|\frac{B_1}{2C_1}| > 1$ + $B_1 < 0$ $\rightarrow$ "+" gives $|\Gamma_{ms}| < 1$
 $\rightarrow$ "-" gives $|\Gamma_{ms}| > 1$

For Γ_{ml} , if $|\frac{B_2}{2C_2}| > 1$ + $B_2 > 0$ $\rightarrow$ "-" gives $|\Gamma_{ml}| < 1$
 $\rightarrow$ "+" gives $|\Gamma_{ml}| > 1$

if $|\frac{B_2}{2C_2}| > 1$ + $B_2 < 0$ $\rightarrow$ "+" gives $|\Gamma_{ml}| < 1$
 $\rightarrow$ "-" gives $|\Gamma_{ml}| > 1$

From a practical standpoint, it may be easiest just to compute both the $\pm$ solutions and see where they fall on the Γ_s or Γ_L planes.

3.6 cont.

These conditions can be related to

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2}{2|S_{12}S_{21}|}$$

If $K > 1$ and $B_i > 0 \rightarrow$ use "-" solutions,

If $K < -1 \Rightarrow$ No Simultaneous conjugate match.
or $K < 1$



For $|\Gamma_{ms}| < 1$ (i.e. $\text{Re}(z_s) > 0$) and $|\Gamma_{ml}| < 1$ (i.e. $\text{Re}(z_L) > 0$)

$\hookrightarrow$ $K > 1$ and $|\Delta| < 1$

Note: $|\Delta| < 1$ implies $B_1 > 0$ and $B_2 > 0 \Rightarrow$ use "-" soln

What about potentially unstable problems?

$\hookrightarrow$ use G_p and/or G_A per next section.

w/ $\Gamma_S = \Gamma_{ms} = \Gamma_{IN}^*$ and $\Gamma_L = \Gamma_{ml} = \Gamma_{OUT}^*$

$$G_{T,max} = \frac{1}{1 - |\Gamma_{ms}|^2} |S_{21}|^2 \frac{1 - |\Gamma_{ml}|^2}{|1 - S_{22}\Gamma_{ml}|^2} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1})$$

+

$$G_{T,max} = G_{p,max} = G_{A,max}$$

↑
Note: Need
 $K > 1$

From the last eqn, we see that $G_{T,max}$ is largest when $K=1$. Call it the maximum stable gain

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|}.$$

If a transistor is potentially unstable (ie. $K < 1$), the ratio $\frac{|S_{21}|}{|S_{12}|}$ is used as a figure of merit.

What if $K > 1$ but $|A| > 1$?

Then, the "+" solutions to Γ_{ms} and Γ_{ml} yield the minimum value $G_{T,min}$ of the transducer gain and the input & output VSWR = 1.

$$G_{T,min} = \frac{|S_{21}|}{|S_{12}|} (K + \sqrt{K^2 - 1})$$

What if we do NOT want $G_{T,max}$?

→ A constant gain circle approach is possible, but not practical (very iterative as Γ_{in} is a function of Γ_L which makes the G_s' function dependent on G_L).

→ A better set of approaches for bilateral transistors is described in Section 3.7.

Some possibilities

- ① Unconditionally stable bilateral transistor
 - a) design for $G_{T, \max}$
 - b) design for desired operating power gain G_p
 - c) design for desired available power gain G_A
- ② Potentially unstable bilateral transistor
↳ b) or c) from above.

Simultaneous Conjugate Match: Bilateral Case example

1) For the MLN2037F NPN silicon RF power transistor at 1 GHz:

$$\begin{aligned}
 Z_0 &:= 50 \quad \Omega \\
 S_{11} &:= 0.8128 \cdot e^{j \cdot 156 \cdot \frac{\pi}{180}} & S_{12} &:= 0.0944 \cdot e^{j \cdot 63 \cdot \frac{\pi}{180}} \\
 S_{21} &:= 1.81 \cdot e^{j \cdot 55 \cdot \frac{\pi}{180}} & S_{22} &:= 0.3801 \cdot e^{j \cdot -136 \cdot \frac{\pi}{180}}
 \end{aligned}$$

$$\Delta := S_{11} \cdot S_{22} - S_{12} \cdot S_{21} \quad \boxed{|\Delta| = 0.37328} \quad \leq 1, \text{ good}$$

$$K := \frac{1 - (|S_{11}|)^2 - (|S_{22}|)^2 + (|\Delta|)^2}{2 |S_{12} \cdot S_{21}|} \quad \boxed{K = 0.978} \quad \leq 1, \text{ bad}$$

Stability Conditions are NOT met at 1 GHz.

What happens to the load and source reflection coefficient equations?

$$B_1 := 1 + (|S_{11}|)^2 - (|S_{22}|)^2 - (|\Delta|)^2 \quad B_1 = 1.377$$

$$B_2 := 1 + (|S_{22}|)^2 - (|S_{11}|)^2 - (|\Delta|)^2 \quad B_2 = 0.344$$

$$C_1 := S_{11} - \Delta \cdot \overline{S_{22}} \quad |C_1| = 0.689 \quad \arg(C_1) \cdot \frac{180}{\pi} = 161.4 \quad \text{deg}$$

$$C_2 := S_{22} - \Delta \cdot \overline{S_{11}} \quad |C_2| = 0.176 \quad \arg(C_2) \cdot \frac{180}{\pi} = -84.6 \quad \text{deg}$$

$$\Gamma_{Ms_plus} := \frac{B_1 + \sqrt{B_1^2 - 4 \cdot (|C_1|)^2}}{2 \cdot C_1} \quad \boxed{|\Gamma_{Ms_plus}| = 1}$$

$$\arg(\Gamma_{Ms_plus}) \cdot \frac{180}{\pi} = -158.4 \quad \text{deg}$$

$$\Gamma_{Ms_minus} := \frac{B_1 - \sqrt{B_1^2 - 4 \cdot (|C_1|)^2}}{2 \cdot C_1} \quad \boxed{|\Gamma_{Ms_minus}| = 1}$$

$$\arg(\Gamma_{Ms_minus}) \cdot \frac{180}{\pi} = -164.3 \quad \text{deg}$$

$$\Gamma_{ML_plus} := \frac{B2 + \sqrt{B2^2 - 4 \cdot (|C2|)^2}}{2 \cdot C2}$$

$$|\Gamma_{ML_plus}| = 1$$

$$\arg(\Gamma_{ML_plus}) \cdot \frac{180}{\pi} = 96.3 \quad \text{deg}$$

$$\Gamma_{ML_minus} := \frac{B2 - \sqrt{B2^2 - 4 \cdot (|C2|)^2}}{2 \cdot C2}$$

$$|\Gamma_{ML_minus}| = 1$$

$$\arg(\Gamma_{ML_minus}) \cdot \frac{180}{\pi} = 72.9 \quad \text{deg}$$

Obviously, these load and source reflection coefficients are NOT useful (all the power gets reflected!).

2) For a *modified* lower $|S12|$ MLN2037F NPN silicon RF power transistor at 1 GHz where:

$$S12m := 0.08 \cdot e^{j \cdot 63 \cdot \frac{\pi}{180}}$$

$$\Delta m := S11 \cdot S22 - S12m \cdot S21$$

$$|\Delta m| = 0.35898 \quad < 1, \text{ good}$$

$$K_m := \frac{1 - (|S11|)^2 - (|S22|)^2 + (|\Delta m|)^2}{2 |S12m \cdot S21|}$$

$$|K_m| = 1.1179 \quad > 1, \text{ good}$$

Stability Conditions ARE met at 1 GHz.

Now what happens to the load and source reflection coefficient equations?

$$B1m := 1 + (|S11|)^2 - (|S22|)^2 - (|\Delta m|)^2$$

$$B1m = 1.387$$

$$B2m := 1 + (|S22|)^2 - (|S11|)^2 - (|\Delta m|)^2$$

$$B2m = 0.355$$

$$C1m := S11 - \Delta m \cdot \overline{S22}$$

$$|C1m| = 0.69$$

$$\arg(C1m) \cdot \frac{180}{\pi} = 160.5 \quad \text{deg}$$

$$C2m := S22 - \Delta m \cdot \overline{S11}$$

$$|C2m| = 0.162$$

$$\arg(C2m) \cdot \frac{180}{\pi} = -90 \quad \text{deg}$$

$$\Gamma_{\text{Msm_plus}} := \frac{B1m + \sqrt{B1m^2 - 4 \cdot (|C1m|)^2}}{2 \cdot C1m}$$

$$|\Gamma_{\text{Msm_plus}}| = 1.11037$$

$$\arg(\Gamma_{\text{Msm_plus}}) \cdot \frac{180}{\pi} = -160.5 \quad \text{deg}$$

$$Z_{\text{sm_plus}} := Z0 \cdot \left(\frac{1 - \Gamma_{\text{Msm_plus}}}{1 + \Gamma_{\text{Msm_plus}}} \right)$$

$$Z_{\text{sm_plus}} = -83.695 + 265.945i \quad \Omega$$

$$\Gamma_{\text{Msm_minus}} := \frac{B1m - \sqrt{B1m^2 - 4 \cdot (|C1m|)^2}}{2 \cdot C1m}$$

$$|\Gamma_{\text{Msm_minus}}| = 0.9006$$

$$\arg(\Gamma_{\text{Msm_minus}}) \cdot \frac{180}{\pi} = -160.5 \quad \text{deg}$$

$$Z_{\text{sm_minus}} := Z0 \cdot \left(\frac{1 - \Gamma_{\text{Msm_minus}}}{1 + \Gamma_{\text{Msm_minus}}} \right)$$

$$Z_{\text{sm_minus}} = 83.695 + 265.945i \quad \Omega$$

$$\Gamma_{\text{MLm_plus}} := \frac{B2m + \sqrt{B2m^2 - 4 \cdot (|C2m|)^2}}{2 \cdot C2m}$$

$$|\Gamma_{\text{MLm_plus}}| = 1.54164$$

$$\arg(\Gamma_{\text{MLm_plus}}) \cdot \frac{180}{\pi} = 90 \quad \text{deg}$$

$$Z_{\text{Lm_plus}} := Z0 \cdot \left(\frac{1 - \Gamma_{\text{MLm_plus}}}{1 + \Gamma_{\text{MLm_plus}}} \right)$$

$$Z_{\text{Lm_plus}} = -20.39 - 45.667i \quad \Omega$$

$$\Gamma_{\text{MLm_minus}} := \frac{B2m - \sqrt{B2m^2 - 4 \cdot (|C2m|)^2}}{2 \cdot C2m}$$

$$|\Gamma_{\text{MLm_minus}}| = 0.64866$$

$$\arg(\Gamma_{\text{MLm_minus}}) \cdot \frac{180}{\pi} = 90 \quad \text{deg}$$

$$Z_{\text{Lm_minus}} := Z0 \cdot \left(\frac{1 - \Gamma_{\text{MLm_minus}}}{1 + \Gamma_{\text{MLm_minus}}} \right)$$

$$Z_{\text{Lm_minus}} = 20.39 - 45.667i \quad \Omega$$

Note: The "-" solutions are useful as predicted. However, the "+" solutions are not useful (negative real resistances for corresponding Z_L and Z_s).

What is the maximum transducer gain for the modified transistor?

$$GT_{\max_m1} := \frac{1}{1 - (|\Gamma_{Msm_minus}|)^2} \cdot (|S_{21}|)^2 \cdot \frac{[1 - (|\Gamma_{MLm_minus}|)^2]}{(|1 - S_{22} \cdot \Gamma_{MLm_minus}|)^2}$$

OR

$$GT_{\max_m2} := \frac{|S_{21}|}{|S_{12m}|} \cdot (K_m - \sqrt{K_m^2 - 1})$$

$$\boxed{GT_{\max_m1} = 13.987}$$

$$\boxed{GT_{\max_m2} = 13.987}$$

$$\boxed{10 \cdot \log(GT_{\max_m1}) = 11.457} \text{ dB}$$

$$\boxed{10 \cdot \log(GT_{\max_m2}) = 11.457} \text{ dB}$$

Same answer!

What is the maximum stable (transducer) gain for the modified transistor?

$$G_{_MSG} := \frac{|S_{21}|}{|S_{12m}|}$$

$$\boxed{G_{_MSG} = 22.625}$$

$$\boxed{10 \cdot \log(G_{_MSG}) = 13.546} \text{ dB}$$

3.7 Operating and Available Power-Gain Circles

49

Operating Power-Gain Circles (G_p)

- commonly used for bilateral ($S_{12} \neq 0$) transistors
- G_p does NOT depend on Γ_S (or Z_S)
- useful for both unconditionally stable and potentially unstable transistors

G_p for Unconditionally stable case

$$G_p = |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{\left(1 - \left| \frac{S_{11} - \Delta \Gamma_L}{1 - S_{22} \Gamma_L} \right|^2\right) |1 - S_{22} \Gamma_L|^2} = |S_{21}|^2 g_p$$

So

$$g_p = \frac{G_p}{|S_{21}|^2} = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2 - |S_{11} - \Delta \Gamma_L|^2}$$
$$= \frac{1 - |\Gamma_L|^2}{1 - |S_{11}|^2 + |\Gamma_L|^2 (|S_{22}|^2 - |\Delta|^2) - 2 \operatorname{Re}(\Gamma_L C_2)}$$

where $\Delta = S_{11} S_{22} - S_{12} S_{21}$ and $C_2 = S_{22} - \Delta S_{11}^*$

Both G_p and g_p are real numbers.

Appendix G shows that the equation defining circles of constant g_p on the Γ_L plane is

$$|\Gamma_L - C_p| = r_p$$

Center of circle $\equiv C_p = \frac{g_p C_2^*}{1 + g_p (|S_{22}|^2 - |\Delta|^2)}$ a complex #

radius of circle $\equiv r_p = \frac{[1 - 2K |S_{12} S_{21}| g_p + |S_{12} S_{21}|^2 g_p^2]^{1/2}}{|1 + g_p (|S_{22}|^2 - |\Delta|^2)|}$ Real #

Notes: C_p is always equal to C_2^*
If r_p is imaginary, pick lower G_p

At what value of Γ_L does the maximum G_p occur?

$\Rightarrow$ Maximum G_p occurs when $r_p = 0$

This leads to $g_{p,\max} = \frac{1}{|S_{12} S_{21}|} (K - \sqrt{K^2 - 1})$

and $G_{p,\max} = |S_{21}|^2 g_{p,\max} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1})$
 $= G_{T,\max}$ (as expected!)

To get Γ_L , use the equation for C_p w/ $g_{p,\max}$ yielding

$$\Gamma_L = \Gamma_{ML} = C_{p,\max} = \frac{g_{p,\max} C_2^*}{1 + g_{p,\max} (|S_{22}|^2 - |\Delta|^2)}$$

Lowest gain? $g_p = G_p = 0$

Occurs when $|\Gamma_L| = 1$ (all power reflected from load)

Notes: * $\Gamma_{L,max} = \Gamma_{ML}$ occur where $g_{p,max} = \frac{G_{p,max}}{|S_{21}|^2}$

* Maximum output power when $\Gamma_S = \Gamma_{IN}^*$

where $P_{IN} = P_{AVS}$. Then, $\Gamma_S = \Gamma_{MS}$ and

$$G_{p,max} = G_{T,max}$$

Procedure:

1) Select a value of G_p (helps to calculate $G_{p,max} = G_{T,max}$).

2) Calculate corresponding g_p , C_p , & r_p .
Plot on Γ_L Smith chart.

3) Select desired Γ_L on G_p circle

Note: For selected Γ_L , maximum output power is obtained when $\Gamma_S = \Gamma_{IN}^*$.


Then, this $G_p = G_T$. ↑
depends on Γ_L

* Another consideration for selecting Γ_L is the output VSWR, $VSWR_{out}$.

It is desirable to keep $VSWR_{out}$ as low as possible. The input

VSWR, $VSWR_{IN} = 1$ w/ $\Gamma_S = \Gamma_{IN}^*$

3.7 cont.

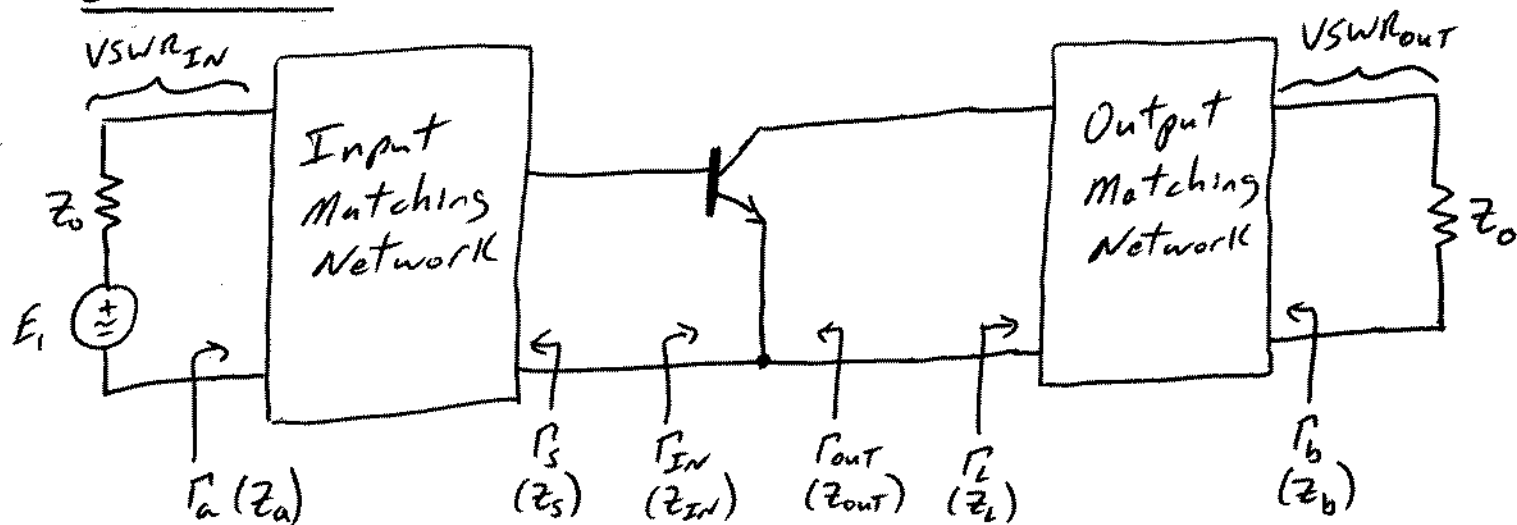

From Section 2.8,

$$VSWR_{IN} = \frac{1 + |\Gamma_a|}{1 - |\Gamma_a|} \quad \text{where } |\Gamma_a| = \left| \frac{\Gamma_{IN} - \Gamma_s^*}{1 - \Gamma_{IN}\Gamma_s} \right|$$

↳ For $\Gamma_s = \Gamma_{IN}^*$, $|\Gamma_a| = 0$ and $VSWR_{IN} = 1$

and

$$VSWR_{OUT} = \frac{1 + |\Gamma_b|}{1 - |\Gamma_b|} \quad \text{where } |\Gamma_b| = \left| \frac{\Gamma_{OUT} - \Gamma_L^*}{1 - \Gamma_{OUT}\Gamma_L} \right|$$

* If $VSWR_{OUT}$ is unacceptably high, choose another value of Γ_L on the G_p circle.

* Sometimes $\Gamma_s \neq \Gamma_{IN}^*$ and hence $VSWR_{IN} > 1$ must be accepted in order to lower $VSWR_{OUT}$.

Operating Power-Gain (GP) Circles for Unconditionally Stable case

For a modified MLN2037F (lower |S12|) RF power transistor at 1 GHz:

$$\begin{aligned} Z_0 &:= 50 \quad \Omega \\ S_{11} &:= 0.8128 \cdot e^{j \cdot 156 \cdot \frac{\pi}{180}} & S_{12m} &:= 0.08 \cdot e^{j \cdot 63 \cdot \frac{\pi}{180}} \\ S_{21} &:= 1.81 \cdot e^{j \cdot 55 \cdot \frac{\pi}{180}} & S_{22} &:= 0.3801 \cdot e^{j \cdot -136 \cdot \frac{\pi}{180}} \end{aligned}$$

$$\Delta := S_{11} \cdot S_{22} - S_{12m} \cdot S_{21} \quad \boxed{|\Delta| = 0.35898} \quad \leq 1, \text{ good}$$

$$K := \frac{1 - (|S_{11}|)^2 - (|S_{22}|)^2 + (|\Delta|)^2}{2 |S_{12m} \cdot S_{21}|} \quad \boxed{K = 1.1179} \quad \geq 1, \text{ good}$$

Stability Conditions ARE met at 1 GHz.

$$C_2 := S_{22} - \Delta \cdot \overline{S_{11}} \quad |C_2| = 0.162 \quad \arg(C_2) \cdot \frac{180}{\pi} = -90 \quad \text{deg}$$

What is the maximum stable (transducer) gain for the modified transistor?

$$G_{MSG} := \frac{|S_{21}|}{|S_{12m}|} \quad \boxed{G_{MSG} = 22.625} \quad \boxed{10 \cdot \log(G_{MSG}) = 13.546} \quad \text{dB}$$

Choose to plot GP for 10 dB. $GP := 10^{\frac{10}{10}}$ $GP = 10$

$$gP := \frac{GP}{(|S_{21}|)^2} \quad gP = 3.052$$

$$CP := \frac{gP \cdot \overline{C_2}}{1 + gP \cdot [(|S_{22}|)^2 - (|\Delta|)^2]} \quad \boxed{|CP| = 0.472} \quad \boxed{\arg(CP) \cdot \frac{180}{\pi} = 90} \quad \text{deg}$$

$$rP := \frac{[1 - 2 \cdot K \cdot |S_{12m} \cdot S_{21}| \cdot gP + (|S_{12m} \cdot S_{21}|)^2 \cdot gP^2]^{0.5}}{|1 + gP \cdot [(|S_{22}|)^2 - (|\Delta|)^2]|} \quad \boxed{rP = 0.434}$$

Plot $G_P = 10$ dB circle on Γ_L Smith Chart.

Select Point A on the Smith Chart. Here the normalized impedance

$z_L = 1.6 + j0.4$ corresponds to $\Gamma_L = 0.274 / 24.94^\circ$.

$$z_L := 1.6 + j \cdot 0.4 \quad \Gamma_L := \frac{z_L - 1}{z_L + 1} \quad |\Gamma_L| = 0.274 \quad \arg(\Gamma_L) \cdot \frac{180}{\pi} = 24.944 \quad \text{deg}$$

For maximum output power, select $\Gamma_S = \Gamma_{IN}^*$. Check input & output VSWR.

$$\Gamma_{IN} := S_{11} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \quad |\Gamma_{IN}| = 0.849 \quad \arg(\Gamma_{IN}) \cdot \frac{180}{\pi} = 155.188 \quad \text{deg}$$

$$\Gamma_S := \overline{\Gamma_{IN}} \quad |\Gamma_S| = 0.849 \quad \arg(\Gamma_S) \cdot \frac{180}{\pi} = -155.188 \quad \text{deg}$$

$$\Gamma_{a_mag} := \left| \frac{\Gamma_{IN} - \overline{\Gamma_S}}{1 - \Gamma_{IN} \cdot \Gamma_S} \right| \quad \text{VSWR}_{IN} := \frac{1 + \Gamma_{a_mag}}{1 - \Gamma_{a_mag}}$$

$$\Gamma_{a_mag} = 0$$

$$\text{VSWR}_{IN} = 1$$

$$\Gamma_{OUT} := S_{22} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S} \quad |\Gamma_{OUT}| = 0.496 \quad \arg(\Gamma_{OUT}) \cdot \frac{180}{\pi} = -84.24 \quad \text{deg}$$

$$\Gamma_{b_mag} := \left| \frac{\Gamma_{OUT} - \overline{\Gamma_L}}{1 - \Gamma_{OUT} \cdot \Gamma_L} \right| \quad \text{VSWR}_{OUT} := \frac{1 + \Gamma_{b_mag}}{1 - \Gamma_{b_mag}}$$

$$\Gamma_{b_mag} = 0.455$$

$$\text{VSWR}_{OUT} = 2.672$$

Check on gain values --> very good agreement.

$$G_T := \frac{1 - (|\Gamma_S|)^2}{(|1 - \Gamma_{IN} \cdot \Gamma_S|)^2} \cdot (|S_{21}|)^2 \cdot \frac{1 - (|\Gamma_L|)^2}{(|1 - S_{22} \cdot \Gamma_L|)^2}$$

$$|G_T| = 9.997$$

$$10 \cdot \log(|G_T|) = 9.999 \quad \text{dB}$$

$$G_P := \frac{1}{1 - (|\Gamma_{IN}|)^2} \cdot (|S_{21}|)^2 \cdot \frac{1 - (|\Gamma_L|)^2}{(|1 - S_{22} \cdot \Gamma_L|)^2}$$


$$|G_P| = 9.997$$

$$10 \cdot \log(|G_P|) = 9.999 \quad \text{dB}$$

$$G_A := \frac{1 - (|\Gamma_S|)^2}{(|1 - S_{11} \cdot \Gamma_S|)^2} \cdot (|S_{21}|)^2 \cdot \frac{1}{1 - (|\Gamma_{OUT}|)^2}$$

$$|G_A| = 12.612$$

$$10 \cdot \log(|G_A|) = 11.008 \quad \text{dB}$$

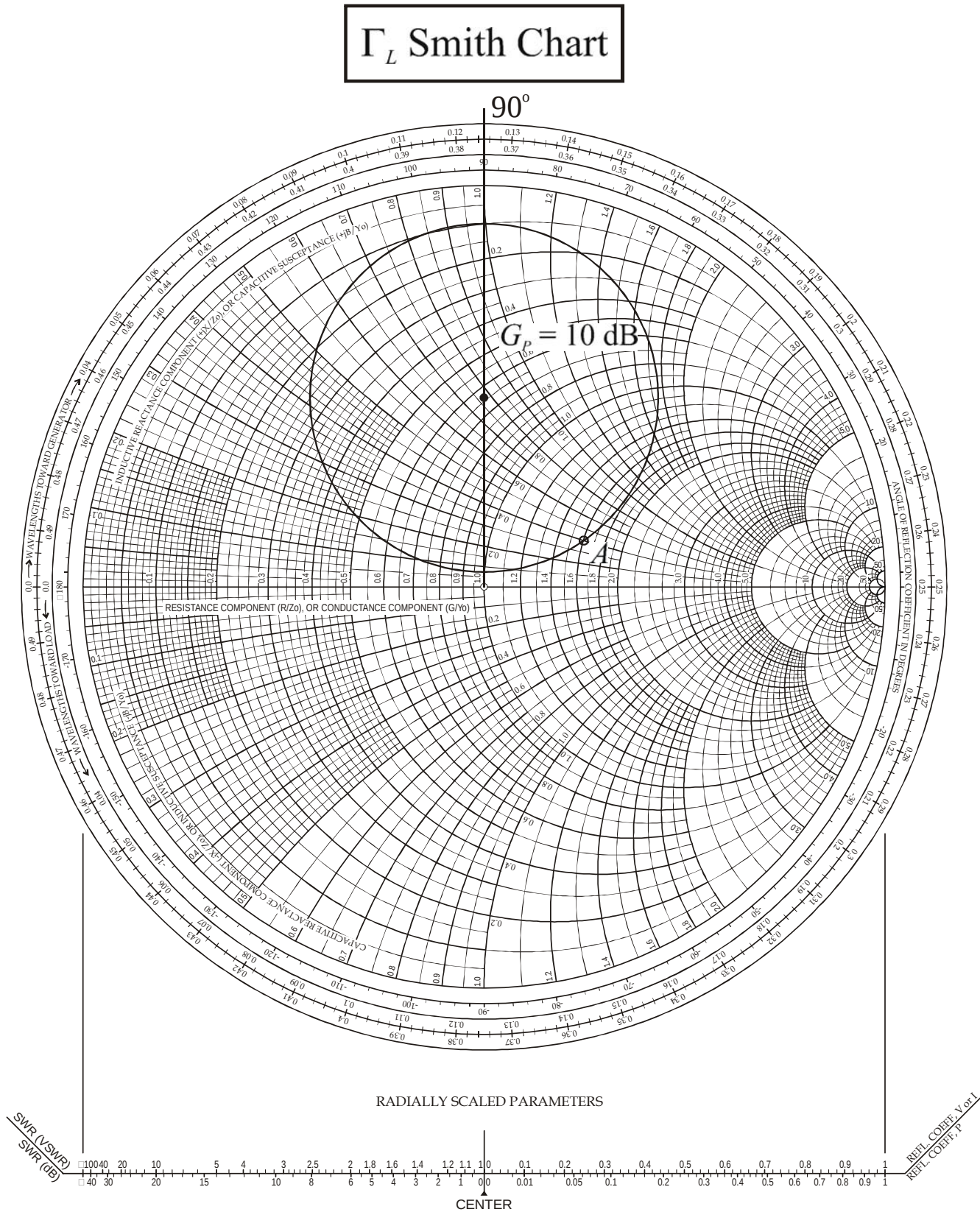

3.7 cont.Potentially unstable bilateral Case G_p Circles

- * G_p can be ∞ in this case
- * As a rule, choose $G_p < G_{msc} = \frac{|S_{21}|}{|S_{12}|}$ to get good stability and acceptable $VSWR_{IN}$ + $VSWR_{OUT}$.

Why? When $G_p > G_{msc}$, Γ_S +/or Γ_L get close to unstable regions and result in large $VSWR_{IN}$ + $VSWR_{OUT}$

Procedure

- 1) Select a value of G_p .
- 2) Calculate g_p , c_p , + r_p . Plot G_p circle on Γ_L Smith Chart.
- 3) Calculate and draw Output Stability Circle (see p. 218) on Γ_L Smith Chart
- 4) Select value of Γ_L on G_p circle that is in stable region (not too close to output stability circle!).
- 5) Calculate $\Gamma_{IN} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$ for this Γ_L .
- 6) Calculate and draw Input Stability Circle (see p. 218) on Γ_S Smith Chart. Is $\Gamma_S = \Gamma_{IN}^*$ in the stable region? Yes, let $\Gamma_S = \Gamma_{IN}^*$.

What if $\Gamma_S = \Gamma_{IN}^*$ is in the unstable region or too close to input stability circle for comfort?

↳ Choose Γ_S arbitrarily considering resulting VSWR_{IN} and output power.

What if $K > 1$ (good) and $|A| > 1$ (bad)?

Then, there is a $G_{p,min}$ (similar to $G_{T,min}$)

where $G_{p,min} = \frac{1}{|S_{12}S_{21}|} (K + \sqrt{K^2 - 1})$

and $G_{p,min} = \frac{|S_{21}|}{|S_{12}|} (K + \sqrt{K^2 - 1})$.

This is the minimum G_p in the stable region when $K > 1$ and $|A| > 1$. The corresponding Γ_L is

$$\Gamma_{L,min} = \frac{G_{p,min} C_2^*}{1 + G_{p,min} (|S_{22}|^2 - |A|^2)} = \Gamma_{ML}$$

↑
when "+" sign used

Note: G_p circles and the

Note: G_p circles and the Output Stability circle - will intersect the outside edge ($|\Gamma_L| = 1$) of the Γ_L Smith Chart at the same points.

3.7 cont.Available Power - Gain Circles (G_A)

- * For a given G_A , we will find the values of $\Gamma_S \Rightarrow G_A$ circle on Γ_S Smith Chart.
- * For a given $G_A + \Gamma_S$, $\Gamma_L = \Gamma_{out}^*$ will yield the maximum output power and $G_A = G_T$.
- * Later (Chapter 4), we will see that constant noise figure circles are also functions of Γ_S and plotted on Γ_S Smith Chart.

 G_A circles - Unconditionally stable bilateral case

$$G_A = |S_{21}|^2 \frac{1 - |\Gamma_S|^2}{\left(1 - \left|\frac{S_{22} - \Delta \Gamma_S}{1 - S_{11} \Gamma_S}\right|^2\right) |1 - S_{11} \Gamma_S|^2} = |S_{21}|^2 g_a$$

$$\text{So } g_a = \frac{G_A}{|S_{21}|^2} = \frac{1 - |\Gamma_S|^2}{1 - |S_{22}|^2 + |\Gamma_S|^2(|S_{11}|^2 - |\Delta|^2) - 2\text{Re}(\Gamma_S C_1)}$$

$$\text{where } C_1 = S_{11} - \Delta S_{22}^*$$

The defining equation for the G_A circles is

$$|\Gamma_S - C_a| = r_a$$

3.7 cont.

Center of G_A circle $\equiv C_a = \frac{g_a C_1^*}{1 + g_a (|S_{11}|^2 - |\Delta|^2)}$ $\leftarrow$ complex #

radius of G_A circle $\equiv r_a = \frac{[1 - 2K|S_{12}S_{21}|g_a + |S_{12}S_{21}|^2 g_a^2]^{1/2}}{|1 + g_a (|S_{11}|^2 - |\Delta|^2)|}$ $\leftarrow$ real #

Procedure

1) Select a value of G_A (helps to calculate $G_{A,max} = G_{T,max}$).

2) Calculate corresponding $g_a, C_a, + r_a$.
Plot on Γ_s Smith Chart.

3) Select desired Γ_s on G_A circle.

* Remember for a given Γ_s , maximum output power is obtained when $\Gamma_L = \Gamma_{out}^*$ which also gives $VSWR_{out} = 1$

* May want to check what $VSWR_{in}$ results from Γ_s selection. It may be unacceptably high. If so, choose another Γ_s on G_A circle.

3.7 cont.

G_A circles - Potentially unstable bilateral case

* G_A can be ∞ in this case.

* Again, as a rule, choose $G_A < G_{msb} = \frac{|S_{21}|}{|S_{12}|}$
to get good stability and acceptable
 $VSWR_{in} + VSWR_{out}$

Procedure

- 1) Select a value of G_A .
- 2) Calculate corresponding $g_a, C_a, + r_a$. Plot G_A circle on Γ_S Smith Chart.
- 3) Calculate and draw Input Stability Circle (see p. 218) on Γ_S Smith Chart.
- 4) Select value of Γ_S on G_A circle that is in the stable region (not too close to input stability circle!).
- 5) Calculate $\Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$ for this Γ_S .
- 6) Calculate and draw Output Stability Circle (see p. 218) on Γ_L Smith Chart. Is $\Gamma_L = \Gamma_{out}^*$ in the stable region? Yes, let $\Gamma_L = \Gamma_{out}^*$ to get maximum output power.

3.7 cont.

61

What if $\Gamma_L = \Gamma_{out}^*$ is in the unstable region
(or too close to output stability circle for comfort)?

↳ Choose Γ_L arbitrarily considering
resulting $VSWR_{out}$ and output power.