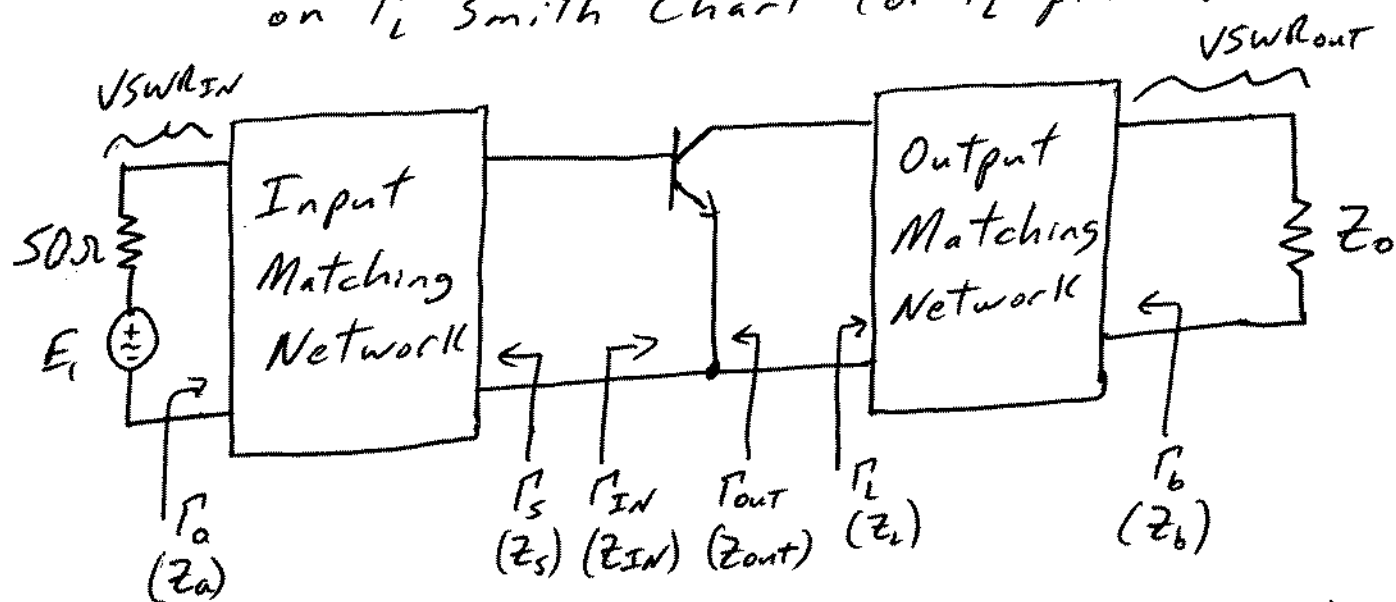


3.8 Constant VSWR Circles

* Maximum $VSWR_{IN}$ and $VSWR_{OUT}$ are usually part of amplifier design specifications.

* Can draw circles of constant $VSWR_{IN}$ on Γ_S Smith Chart (or Γ_S plane).

* Can draw circles of constant $VSWR_{OUT}$ on Γ_L Smith Chart (or Γ_L plane).



$$VSWR_{IN} = \frac{1 + |\Gamma_a|}{1 - |\Gamma_a|}$$

$$VSWR_{OUT} = \frac{1 + |\Gamma_b|}{1 - |\Gamma_b|}$$

$$|\Gamma_a| = \left| \frac{\Gamma_{IN} - \Gamma_S^*}{1 - \Gamma_{IN} \Gamma_S} \right|$$

$$|\Gamma_b| = \left| \frac{\Gamma_{OUT} - \Gamma_L^*}{1 - \Gamma_{OUT} \Gamma_L} \right|$$

↑
 Γ_a & Γ_S related
 by bilinear transformation

⇓
 Circle on Γ_S plane

↑
 Γ_L & Γ_b related
 by bilinear transformation

⇓
 Circle on Γ_L plane

VSWR_{IN} (or $|\Gamma_a|$) Circle on Γ_s plane

Circle equation $|\Gamma_s - C_{Vi}| = r_{Vi}$
for VSWR_{IN}

Center of VSWR_{IN} Circle $\equiv C_{Vi} = \frac{\Gamma_{IN}^* (1 - |\Gamma_a|^2)}{1 - |\Gamma_a \Gamma_{IN}|^2}$

$= \frac{\Gamma_{IN}^* (1 - |\Gamma_a|^2)}{1 - |\Gamma_a|^2 |\Gamma_{IN}|^2}$ or complex #

Radius of VSWR_{IN} Circle $\equiv r_{Vi} = \frac{|\Gamma_a| (1 - |\Gamma_{IN}|^2)}{1 - |\Gamma_a \Gamma_{IN}|^2}$

$= \frac{|\Gamma_a| (1 - |\Gamma_{IN}|^2)}{1 - |\Gamma_a|^2 |\Gamma_{IN}|^2}$ or real #

How do we get $|\Gamma_a|$?

For a given VSWR_{IN}, $|\Gamma_a| = \frac{\text{VSWR}_{IN} - 1}{\text{VSWR}_{IN} + 1}$

What about VSWR_{IN} = 1? (a point)

$\hookrightarrow \Gamma_s = \Gamma_{IN}^*$ and $|\Gamma_a| = 0$

So $C_{Vi}|_{|\Gamma_a|=0} = \Gamma_{IN}^*$

$r_{Vi}|_{|\Gamma_a|=0} = 0$

VSWR_{IN} circle reduces to a point at

$\Gamma_s = \Gamma_{IN}^*$

VSWR_{out} (or $|\Gamma_b|$) Circle on Γ_L plane

Circle Equation for $VSWR_{out}$ $|\Gamma_L - C_{V_0}| = r_{V_0}$

Center of VSWR_{out} Circle $\equiv C_{V_0} = \frac{\Gamma_{out}^* (1 - |\Gamma_b|^2)}{1 - |\Gamma_b| |\Gamma_{out}|^2}$

$= \frac{\Gamma_{out}^* (1 - |\Gamma_b|)}{1 - |\Gamma_b|^2 |\Gamma_{out}|^2}$ ← complex #

Radius of VSWR_{out} Circle $\equiv r_{V_0} = \frac{|\Gamma_b| (1 - |\Gamma_{out}|^2)}{1 - |\Gamma_b| |\Gamma_{out}|^2}$

$= \frac{|\Gamma_b| (1 - |\Gamma_{out}|^2)}{1 - |\Gamma_b|^2 |\Gamma_{out}|^2}$

How do we get $|\Gamma_b|$?

For a given (selected) VSWR_{out}, $|\Gamma_b| = \frac{VSWR_{out} - 1}{VSWR_{out} + 1}$

What about VSWR_{out} = 1?

↳ $\Gamma_L = \Gamma_{out}^*$ and $|\Gamma_b| = 0$

So $C_{V_0} |_{|\Gamma_b|=0} = \Gamma_{out}^*$
 $r_{V_0} |_{|\Gamma_b|=0} = 0$ } VSWR_{out} circle reduces to a point at $\Gamma_L = \Gamma_{out}^*$

VSWR Circles applied to the unconditionally stable modified MLN2037F RF power transistor at 1 GHz where $G_P = 10$ dB.

In the prior example, we achieved a $G_P = G_T = 10$ dB gain with $VSWR_{IN} = 1$ (let $\Gamma_S = \Gamma_{IN}^*$) but $VSWR_{OUT} = 2.672$. Here, we'll try reducing $VSWR_{OUT}$ to < 2 by allowing for a higher $VSWR_{IN}$ (new Γ_S).

$$\begin{aligned} Z_0 &:= 50 \quad \Omega \\ S_{11} &:= 0.8128 \cdot e^{j \cdot 156 \cdot \frac{\pi}{180}} & S_{12m} &:= 0.08 \cdot e^{j \cdot 63 \cdot \frac{\pi}{180}} \\ S_{21} &:= 1.81 \cdot e^{j \cdot 55 \cdot \frac{\pi}{180}} & S_{22} &:= 0.3801 \cdot e^{j \cdot -136 \cdot \frac{\pi}{180}} \end{aligned}$$

$$\Delta := S_{11} \cdot S_{22} - S_{12m} \cdot S_{21} \quad \boxed{|\Delta| = 0.35898} \quad \leq 1, \text{ good}$$

$$K := \frac{1 - (|S_{11}|)^2 - (|S_{22}|)^2 + (|\Delta|)^2}{2 |S_{12m} \cdot S_{21}|} \quad \boxed{K = 1.1179} \quad \geq 1, \text{ good}$$

Stability Conditions ARE met at 1 GHz.

$$C_2 := S_{22} - \Delta \cdot \overline{S_{11}} \quad |C_2| = 0.162 \quad \arg(C_2) \cdot \frac{180}{\pi} = -90 \quad \text{deg}$$

$$G_{MSG} := \frac{|S_{21}|}{|S_{12m}|} \quad \boxed{G_{MSG} = 22.625} \quad \boxed{10 \cdot \log(G_{MSG}) = 13.546} \quad \text{dB}$$

Choose to plot GP for 10 dB. $GP := 10^{\frac{10}{10}} \quad GP = 10$

$$gP := \frac{GP}{(|S_{21}|)^2} \quad gP = 3.052$$

$$CP := \frac{gP \cdot \overline{C_2}}{1 + gP \cdot [(|S_{22}|)^2 - (|\Delta|)^2]} \quad \boxed{|CP| = 0.472} \quad \boxed{\arg(CP) \cdot \frac{180}{\pi} = 90} \quad \text{deg}$$

$$rP := \frac{[1 - 2 \cdot K \cdot |S_{12m} \cdot S_{21}| \cdot gP + (|S_{12m} \cdot S_{21}|)^2 \cdot gP^2]^{0.5}}{|1 + gP \cdot [(|S_{22}|)^2 - (|\Delta|)^2]|} \quad \boxed{rP = 0.434}$$

Plot $G_P = 10$ dB circle on Γ_L Smith Chart.

Again select Point A on the Γ_L Smith Chart. Here the normalized impedance

$z_L = 1.6 + j0.4$ corresponds to $\Gamma_L = 0.274 / 24.94^\circ$.

$$z_L := 1.6 + j \cdot 0.4 \quad \Gamma_L := \frac{z_L - 1}{z_L + 1} \quad |\Gamma_L| = 0.274 \quad \boxed{\arg(\Gamma_L) \cdot \frac{180}{\pi} = 24.944} \text{ deg}$$

For maximum output power, select $\Gamma_S = \Gamma_{IN}^*$. Check input & output VSWR.

$$\Gamma_{IN} := S_{11} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \quad |\Gamma_{IN}| = 0.849 \quad \boxed{\arg(\Gamma_{IN}) \cdot \frac{180}{\pi} = 155.188} \text{ deg}$$

$$\Gamma_S := \overline{\Gamma_{IN}} \quad |\Gamma_S| = 0.849 \quad \boxed{\arg(\Gamma_S) \cdot \frac{180}{\pi} = -155.188} \text{ deg}$$

$$\Gamma_{a_mag} := \left| \frac{\Gamma_{IN} - \overline{\Gamma_S}}{1 - \Gamma_{IN} \cdot \Gamma_S} \right| \quad VSWR_{IN} := \frac{1 + \Gamma_{a_mag}}{1 - \Gamma_{a_mag}} \quad \boxed{VSWR_{IN} = 1}$$

$$\Gamma_{OUT} := S_{22} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S} \quad |\Gamma_{OUT}| = 0.496 \quad \boxed{\arg(\Gamma_{OUT}) \cdot \frac{180}{\pi} = -84.24} \text{ deg}$$

$$\Gamma_{b_mag} := \left| \frac{\Gamma_{OUT} - \overline{\Gamma_L}}{1 - \Gamma_{OUT} \cdot \Gamma_L} \right| \quad VSWR_{OUT} := \frac{1 + \Gamma_{b_mag}}{1 - \Gamma_{b_mag}} \quad \boxed{VSWR_{OUT} = 2.672}$$

Let's shoot for $VSWR_{IN} = \underline{1.666}$ and see what we can get for $VSWR_{OUT}$.

$$\Gamma_{a_1666} := \frac{1.666 - 1}{1.666 + 1} \quad \boxed{\Gamma_{a_1666} = 0.2498}$$

$$C_{vi1666} := \frac{\overline{\Gamma_{IN}} \cdot (1 - \Gamma_{a_1666}^2)}{1 - \Gamma_{a_1666}^2 \cdot (|\Gamma_{IN}|)^2} \quad r_{vi1666} := \frac{\Gamma_{a_1666} \cdot [1 - (|\Gamma_{IN}|)^2]}{1 - \Gamma_{a_1666}^2 \cdot (|\Gamma_{IN}|)^2}$$

$$\boxed{|C_{vi1666}| = 0.83354} \quad \boxed{\arg(C_{vi1666}) \cdot \frac{180}{\pi} = -155.188} \text{ deg} \quad \boxed{r_{vi1666} = 0.073}$$

Plot $VSWR_{IN} = 1.666$ circle on Γ_S Smith Chart along with $\Gamma_S = \Gamma_{IN}^*$ point.

Select Γ_S values on the $VSWR_{IN} = 1.666$ circle at the points A-D (placed at 90° intervals on circle) and evaluate how the VSWRs change.

$$\Gamma_{SA} := C_{vi1666} + r_{vi1666} \cdot e^{j \cdot 0} \quad \boxed{|\Gamma_{SA}| = 0.768} \quad \boxed{\arg(\Gamma_{SA}) \cdot \frac{180}{\pi} = -152.901} \text{ deg}$$

$$\Gamma_{OUTA} := S_{22} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_{SA}}{1 - S_{11} \cdot \Gamma_{SA}} \quad \boxed{|\Gamma_{OUTA}| = 0.41} \quad \boxed{\arg(\Gamma_{OUTA}) \cdot \frac{180}{\pi} = -92.56} \text{ deg}$$

$$\Gamma_{aA} := \left| \frac{\Gamma_{IN} - \overline{\Gamma_{SA}}}{1 - \Gamma_{IN} \cdot \Gamma_{SA}} \right| \quad VSWR_{INA} := \frac{1 + \Gamma_{aA}}{1 - \Gamma_{aA}} \quad \boxed{VSWR_{INA} = 1.666}$$

$$\Gamma_{bA} := \left| \frac{\Gamma_{OUTA} - \overline{\Gamma_L}}{1 - \Gamma_{OUTA} \cdot \Gamma_L} \right| \quad VSWR_{OUTA} := \frac{1 + \Gamma_{bA}}{1 - \Gamma_{bA}} \quad \boxed{VSWR_{OUTA} = 2.406}$$

$$\Gamma_{SB} := C_{vi1666} + r_{vi1666} \cdot e^{j \cdot \frac{\pi}{2}} \quad \boxed{|\Gamma_{SB}| = 0.806} \quad \boxed{\arg(\Gamma_{SB}) \cdot \frac{180}{\pi} = -159.907} \text{ deg}$$

$$\Gamma_{OUTB} := S_{22} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_{SB}}{1 - S_{11} \cdot \Gamma_{SB}} \quad \boxed{|\Gamma_{OUTB}| = 0.52} \quad \boxed{\arg(\Gamma_{OUTB}) \cdot \frac{180}{\pi} = -96.13} \text{ deg}$$

$$\Gamma_{aB} := \left| \frac{\Gamma_{IN} - \overline{\Gamma_{SB}}}{1 - \Gamma_{IN} \cdot \Gamma_{SB}} \right| \quad VSWR_{INB} := \frac{1 + \Gamma_{aB}}{1 - \Gamma_{aB}} \quad \boxed{VSWR_{INB} = 1.666}$$

$$\Gamma_{bB} := \left| \frac{\Gamma_{OUTB} - \overline{\Gamma_L}}{1 - \Gamma_{OUTB} \cdot \Gamma_L} \right| \quad VSWR_{OUTB} := \frac{1 + \Gamma_{bB}}{1 - \Gamma_{bB}} \quad \boxed{VSWR_{OUTB} = 3.188}$$

$$\Gamma_{SC} := C_{vi1666} + r_{vi1666} \cdot e^{j \cdot \pi} \quad \boxed{|\Gamma_{SC}| = 0.9} \quad \boxed{\arg(\Gamma_{SC}) \cdot \frac{180}{\pi} = -157.138} \text{ deg}$$

$$\Gamma_{OUTC} := S_{22} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_{SC}}{1 - S_{11} \cdot \Gamma_{SC}} \quad \boxed{|\Gamma_{OUTC}| = 0.6} \quad \boxed{\arg(\Gamma_{OUTC}) \cdot \frac{180}{\pi} = -81.73} \text{ deg}$$

$$\Gamma_{aC} := \left| \frac{\Gamma_{IN} - \overline{\Gamma_{SC}}}{1 - \Gamma_{IN} \cdot \Gamma_{SC}} \right| \quad VSWR_{INC} := \frac{1 + \Gamma_{aC}}{1 - \Gamma_{aC}} \quad \boxed{VSWR_{INC} = 1.666}$$


$$\Gamma_{bC} := \left| \frac{\Gamma_{OUTC} - \overline{\Gamma_L}}{1 - \Gamma_{OUTC} \cdot \Gamma_L} \right| \quad VSWR_{OUTC} := \frac{1 + \Gamma_{bC}}{1 - \Gamma_{bC}} \quad \boxed{VSWR_{OUTC} = 3.395}$$

$$\begin{aligned} \Gamma_{SD} &:= C_{vi1666} + r_{vi1666} \cdot e^{j \cdot 1.5\pi} & |\Gamma_{SD}| &= 0.867 & \arg(\Gamma_{SD}) \cdot \frac{180}{\pi} &= -150.802 \text{ deg} \\ \Gamma_{OUTD} &:= S_{22} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_{SD}}{1 - S_{11} \cdot \Gamma_{SD}} & |\Gamma_{OUTD}| &= 0.42 & \arg(\Gamma_{OUTD}) \cdot \frac{180}{\pi} &= -74.81 \text{ deg} \\ \Gamma_{aD} &:= \left| \frac{\Gamma_{IN} - \overline{\Gamma_{SD}}}{1 - \Gamma_{IN} \cdot \Gamma_{SD}} \right| & VSWR_{IND} &:= \frac{1 + \Gamma_{aD}}{1 - \Gamma_{aD}} & VSWR_{IND} &= 1.666 \\ \Gamma_{bD} &:= \left| \frac{\Gamma_{OUTD} - \overline{\Gamma_L}}{1 - \Gamma_{OUTD} \cdot \Gamma_L} \right| & VSWR_{OUTD} &:= \frac{1 + \Gamma_{bD}}{1 - \Gamma_{bD}} & VSWR_{OUTD} &= 2.073 \end{aligned}$$

The Γ_S values on the $VSWR_{IN} = 1.666$ circle near point D yielded the lowest $VSWR_{OUT}$. Now, iteratively search on either side of point D for the best Γ_S .

$$\begin{aligned} \Gamma_{SE} &:= C_{vi1666} + r_{vi1666} \cdot e^{j \cdot 1.574\pi} & |\Gamma_{SE}| &= 0.851 & \arg(\Gamma_{SE}) \cdot \frac{180}{\pi} &= -150.365 \text{ deg} \\ \Gamma_{OUTE} &:= S_{22} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_{SE}}{1 - S_{11} \cdot \Gamma_{SE}} & |\Gamma_{OUTE}| &= 0.41 & \arg(\Gamma_{OUTE}) \cdot \frac{180}{\pi} &= -77.27 \text{ deg} \\ \Gamma_{aE} &:= \left| \frac{\Gamma_{IN} - \overline{\Gamma_{SE}}}{1 - \Gamma_{IN} \cdot \Gamma_{SE}} \right| & VSWR_{INE} &:= \frac{1 + \Gamma_{aE}}{1 - \Gamma_{aE}} & VSWR_{INE} &= 1.666 \\ \Gamma_{bE} &:= \left| \frac{\Gamma_{OUTE} - \overline{\Gamma_L}}{1 - \Gamma_{OUTE} \cdot \Gamma_L} \right| & VSWR_{OUTE} &:= \frac{1 + \Gamma_{bE}}{1 - \Gamma_{bE}} & VSWR_{OUTE} &= 2.0532 \end{aligned}$$

We allowed $VSWR_{IN} = 1.666$ and achieved a $VSWR_{OUT} = 2.0532$ (not quite < 2).

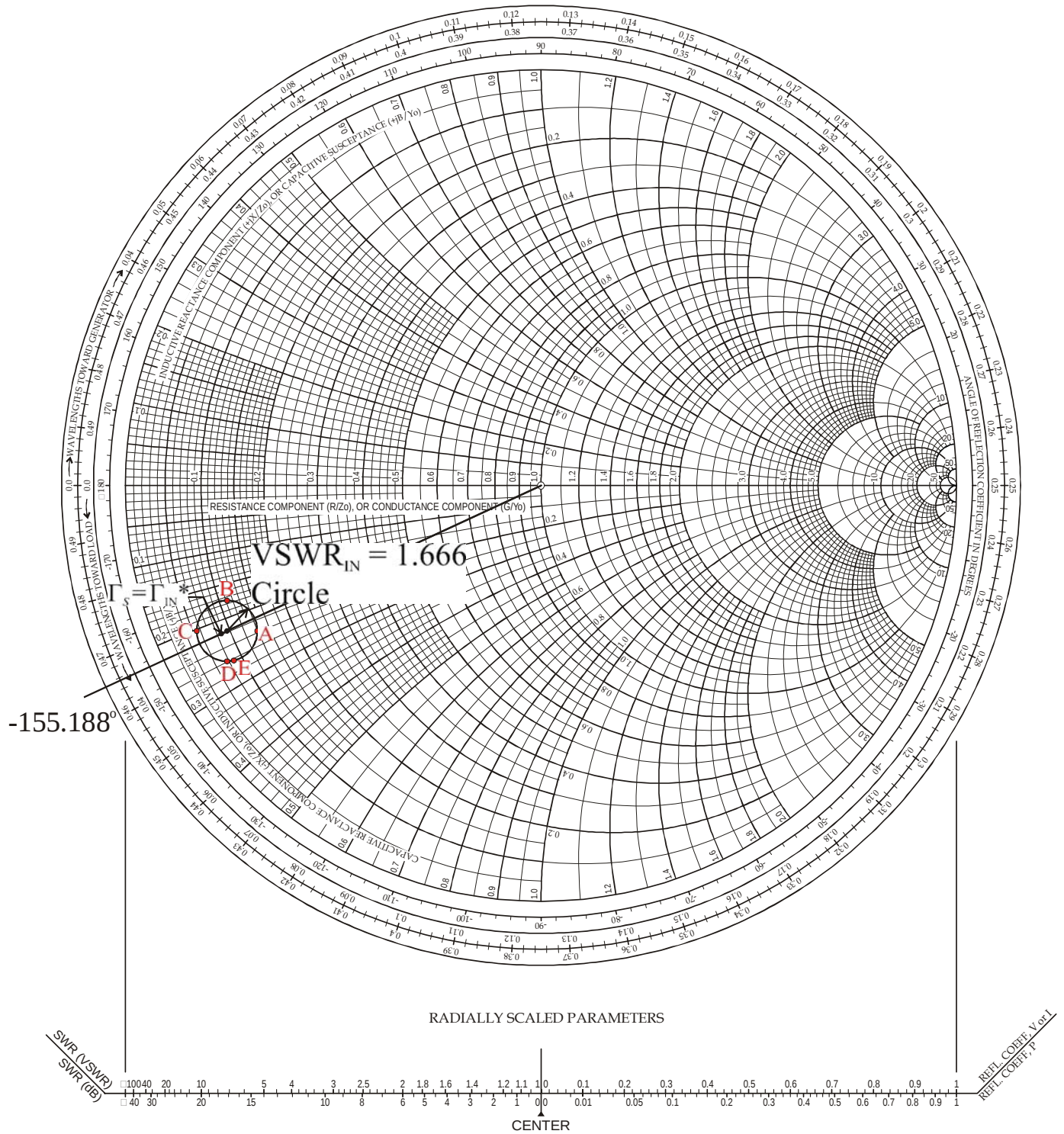Γ_s Smith Chart

How are the gains with the new Γ_S value at point E?

With $\Gamma_S = \Gamma_{IN}^*$, we had $G_T = G_P = 9.999$ dB and $G_A = 11.008$ dB.

$$G_{TE} := \frac{1 - (|\Gamma_{SE}|)^2}{(|1 - \Gamma_{IN} \cdot \Gamma_{SE}|)^2} \cdot (|S_{21}|)^2 \cdot \frac{1 - (|\Gamma_L|)^2}{(|1 - S_{22} \cdot \Gamma_L|)^2}$$

$$|G_{TE}| = 9.373$$

$$\boxed{10 \cdot \log(|G_{TE}|) = 9.719} \text{ dB}$$

$$G_P := \frac{1}{1 - (|\Gamma_{IN}|)^2} \cdot (|S_{21}|)^2 \cdot \frac{1 - (|\Gamma_L|)^2}{(|1 - S_{22} \cdot \Gamma_L|)^2}$$

$$|G_P| = 9.997$$

$$\boxed{10 \cdot \log(|G_P|) = 9.999} \text{ dB}$$

$$G_A := \frac{1 - (|\Gamma_{SE}|)^2}{(|1 - S_{11} \cdot \Gamma_{SE}|)^2} \cdot (|S_{21}|)^2 \cdot \frac{1}{1 - (|\Gamma_{OUT}|)^2}$$

$$|G_A| = 10.639$$

$$\boxed{10 \cdot \log(|G_A|) = 10.269} \text{ dB}$$

As expected, G_P is unchanged.

However, G_T decreased by 0.28 dB and G_A decreased by 0.739 dB.

Pretty minimal changes for a substantial improvement in $VSWR_{OUT}$ albeit at the cost of $VSWR_{IN}$ increasing to 1.666.

3.8 cont.

Next, note that $\Gamma_{out} = \frac{S_{22} - \Delta \Gamma_S}{1 - S_{11} \Gamma_S}$

$$\text{and } \Gamma_S = \frac{S_{22} - \Gamma_{out}}{\Delta - S_{11} \Gamma_{out}}$$

are related by a bilinear transformation. Therefore, it is possible to map circles of constant G_A on the Γ_S plane into circles on the Γ_{out} plane and in turn onto circles on the Γ_L plane where $\Gamma_L = \Gamma_{out}^*$

For a G_A circle, $|\Gamma_S - C_A| = r_A$, where

$$C_A = \frac{g_A C_1^*}{1 + g_A (|S_{11}|^2 - |\Delta|^2)}$$

$$r_A = \frac{[1 - 2K |S_{12} S_{21}| g_A + |S_{12} S_{21}|^2 g_A^2]^{1/2}}{|1 + g_A (|S_{11}|^2 - |\Delta|^2)|}$$

$$\text{w/ } g_A = \frac{G_A}{|S_{21}|^2} \quad \text{and } C_1 = S_{11} - \Delta S_{22}^*$$

This maps into a circle on the Γ_{out} plane

$$|\Gamma_{out} - C_{out}| = r_{out} \quad \text{where}$$

$$C_{out} = \frac{(1 - S_{11} C_A)^* (S_{22} - \Delta C_A) - r_A^2 \Delta S_{11}^*}{|1 - S_{11} C_A|^2 - r_A^2 |S_{11}|^2} \quad \leftarrow \text{center (complex \#)}$$

$$r_{out} = \frac{r_A |S_{12} S_{21}|}{|1 - S_{11} C_A|^2 - r_A^2 |S_{11}|^2} \quad \leftarrow \text{radius (real \#)}$$

Then, on the Γ_L plane, we define the circle for

$$\Gamma_L = \Gamma_{out}^* \text{ as } |\Gamma_L - C_0| = r_0$$

$$\text{where } C_0 = C_{out}^* \text{ and } r_0 = r_{out}.$$

A similar process to take $\Gamma_{IN} = \frac{S_{11} - \Delta \Gamma_L}{1 - S_{22} \Gamma_L}$

$$\text{and } \Gamma_L = \frac{S_{11} - \Gamma_{IN}}{\Delta - S_{22} \Gamma_{IN}} \text{ (also related by bilinear trans.)}$$

and map circles of constant G_p on the Γ_L plane into circles on the Γ_{IN} plane and in turn onto circles on the Γ_S plane where $\Gamma_S = \Gamma_{IN}^*$.

For a G_p circle, $|\Gamma_L - C_p| = r_p$, where

$$C_p = \frac{g_p C_2^*}{1 + g_p (|S_{22}|^2 - |\Delta|^2)}$$

$$r_p = \frac{[1 - 2K |S_{12} S_{21}| g_p + |S_{12} S_{21}|^2 g_p^2]^{1/2}}{|1 + g_p (|S_{22}|^2 - |\Delta|^2)|}$$

$$\text{w/ } g_p = \frac{G_p}{|S_{21}|^2} \text{ and } C_2 = S_{22} - \Delta S_{11}^*$$

maps to a circle on the Γ_{IN} plane $|\Gamma_{IN} - C_{IN}| = r_{IN}$

where

$$C_{IN} = \frac{(1 - S_{22} C_p)^* (S_{11} - \Delta C_p) - r_p^2 \Delta S_{22}^*}{|1 - S_{22} C_p|^2 - r_p^2 |S_{22}|^2} \quad \text{center (complex \#)}$$

$$r_{IN} = \frac{r_p |S_{12} S_{21}|}{|1 - S_{22} C_p|^2 - r_p^2 |S_{22}|^2|} \quad \text{radius (real \#)}$$

3.8 cont.

Then, on the Γ_S plane, we define the circle for $\Gamma_S = \Gamma_{IN}^*$ as $|\Gamma_S - C_i| = r_i$

where $C_i = C_{IN}^*$ and $r_i = r_{IN}$.

These mappings of circles are useful for analyzing the trade-offs between gains (e.g., G_A and G_P), stability, and VSWRs.

In this example, we will map the $G_P = 10$ dB circle to the Γ_S plane, keeping our $VSWR_{IN} = 1.666$ circle for an unconditionally stable, modified MLN2037F RF power transistor at 1 GHz.

$$Z_0 := 50 \quad \Omega$$

$$S_{11} := 0.8128 \cdot e^{j \cdot 156 \cdot \frac{\pi}{180}} \quad S_{12m} := 0.08 \cdot e^{j \cdot 63 \cdot \frac{\pi}{180}}$$

$$S_{21} := 1.81 \cdot e^{j \cdot 55 \cdot \frac{\pi}{180}} \quad S_{22} := 0.3801 \cdot e^{j \cdot -136 \cdot \frac{\pi}{180}}$$

$$\Delta := S_{11} \cdot S_{22} - S_{12m} \cdot S_{21} \quad \boxed{|\Delta| = 0.35898} \quad \leq 1, \text{ good}$$

$$K := \frac{1 - (|S_{11}|)^2 - (|S_{22}|)^2 + (|\Delta|)^2}{2 |S_{12m} \cdot S_{21}|} \quad \boxed{K = 1.1179} \quad \geq 1, \text{ good}$$

Stability Conditions ARE met at 1 GHz.

$$C_2 := S_{22} - \Delta \cdot \overline{S_{11}} \quad |C_2| = 0.162 \quad \arg(C_2) \cdot \frac{180}{\pi} = -90 \quad \text{deg}$$

$$G_{MSG} := \frac{|S_{21}|}{|S_{12m}|} \quad \boxed{G_{MSG} = 22.625} \quad \boxed{10 \cdot \log(G_{MSG}) = 13.546} \quad \text{dB}$$

Choose to plot G_P for 10 dB. $G_P := 10^{\frac{10}{10}} \quad G_P = 10$

$$g_P := \frac{G_P}{(|S_{21}|)^2} \quad g_P = 3.052$$

$$C_P := \frac{g_P \cdot \overline{C_2}}{1 + g_P \cdot [(|S_{22}|)^2 - (|\Delta|)^2]} \quad \boxed{|C_P| = 0.472} \quad \boxed{\arg(C_P) \cdot \frac{180}{\pi} = 90} \quad \text{deg}$$

$$r_P := \frac{[1 - 2 \cdot K \cdot |S_{12m} \cdot S_{21}| \cdot g_P + (|S_{12m} \cdot S_{21}|)^2 \cdot g_P^2]^{0.5}}{|1 + g_P \cdot [(|S_{22}|)^2 - (|\Delta|)^2]|} \quad \boxed{r_P = 0.434}$$

C_P & r_P are for the Γ_L plane.

First, map the circle of Γ_L values where $GP = 10$ dB to the Γ_{IN} plane.

$$CIN := \frac{\overline{(1 - S22 \cdot CP)} \cdot (S11 - \Delta \cdot CP) - rP^2 \cdot \Delta \cdot \overline{S22}}{(|1 - S22 \cdot CP|)^2 - rP^2 \cdot (|S22|)^2}$$

$$rIN := \frac{rP \cdot |S12m \cdot S21|}{|(|1 - S22 \cdot CP|)^2 - rP^2 \cdot (|S22|)^2|}$$

$$|CIN| = 0.87157$$

$$\arg(CIN) \cdot \frac{180}{\pi} = 160.53137 \quad \text{deg}$$

$$rIN = 0.083262$$

Now, map the circle on the Γ_{IN} plane to the $\Gamma_S = \Gamma_{IN}^*$ plane and plot on the Γ_S Smith Chart.

$$Ci := \overline{CIN} \quad ri := rIN$$

$$|Ci| = 0.87157$$

$$\arg(Ci) \cdot \frac{180}{\pi} = -160.53137 \quad \text{deg}$$

$$ri = 0.083262$$

Select Point A on the Γ_L Smith Chart. Here the normalized impedance

$z_L = 1.6 + j0.4$ corresponds to $\Gamma_L = 0.274 / 24.94^\circ$.

$$z_L := 1.6 + j \cdot 0.4 \quad \Gamma_L := \frac{z_L - 1}{z_L + 1} \quad \boxed{|\Gamma_L| = 0.274} \quad \boxed{\arg(\Gamma_L) \cdot \frac{180}{\pi} = 24.944} \text{ deg}$$

For maximum output power, select $\Gamma_S = \Gamma_{IN}^*$. Check input & output VSWR.

$$\Gamma_{IN} := S_{11} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \quad \boxed{|\Gamma_{IN}| = 0.849} \quad \boxed{\arg(\Gamma_{IN}) \cdot \frac{180}{\pi} = 155.188} \text{ deg}$$

$$\Gamma_S := \overline{\Gamma_{IN}} \quad \boxed{|\Gamma_S| = 0.849} \quad \boxed{\arg(\Gamma_S) \cdot \frac{180}{\pi} = -155.188} \text{ deg}$$

$$\Gamma_{a_mag} := \left| \frac{\Gamma_{IN} - \overline{\Gamma_S}}{1 - \Gamma_{IN} \cdot \Gamma_S} \right| \quad VSWR_{IN} := \frac{1 + \Gamma_{a_mag}}{1 - \Gamma_{a_mag}} \quad \boxed{VSWR_{IN} = 1}$$

$$\Gamma_{OUT} := S_{22} + \frac{S_{12m} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S} \quad \boxed{|\Gamma_{OUT}| = 0.496} \quad \boxed{\arg(\Gamma_{OUT}) \cdot \frac{180}{\pi} = -84.24} \text{ deg}$$

$$\Gamma_{b_mag} := \left| \frac{\Gamma_{OUT} - \overline{\Gamma_L}}{1 - \Gamma_{OUT} \cdot \Gamma_L} \right| \quad VSWR_{OUT} := \frac{1 + \Gamma_{b_mag}}{1 - \Gamma_{b_mag}} \quad \boxed{VSWR_{OUT} = 2.672}$$

$$\Gamma_{a_1666} := \frac{1.666 - 1}{1.666 + 1} \quad \boxed{\Gamma_{a_1666} = 0.2498}$$

$$C_{vi1666} := \frac{\overline{\Gamma_{IN}} \cdot (1 - \Gamma_{a_1666}^2)}{1 - \Gamma_{a_1666}^2 \cdot (|\Gamma_{IN}|)^2} \quad r_{vi1666} := \frac{\Gamma_{a_1666} \cdot [1 - (|\Gamma_{IN}|)^2]}{1 - \Gamma_{a_1666}^2 \cdot (|\Gamma_{IN}|)^2}$$

$$\boxed{|C_{vi1666}| = 0.83354} \quad \boxed{\arg(C_{vi1666}) \cdot \frac{180}{\pi} = -155.188} \text{ deg} \quad \boxed{r_{vi1666} = 0.07302}$$

Plot $VSWR_{IN} = 1.666$ circle on Γ_S Smith Chart.

Γ_s Smith Chart

