

**In this example, we work on a low-noise microwave amplifier based on a M-Pulse Microwave MP42141 silicon npn BJT low noise microwave transistor operating at 2 GHz with  $V_{CE} = 10$  V and  $I_C = 5$  mA.**

\*\*\*\*\*

Transistor info:

$$Z_0 := 50 \quad \Omega \quad F_{dB} := 3.4 \quad dB \text{ (typical)} \quad R_n := 4 \quad \Omega \quad G_{opt} := 0.5 \cdot e^{j \cdot 160 \cdot \frac{\pi}{180}}$$

$$F := 10^{\frac{F_{dB}}{10}} \quad F = 2.188 \quad r_n := \frac{R_n}{Z_0} \quad r_n = 0.08$$

$$S_{11} := 0.561 \cdot e^{j \cdot 166.2 \cdot \frac{\pi}{180}} \quad S_{12} := 0.078 \cdot e^{j \cdot 32.6 \cdot \frac{\pi}{180}}$$

$$S_{21} := 1.894 \cdot e^{j \cdot 43.2 \cdot \frac{\pi}{180}} \quad S_{22} := 0.571 \cdot e^{j \cdot -63.6 \cdot \frac{\pi}{180}}$$

\*\*\*\*\*

Is the transistor stable at 2 GHz?

$$\Delta := S_{11} \cdot S_{22} - S_{12} \cdot S_{21} \quad |\Delta| = 0.19989 \quad < 1, \text{ good}$$

$$K := \frac{1 - (|S_{11}|)^2 - (|S_{22}|)^2 + (|\Delta|)^2}{2 |S_{12} \cdot S_{21}|} \quad K = 1.3511 \quad > 1, \text{ good}$$

Yes, stability Conditions ARE met at 2 GHz.

\*\*\*\*\*

Since the transistor is unconditionally stable at 2 GHz, we do NOT need to bother with calculating the input or output stability circles.

\*\*\*\*\*

The unilateral constant-gain circles should NOT apply since  $|S_{21}| = 0.078$ . However, let's check on the unilateral figure of merit to see if the unilateral case might be useful.

$$U := \frac{|S_{12}| \cdot |S_{21}| \cdot |S_{11}| \cdot |S_{22}|}{\left[1 - (|S_{11}|)^2\right] \left[1 - (|S_{22}|)^2\right]}$$

$$U = 0.102464$$

$$\frac{1}{(1+U)^2} = 0.82276$$

$$\frac{1}{(1-U)^2} = 1.24136$$

$$10 \cdot \log \left[ \frac{1}{(1+U)^2} \right] = -0.84729 \quad \text{dB}$$

$$10 \cdot \log \left[ \frac{1}{(1-U)^2} \right] = 0.93897 \quad \text{dB}$$

Unilateral design will NOT be very useful.

\*\*\*\*\*

The next possibility to examine is whether a simultaneous conjugate match (bilateral case) is viable for both good gain ( $G_{T,\max}$ ), VSWR, and low noise. Since we know the transistor is unconditionally stable, we'll start by calculating  $\Gamma_{MS} = \Gamma_{IN}^*$  and  $\Gamma_{ML} = \Gamma_{OUT}^*$ , choosing the "-" solutions.

$$B1 := 1 + (|S_{11}|)^2 - (|S_{22}|)^2 - (|\Delta|)^2$$

$$B1 = 0.949$$

$$B2 := 1 + (|S_{22}|)^2 - (|S_{11}|)^2 - (|\Delta|)^2$$

$$B2 = 0.971$$

$$C1 := S_{11} - \Delta \cdot \overline{S_{22}}$$

$$|C1| = 0.455$$

$$\arg(C1) \cdot \frac{180}{\pi} = 161.4 \quad \text{deg}$$

$$C2 := S_{22} - \Delta \cdot \overline{S_{11}}$$

$$|C2| = 0.467$$

$$\arg(C2) \cdot \frac{180}{\pi} = -68.2 \quad \text{deg}$$

$$\Gamma_{MS} := \frac{B1 - \sqrt{B1^2 - 4 \cdot (|C1|)^2}}{2 \cdot C1}$$

$$|\Gamma_{MS}| = 0.74761$$

$$\arg(\Gamma_{MS}) \cdot \frac{180}{\pi} = -161.4 \quad \text{deg}$$

$$\Gamma_{ML} := \frac{B2 - \sqrt{B2^2 - 4 \cdot (|C2|)^2}}{2 \cdot C2}$$

$$|\Gamma_{ML}| = 0.75297$$

$$\arg(\Gamma_{ML}) \cdot \frac{180}{\pi} = 68.2 \quad \text{deg}$$

How does  $\Gamma_{MS}$  do for noise performance? First, plot it on a Smith chart. Then, calculate and plot noise figure circles (in black) for  $F = 3.5, 3.7, \& 4$  dB.

$$F35 := 10^{\frac{3.5}{10}} \quad F35 = 2.239$$

$$N35 := \frac{F35 - F}{4 \cdot r_n} \cdot (|1 + \Gamma_{opt}|)^2 \quad N35 = 0.049$$

$$CF35 := \frac{\Gamma_{opt}}{1 + N35} \quad |CF35| = 0.47646 \quad \boxed{\arg(CF35) \cdot \frac{180}{\pi} = 160 \text{ deg}}$$

$$rF35 := \frac{1}{1 + N35} \cdot \sqrt{N35^2 + N35 \cdot [1 + (|\Gamma_{opt}|)^2]} \quad \boxed{rF35 = 0.2415}$$

$$F37 := 10^{\frac{3.7}{10}} \quad F37 = 2.344$$

$$N37 := \frac{F37 - F}{4 \cdot r_n} \cdot (|1 + \Gamma_{opt}|)^2 \quad N37 = 0.152$$

$$CF37 := \frac{\Gamma_{opt}}{1 + N37} \quad |CF37| = 0.4341 \quad \boxed{\arg(CF37) \cdot \frac{180}{\pi} = 160 \text{ deg}}$$

$$rF37 := \frac{1}{1 + N37} \cdot \sqrt{N37^2 + N37 \cdot [1 + (|\Gamma_{opt}|)^2]} \quad \boxed{rF37 = 0.4004}$$

$$F40 := 10^{\frac{4}{10}} \quad F40 = 2.512$$

$$N40 := \frac{F40 - F}{4 \cdot r_n} \cdot (|1 + \Gamma_{opt}|)^2 \quad N40 = 0.314$$

$$CF40 := \frac{\Gamma_{opt}}{1 + N40} \quad |CF40| = 0.3804 \quad \boxed{\arg(CF40) \cdot \frac{180}{\pi} = 160 \text{ deg}}$$

$$rF40 := \frac{1}{1 + N40} \cdot \sqrt{N40^2 + N40 \cdot [1 + (|\Gamma_{opt}|)^2]} \quad \boxed{rF40 = 0.5335}$$

As can be seen on the  $\Gamma_S$  Smith chart, the  $\Gamma_{MS}$  point is inside the  $F = 4$  dB noise figure circle. An exact calculation of  $F_{MS}$  is shown below.

$$F_{MS} := F + \frac{4 \cdot r_n \cdot (|\Gamma_{MS} - \Gamma_{opt}|)^2}{\left[1 - (|\Gamma_{MS}|)^2\right] \cdot \left[1 - (|\Gamma_{opt}|)^2\right]} \quad F_{MS} = 2.405$$

$$\boxed{10 \cdot \log(F_{MS}) = 3.811 \text{ dB}}$$

So,  $F_{MS}$  is 0.411 dB above  $F_{min} = 3.4$  dB. This might be perfectly acceptable.

How did we do for gain and VSWRs at the simultaneous complex conjugate match points?

$$GT_{max} := \frac{1}{1 - (|\Gamma_{MS}|)^2} \cdot (|S_{21}|)^2 \cdot \frac{\left[1 - (|\Gamma_{ML}|)^2\right]}{\left(|1 - S_{22} \cdot \Gamma_{ML}|^2\right)} \quad GT_{max} = 10.746 \quad \boxed{10 \cdot \log(GT_{max}) = 10.3125 \text{ dB}}$$

For comparison, the maximum stable (transducer) gain for the transistor is:

$$G_{MSG} := \frac{|S_{21}|}{|S_{12}|} \quad \boxed{G_{MSG} = 24.282} \quad \boxed{10 \cdot \log(G_{MSG}) = 13.853 \text{ dB}}$$


$$\Gamma_{IN} := S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_{ML}}{1 - S_{22} \cdot \Gamma_{ML}} \quad \boxed{|\Gamma_{IN}| = 0.7476} \quad \boxed{\arg(\Gamma_{IN}) \cdot \frac{180}{\pi} = 161.405 \text{ deg}}$$

$$\Gamma_{OUT} := S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_{MS}}{1 - S_{11} \cdot \Gamma_{MS}} \quad \boxed{|\Gamma_{OUT}| = 0.753} \quad \boxed{\arg(\Gamma_{OUT}) \cdot \frac{180}{\pi} = -68.19 \text{ deg}}$$

$$\Gamma_{a\_mag} := \left| \frac{\Gamma_{IN} - \overline{\Gamma_{MS}}}{1 - \Gamma_{IN} \cdot \Gamma_{MS}} \right| \quad VSWR_{IN} := \frac{1 + \Gamma_{a\_mag}}{1 - \Gamma_{a\_mag}} \quad \boxed{VSWR_{IN} = 1}$$

$$\Gamma_{b\_mag} := \left| \frac{\Gamma_{OUT} - \overline{\Gamma_{ML}}}{1 - \Gamma_{OUT} \cdot \Gamma_{ML}} \right| \quad VSWR_{OUT} := \frac{1 + \Gamma_{b\_mag}}{1 - \Gamma_{b\_mag}} \quad \boxed{VSWR_{OUT} = 1}$$

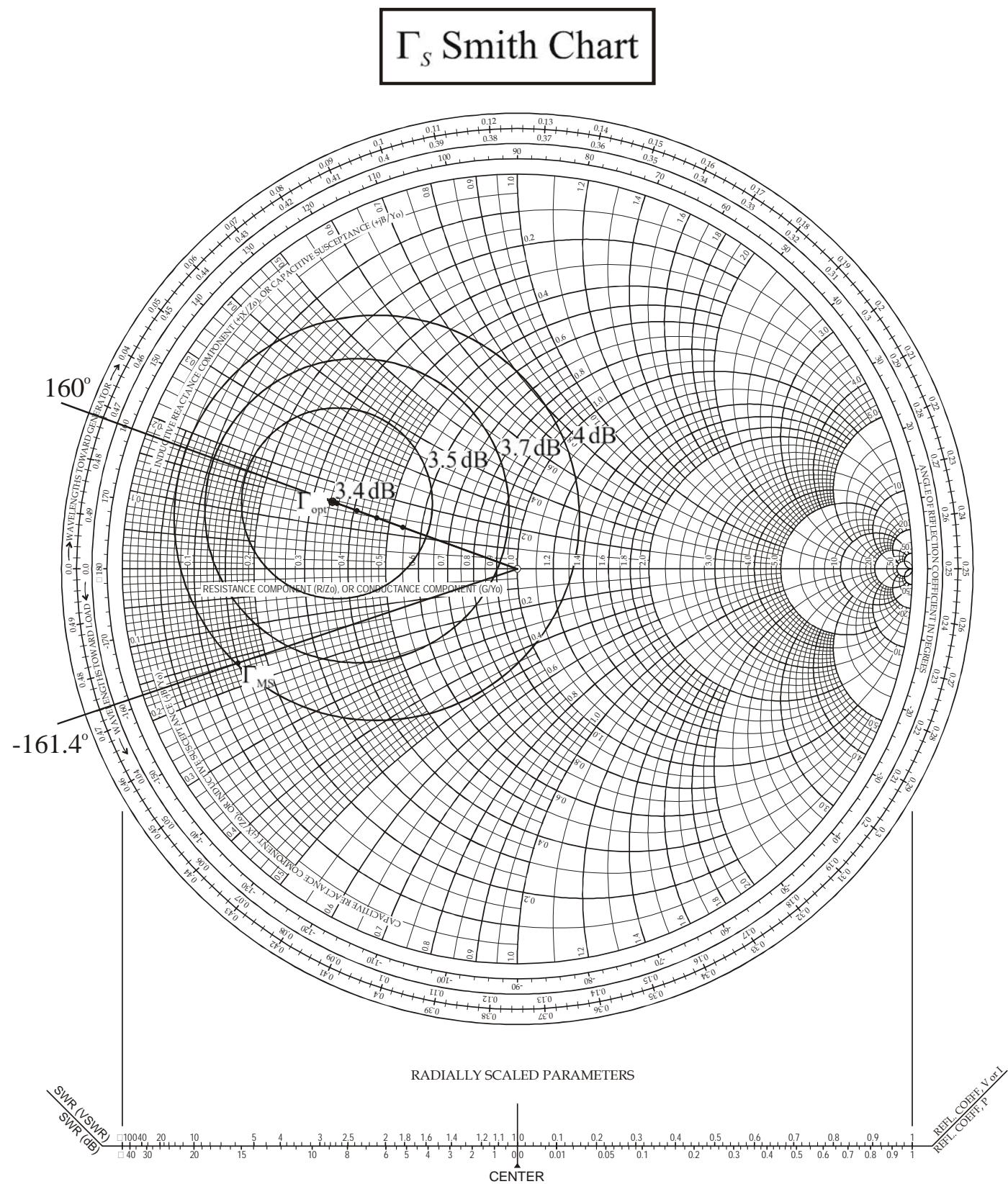The gains ( $G_{Tmax} = G_{Pmax} = G_{Amax}$ ) are a little above 10 dB and about 3.5 dB below the maximum stable gain. As expected,  $VSWR_{OUT} = VSWR_{IN} = 1$  at the simultaneous complex conjugate match points.



\*\*\*\*\*

How much gain and VSWR would we need to give up to achieve a lower noise figure?

Since we are working on the  $\Gamma_S$  Smith chart, let's plot circles of constant available power gain (in blue) for  $G_A = 9.4, 9.7 \text{ & } 10 \text{ dB}$ .

$$GA10 := 10^{\frac{10}{10}} \quad ga10 := \frac{GA10}{(|S_{21}|)^2} \quad GA10 = 10 \quad ga10 = 2.788$$

$$GA97 := 10^{\frac{9.7}{10}} \quad ga97 := \frac{GA97}{(|S_{21}|)^2} \quad GA97 = 9.333 \quad ga97 = 2.602$$

$$GA94 := 10^{\frac{9.4}{10}} \quad ga94 := \frac{GA94}{(|S_{21}|)^2} \quad GA94 = 8.71 \quad ga94 = 2.428$$

$$Ca10 := \frac{ga10 \cdot \overline{C1}}{1 + ga10 \cdot [(|S_{11}|)^2 - (|\Delta|)^2]} \quad Ca97 := \frac{ga97 \cdot \overline{C1}}{1 + ga97 \cdot [(|S_{11}|)^2 - (|\Delta|)^2]}$$

$$Ca94 := \frac{ga94 \cdot \overline{C1}}{1 + ga94 \cdot [(|S_{11}|)^2 - (|\Delta|)^2]}$$

$$ra10 := \frac{\left[ 1 - 2 \cdot K \cdot |S_{12} \cdot S_{21}| \cdot ga10 + (|S_{12} \cdot S_{21}|)^2 \cdot ga10^2 \right]^{0.5}}{\left| 1 + ga10 \cdot [(|S_{11}|)^2 - (|\Delta|)^2] \right|}$$

$$ra97 := \frac{\left[ 1 - 2 \cdot K \cdot |S_{12} \cdot S_{21}| \cdot ga97 + (|S_{12} \cdot S_{21}|)^2 \cdot ga97^2 \right]^{0.5}}{\left| 1 + ga97 \cdot [(|S_{11}|)^2 - (|\Delta|)^2] \right|}$$

$$ra94 := \frac{\left[ 1 - 2 \cdot K \cdot |S_{12} \cdot S_{21}| \cdot ga94 + (|S_{12} \cdot S_{21}|)^2 \cdot ga94^2 \right]^{0.5}}{\left| 1 + ga94 \cdot [(|S_{11}|)^2 - (|\Delta|)^2] \right|}$$

$$|Ca10| = 0.71821$$

$$\arg(Ca10) \cdot \frac{180}{\pi} = -161.4$$

deg

$$ra10 = 0.13494$$

$$|Ca97| = 0.69026$$

$$\arg(Ca97) \cdot \frac{180}{\pi} = -161.4$$

deg

$$ra97 = 0.19268$$

$$|Ca94| = 0.66262$$

$$\arg(Ca94) \cdot \frac{180}{\pi} = -161.4$$

deg

$$ra94 = 0.23951$$

Next, since we are working on the  $\Gamma_S$  Smith chart, let's plot circles of constant input VSWR (in red) for  $VSWR_{IN} = 1.5, 1.75 & 2$ .

$$\Gamma a15 := \frac{1.5 - 1}{1.5 + 1}$$

$$\Gamma a15 = 0.2$$

$$\Gamma a175 := \frac{1.75 - 1}{1.75 + 1}$$

$$\Gamma a175 = 0.2727$$

$$\Gamma a2 := \frac{2 - 1}{2 + 1}$$

$$\Gamma a2 = 0.3333$$

$$Cvi15 := \frac{\overline{\Gamma IN} \cdot (1 - \Gamma a15^2)}{1 - \Gamma a15^2 \cdot (|\Gamma IN|)^2}$$

$$rvi15 := \frac{\Gamma a15 \cdot [1 - (|\Gamma IN|)^2]}{1 - \Gamma a15^2 \cdot (|\Gamma IN|)^2}$$

$$Cvi175 := \frac{\overline{\Gamma IN} \cdot (1 - \Gamma a175^2)}{1 - \Gamma a175^2 \cdot (|\Gamma IN|)^2}$$

$$rvi175 := \frac{\Gamma a175 \cdot [1 - (|\Gamma IN|)^2]}{1 - \Gamma a175^2 \cdot (|\Gamma IN|)^2}$$

$$Cvi2 := \frac{\overline{\Gamma IN} \cdot (1 - \Gamma a2^2)}{1 - \Gamma a2^2 \cdot (|\Gamma IN|)^2}$$

$$rvi2 := \frac{\Gamma a2 \cdot [1 - (|\Gamma IN|)^2]}{1 - \Gamma a2^2 \cdot (|\Gamma IN|)^2}$$

$$|Cvi15| = 0.73411$$

$$\arg(Cvi15) \cdot \frac{180}{\pi} = -161.4$$

deg

$$rvi15 = 0.0902$$

$$|Cvi175| = 0.72201$$

$$\arg(Cvi175) \cdot \frac{180}{\pi} = -161.4$$

deg


$$rvi175 = 0.1255$$

$$|Cvi2| = 0.70854$$

$$\arg(Cvi2) \cdot \frac{180}{\pi} = -161.4$$

deg

$$rvi2 = 0.1568$$

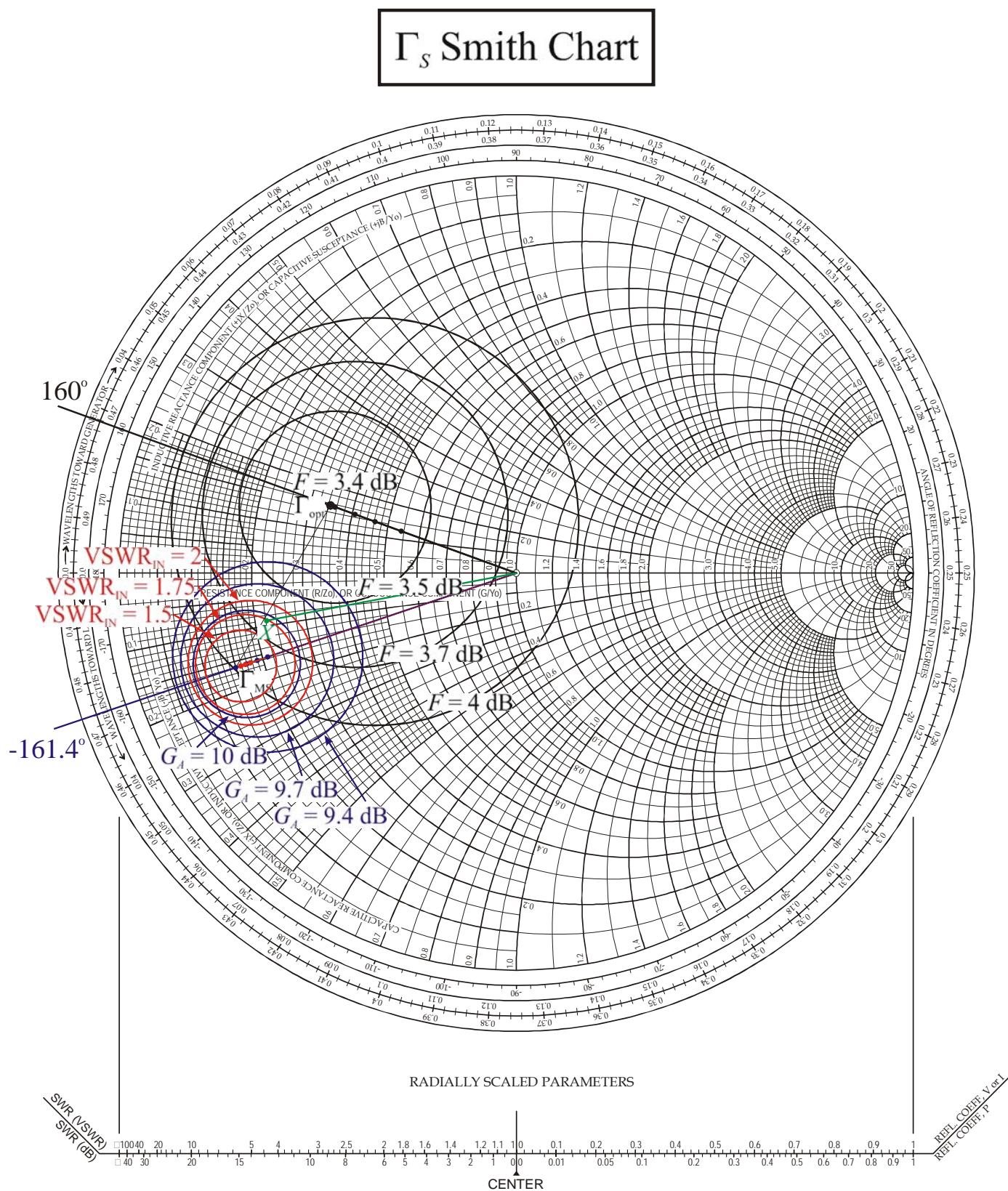

On examining the  $F$  (black),  $G_A$  (blue) and  $\text{VSWR}_{\text{IN}}$  (red) circles on the  $\Gamma_S$  Smith chart, let's select the point  $X$  (green) as a potential compromise and see how it works out for gains, VSWRs, and noise figure.

$$z_{SX} := 0.22 - j \cdot 0.09 \quad \Gamma_{SX} := \frac{z_{SX} - 1}{z_{SX} + 1}$$

$$|\Gamma_{SX}| = 0.6418$$

$$\arg(\Gamma_{SX}) \cdot \frac{180}{\pi} = -169.2$$

$$\Gamma_{OUTX} := S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_{SX}}{1 - S_{11} \cdot \Gamma_{SX}}$$

$$|\Gamma_{OUTX}| = 0.701$$

$$\arg(\Gamma_{OUTX}) \cdot \frac{180}{\pi} = -69.9$$

deg

Choose to complex conjugate match  $\Gamma_L$  to  $\Gamma_{OUTX}$  for best  $\text{VSWR}_{\text{OUT}}$ .

$$\Gamma_{LX} := \overline{\Gamma_{OUTX}}$$

$$|\Gamma_{LX}| = 0.7015$$

$$\arg(\Gamma_{LX}) \cdot \frac{180}{\pi} = 69.93$$

deg

$$\Gamma_{INX} := S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_{LX}}{1 - S_{22} \cdot \Gamma_{LX}}$$

$$|\Gamma_{INX}| = 0.727$$

$$\arg(\Gamma_{INX}) \cdot \frac{180}{\pi} = 162.4$$

deg

$$\Gamma_{aX} := \left| \frac{\Gamma_{INX} - \overline{\Gamma_{SX}}}{1 - \Gamma_{INX} \cdot \Gamma_{SX}} \right|$$

$$\Gamma_{aX} = 0.218$$

$$\text{VSWR\_INX} := \frac{1 + \Gamma_{aX}}{1 - \Gamma_{aX}}$$

$$\Gamma_{bX} := \left| \frac{\Gamma_{OUTX} - \overline{\Gamma_{LX}}}{1 - \Gamma_{OUTX} \cdot \Gamma_{LX}} \right|$$

$$\Gamma_{bX} = 0$$

$$\text{VSWR\_OUTX} := \frac{1 + \Gamma_{bX}}{1 - \Gamma_{bX}}$$

$$\boxed{\text{VSWR\_INX} = 1.559}$$

$$\boxed{\text{VSWR\_OUTX} = 1}$$

The input VSWR is now 1.559 (corresponds to a reflection coefficient magnitude of 0.218) which is not too bad while the output VSWR is still 1.

$$GTX := \frac{1 - (|\Gamma_{SX}|)^2}{(|1 - \Gamma_{INX} \cdot \Gamma_{SX}|)^2} \cdot (|S_{21}|)^2 \cdot \frac{1 - (|\Gamma_{LX}|)^2}{(|1 - S_{22} \cdot \Gamma_{LX}|)^2}$$

$$\boxed{|\Gamma_{TX}| = 10.1172}$$

$$\boxed{[10 \cdot \log(|\Gamma_{TX}|)] = 10.051 \text{ dB}}$$

$$GPX := \frac{1}{1 - (|\Gamma_{INX}|)^2} \cdot (|S_{21}|)^2 \cdot \frac{1 - (|\Gamma_{LX}|)^2}{(|1 - S_{22} \cdot \Gamma_{LX}|)^2}$$

$$\boxed{|\Gamma_{PX}| = 10.6244}$$

$$\boxed{[10 \cdot \log(|\Gamma_{PX}|)] = 10.263 \text{ dB}}$$

$$GAX := \frac{1 - (|\Gamma_{SX}|)^2}{(|1 - S_{11} \cdot \Gamma_{SX}|)^2} \cdot (|S_{21}|)^2 \cdot \frac{1}{1 - (|\Gamma_{OUTX}|)^2}$$

$$\boxed{|\Gamma_{AX}| = 10.1172}$$

$$\boxed{[10 \cdot \log(|\Gamma_{AX}|)] = 10.051 \text{ dB}}$$

The gains are only slightly below the the maximum transducer gain of 10.3125 dB .

$$FX := F + \frac{4 \cdot rn \cdot (|\Gamma_{SX} - \Gamma_{opt}|)^2}{\left[ 1 - (|\Gamma_{SX}|)^2 \right] \cdot \left[ 1 - (|\Gamma_{opt}|)^2 \right]}$$

$$\boxed{FX = 2.268}$$

$$\boxed{[10 \cdot \log(FX)] = 3.557 \text{ dB}}$$

The noise figure is only slightly above the minimum noise figure of 3.4 dB .

Not too bad of a compromise. Still have very good gains, VSWRs, and only a small degradation in the noise figure  $F$ .